

Contents

Preface xiii

Chapter 1 Introduction 2

- | | | | |
|-----|-----------------------------|-----|--------------------|
| 1-1 | The Three Kinds of Formulas | 1-5 | Thevenin's Theorem |
| 1-2 | Approximations | 1-6 | Norton's Theorem |
| 1-3 | Voltage Sources | 1-7 | Troubleshooting |
| 1-4 | Current Sources | | |

Chapter 2 Semiconductors 28

- | | | | |
|-----|---------------------------------------|------|-----------------------------------|
| 2-1 | Conductors | 2-9 | Forward Bias |
| 2-2 | Semiconductors | 2-10 | Reverse Bias |
| 2-3 | Silicon Crystals | 2-11 | Breakdown |
| 2-4 | Intrinsic Semiconductors | 2-12 | Energy Levels |
| 2-5 | Two Types of Flow | 2-13 | The Energy Hill |
| 2-6 | Doping a Semiconductor | 2-14 | Barrier Potential and Temperature |
| 2-7 | Two Types of Extrinsic Semiconductors | 2-15 | Reverse-Biased Diode |
| 2-8 | The Unbiased Diode | | |

Chapter 3 Diode Theory 58

- | | | | |
|-----|--------------------------|------|----------------------------------|
| 3-1 | Basic Ideas | 3-7 | Reading a Data Sheet |
| 3-2 | The Ideal Diode | 3-8 | How to Calculate Bulk Resistance |
| 3-3 | The Second Approximation | 3-9 | DC Resistance of a Diode |
| 3-4 | The Third Approximation | 3-10 | Load Lines |
| 3-5 | Troubleshooting | 3-11 | Surface-Mount Diodes |
| 3-6 | Up-Down Circuit Analysis | | |

Chapter 4 Diode Circuits 88

- | | | | |
|-----|--|------|---------------------------|
| 4-1 | The Half-Wave Rectifier | 4-8 | Other Power-Supply Topics |
| 4-2 | The Transformer | 4-9 | Troubleshooting |
| 4-3 | The Full-Wave Rectifier | 4-10 | Clippers and Limiters |
| 4-4 | The Bridge Rectifier | 4-11 | Clampers |
| 4-5 | The Choke-Input Filter | 4-12 | Voltage Multipliers |
| 4-6 | The Capacitor-Input Filter | | |
| 4-7 | Peak Inverse Voltage and Surge Current | | |

Chapter 5 Special-Purpose Diodes 142

- | | | | |
|-----|---------------------------------------|------|------------------------|
| 5-1 | The Zener Diode | 5-6 | Troubleshooting |
| 5-2 | The Loaded Zener Regulator | 5-7 | Load Lines |
| 5-3 | Second Approximation of a Zener Diode | 5-8 | Optoelectronic Devices |
| 5-4 | Zener Drop-Out Point | 5-9 | The Schottky Diode |
| 5-5 | Reading a Data Sheet | 5-10 | The Varactor |
| | | 5-11 | Other Diodes |

Chapter 6 Bipolar Junction Transistors 188

- | | | | |
|-----|-------------------------|------|---------------------------|
| 6-1 | The Unbiased Transistor | 6-7 | Transistor Approximations |
| 6-2 | The Biased Transistor | 6-8 | Reading Data Sheets |
| 6-3 | Transistor Currents | 6-9 | Surface-Mount Transistors |
| 6-4 | The CE Connection | 6-10 | Troubleshooting |
| 6-5 | The Base Curve | | |
| 6-6 | Collector Curves | | |

Chapter 7 Transistor Fundamentals 222

- | | | | |
|-----|----------------------------|------|-----------------------------|
| 7-1 | Variations in Current Gain | 7-7 | LED Drivers |
| 7-2 | The Load Line | 7-8 | The Effect of Small Changes |
| 7-3 | The Operating Point | 7-9 | Troubleshooting |
| 7-4 | Recognizing Saturation | 7-10 | More Optoelectronic Devices |
| 7-5 | The Transistor Switch | | |
| 7-6 | Emitter Bias | | |

Chapter 8 Transistor Biasing 260

- | | | | |
|------------|----------------------------------|------------|------------------------|
| 8-1 | Voltage-Divider Bias | 8-5 | Other Types of Bias |
| 8-2 | Accurate VDB Analysis | 8-6 | Troubleshooting |
| 8-3 | VDB Load Line and <i>Q</i> Point | 8-7 | <i>PNP</i> Transistors |
| 8-4 | Two-Supply Emitter Bias | | |

Chapter 9 AC Models 286

- | | | | |
|------------|------------------------------------|------------|---------------------------------|
| 9-1 | Base-Biased Amplifier | 9-6 | Two Transistor Models |
| 9-2 | Emitter-Biased Amplifier | 9-7 | Analyzing an Amplifier |
| 9-3 | Small-Signal Operation | 9-8 | AC Quantities on the Data Sheet |
| 9-4 | AC Beta | | |
| 9-5 | AC Resistance of the Emitter Diode | | |

Chapter 10 Voltage Amplifiers 318

- | | | | |
|-------------|---------------------------------------|-------------|--------------------|
| 10-1 | Voltage Gain | 10-4 | Swamped Amplifier |
| 10-2 | The Loading Effect of Input Impedance | 10-5 | Two-Stage Feedback |
| 10-3 | Multistage Amplifiers | 10-6 | Troubleshooting |

Chapter 11 CC and CB Amplifiers 344

- | | | | |
|-------------|---------------------|-------------|---------------------------|
| 11-1 | CC Amplifier | 11-4 | Darlington Connections |
| 11-2 | Output Impedance | 11-5 | Voltage Regulation |
| 11-3 | Cascading CE and CC | 11-6 | The Common-Base Amplifier |

Chapter 12 Power Amplifiers 376

- | | | | |
|-------------|------------------------------------|--------------|-------------------------------|
| 12-1 | Amplifier Terms | 12-6 | Biasing Class B/AB Amplifiers |
| 12-2 | Two Load Lines | 12-7 | Class B/AB Driver |
| 12-3 | Class A Operation | 12-8 | Class C Operation |
| 12-4 | Class B Operation | 12-9 | Class C Formulas |
| 12-5 | Class B Push-Pull Emitter Follower | 12-10 | Transistor Power Rating |

Chapter 13 JFETs 424

- | | | | |
|-------------|------------------------------|--------------|-------------------------|
| 13-1 | Basic Ideas | 13-7 | JFET Amplifiers |
| 13-2 | Drain Curves | 13-8 | The JFET Analog Switch |
| 13-3 | The Transconductance Curve | 13-9 | Other JFET Applications |
| 13-4 | Biasing in the Ohmic Region | 13-10 | Reading Data Sheets |
| 13-5 | Biasing in the Active Region | 13-11 | JFET Testing |
| 13-6 | Transconductance | | |

Chapter 14 MOSFETs 478

- | | | | |
|-------------|----------------------------------|--------------|---------------------|
| 14-1 | The Depletion-Mode MOSFET | 14-6 | Digital Switching |
| 14-2 | D-MOSFET Curves | 14-7 | CMOS |
| 14-3 | Depletion-Mode MOSFET Amplifiers | 14-8 | Power FETs |
| 14-4 | The Enhancement-Mode MOSFET | 14-9 | E-MOSFET Amplifiers |
| 14-5 | The Ohmic Region | 14-10 | MOSFET Testing |

Chapter 15 Thyristors 520

- | | | | |
|-------------|----------------------------------|-------------|--------------------------|
| 15-1 | The Four-Layer Diode | 15-5 | Bidirectional Thyristors |
| 15-2 | The Silicon Controlled Rectifier | 15-6 | IGBTs |
| 15-3 | The SCR Crowbar | 15-7 | Other Thyristors |
| 15-4 | SCR Phase Control | 15-8 | Troubleshooting |

Chapter 16 Frequency Effects 562

- | | | | |
|-------------|------------------------------------|--------------|---|
| 16-1 | Frequency Response of an Amplifier | 16-9 | Risetime-Bandwidth Relationship |
| 16-2 | Decibel Power Gain | 16-10 | Frequency Analysis of BJT Stages |
| 16-3 | Decibel Voltage Gain | 16-11 | Frequency Analysis of FET Stages |
| 16-4 | Impedance Matching | 16-12 | Frequency Effects of Surface-Mount Circuits |
| 16-5 | Decibels above a Reference | | |
| 16-6 | Bode Plots | | |
| 16-7 | More Bode Plots | | |
| 16-8 | The Miller Effect | | |

Chapter 17 Differential Amplifiers 618

- | | | | |
|-------------|------------------------------------|-------------|---------------------|
| 17-1 | The Differential Amplifier | 17-5 | Common-Mode Gain |
| 17-2 | DC Analysis of a Diff Amp | 17-6 | Integrated Circuits |
| 17-3 | AC Analysis of a Diff Amp | 17-7 | The Current Mirror |
| 17-4 | Input Characteristics of an Op Amp | 17-8 | The Loaded Diff Amp |

Chapter 18 Operational Amplifiers 660

- | | | | |
|-------------|----------------------------|-------------|----------------------------------|
| 18-1 | Introduction to Op Amps | 18-6 | Linear ICs |
| 18-2 | The 741 Op Amp | 18-7 | Op Amps as Surface-Mount Devices |
| 18-3 | The Inverting Amplifier | | |
| 18-4 | The Noninverting Amplifier | | |
| 18-5 | Two Op-Amp Applications | | |

Chapter 19 Negative Feedback 704

- | | | | |
|-------------|---------------------------------|-------------|--------------------|
| 19-1 | Four Types of Negative Feedback | 19-5 | The VCIS Amplifier |
| 19-2 | VCVS Voltage Gain | 19-6 | The ICIS Amplifier |
| 19-3 | Other VCVS Equations | 19-7 | Bandwidth |
| 19-4 | The ICVS Amplifier | | |

Chapter 20 Linear Op-Amp Circuits 734

- | | | | |
|-------------|---------------------------------|--------------|------------------------------------|
| 20-1 | Inverting-Amplifier Circuits | 20-7 | Current Boosters |
| 20-2 | Noninverting-Amplifier Circuits | 20-8 | Voltage-Controlled Current Sources |
| 20-3 | Inverter/Noninverter Circuits | | |
| 20-4 | Differential Amplifiers | 20-9 | Automatic Gain Control |
| 20-5 | Instrumentation Amplifiers | 20-10 | Single-Supply Operation |
| 20-6 | Summing Amplifier Circuits | | |

Chapter 21 Active Filters 782

- | | | | |
|-------------|-----------------------|-------------|--------------------|
| 21-1 | Ideal Responses | 21-3 | Passive Filters |
| 21-2 | Approximate Responses | 21-4 | First-Order Stages |

21-5	VCVS Unity-Gain Second-Order Low-Pass Filters	21-10	Bandstop Filters
21-6	Higher-Order Filters	21-11	The All-Pass Filter
21-7	VCVS Equal-Component Low-Pass Filters	21-12	Biquadratic and State-Variable Filters
21-8	VCVS High-Pass Filters		
21-9	MFB Bandpass Filters		

Chapter 22 Nonlinear Op-Amp Circuits 842

22-1	Comparators with Zero Reference	22-7	Waveform Generation
22-2	Comparators with Nonzero References	22-8	Another Triangular Generator
22-3	Comparators with Hysteresis	22-9	Active Diode Circuits
22-4	Window Comparator	22-10	The Differentiator
22-5	The Integrator	22-11	Class-D Amplifier
22-6	Waveform Conversion		

Chapter 23 Oscillators 890

23-1	Theory of Sinusoidal Oscillation	23-7	The 555 Timer
23-2	The Wien-Bridge Oscillator	23-8	Astable Operation of the 555 Timer
23-3	Other <i>RC</i> Oscillators	23-9	555 Circuits
23-4	The Colpitts Oscillator	23-10	The Phase-Locked Loop
23-5	Other <i>LC</i> Oscillators	23-11	Function Generator ICs
23-6	Quartz Crystals		

Chapter 24 Regulated Power Supplies 946

24-1	Supply Characteristics	24-5	Current Boosters
24-2	Shunt Regulators	24-6	DC-to-DC Converters
24-3	Series Regulators	24-7	Switching Regulators
24-4	Monolithic Linear Regulators		

Appendix A Mathematical Derivations 993

Answers Odd-Numbered Problems 999

Index 1007