

2. Both terminals of the resistance were connected to the same terminal of the battery, so they both will be at the same potential with the result that the potential difference across them will be zero, and there will be no current.