

3. Ohm's Law gives the relationship between potential difference, current, and resistance as

$$\Delta V = I R$$

$$\Delta V = (2.4 \text{ A}) (50 \Omega) = 120 \text{ V}$$