

Test 3

1. Implement each of the following function using only two-input NAND gates. NO GATE MAY BE USED AS A NOT GATE. The functions are in minimum sum of product form. Assume all inputs are available both uncomplemented and complemented.

a) (15) $f = w x' + w' y + y z' + x y' z$ (7 gates)

b) (15) $G = A B C E + A C' D E' + D' E + B D' + A' B' D$
(12 gates)

2. Find the minimum sum of products expression(s) for each of the following functions (that is, circle the terms on the map and write the algebraic expressions).

a) (10) one solution

		a b			
		00	01	11	10
c d	00	1		1	1
	01		1		
	11	1			
	10	1		1	1

b) (15) two solutions

		w x			
		00	01	11	10
y z	00	1			1
	01		1	1	1
	11		1	1	1
	10	1		1	1

3. (15) Find both minimum sum of product expressions for the following function. (Two copies of the map are given for your convenience.)

		a b			
		00	01	11	10
c d	00	1	1		1
	01		1	1	1
	11			1	1
	10	1	1	1	1

		a b			
		00	01	11	10
c d	00	1	1		1
	01		1	1	1
	11			1	1
	10	1	1	1	1

4. (15) For the following function (three copies of map shown).
- List all of the prime implicants. Indicate which, if any, are essential.
 - Find all four minimum sum of products expressions.

		w x			
	y z	00	01	11	10
00		X	1	X	1
01		X	1	X	
11			1	X	X
10				X	1

		w x			
	y z	00	01	11	10
00		X	1	X	1
01		X	1	X	
11			1	X	X
10				X	1

		w x			
	y z	00	01	11	10
00		X	1	X	1
01		X	1	X	
11			1	X	X
10				X	1

5. (15) For the following function, f , find BOTH minimum sum of products expressions and the minimum product of sums expression.

		w x			
	y z	00	01	11	10
00			1		
01		X	1		
11		X	1	1	X
10			1	X	

		w x			
	y z	00	01	11	10
00					
01					
11					
10					