
 


Test 7
All Problems worth 20%.

 1. For the following JK trailing-edge triggered flip flop with an active low clear, show the timing diagram for Q.
 - a) Assuming no PRE' or CLR' input.
 - b) With the PRE' and CLR' inputs shown.




2. For the following state table, complete the timing trace as far as you can

$q_1 q_2$	$q_1^* q_2^*$		z	
	x = 0	x = 1	x = 0	x = 1
00	01	00	0	0
01	10	01	1	0
10	00	11	1	1
11	10	10	0	0

x 0 0 1 1 0 0 0 1 0 1
 q_1 0
 q_2 0
z

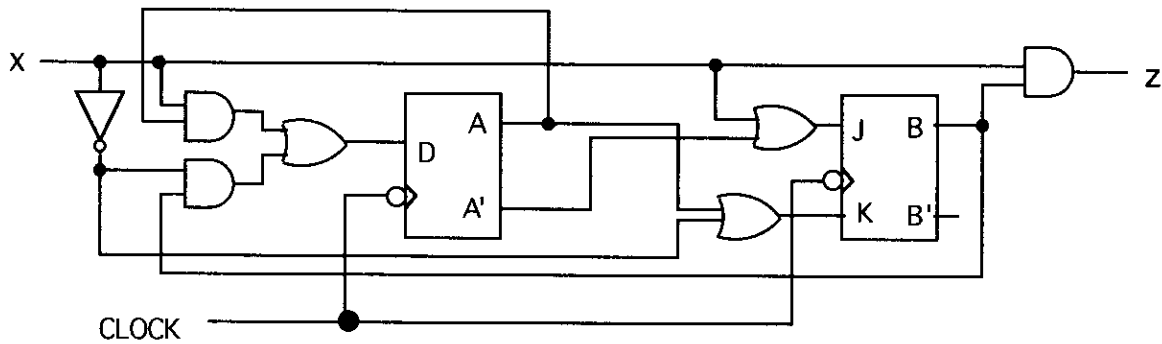3. For the following circuit, complete the state table. (Decide if you need one or two columns for z.)



A B	$A^* B^*$		z
	x = 0	x = 1	
00			
01			
10			
11			

4. For the following state table, design a system using a JK flip flop for A, a D flip flop for B, and AND, OR and NOT gate. Show the flip flop input equations and the output equation; you do NOT need to draw a block diagram.

A B	A* B*		z	
	x= 0	x= 1	x= 0	x= 1
0 0	0 1	0 1	0	0
0 1	0 1	1 0	1	0
1 0	1 1	0 0	1	1
1 1	1 0	1 0	0	0

5. For the following state table and state assignment, design a system using an JK flip flop for q_1 and a SR flip flop for q_2 . Show the flip flop input equations and the output equation; you do NOT need to draw a block diagram.

q	q *		z
	x = 0	x = 1	
A	C	B	0
B	B	A	1
C	A	B	1

q	q_1	q_2
A	0	0
B	1	1
C	0	1