1. Consider the following state table:

q	q	Z	
	x = 0	x = 1	.
Α	D	В	1
В	D	Α	1
С	E	Α	0
D	E	В	0
Е	D	С	0

a) (20) For each of the following partitions, indicate whether or not it is SP and whether or not it is output consistent.

$$P_1 = (A B C) (D E)$$

$$P_2 = (A B) (C D E)$$

$$P_3 = (A C) (B D) (E)$$

$$P_4 = (A B) (C) (D) (E)$$

$$P_5 = (ADE)(BC)$$

$$P_6 = (A) (B) (C) (D) (E)$$

$$P_7 = (A E) (B) (C D)$$

$$P_8 = (ABCDE)$$

$$P_9 = (A) (BC) (DE)$$

$$P_{10} = (A B) (C D) (E)$$

b) (10) Using one of these partitions, reduce the system to the one with the smallest number of states, showing a new state table.

2. (30) For the following state table, find all of the non-trivial SP partitions.

q	q	Z	
	x = 0	x = 1	
A	D	В	1
В	D	Α	1
С	Α	Α	0
D	D	С	0

3. For the following state table (with two different output columns shown)

q	q *		z ₁	z ₂
	x = 0	x = 1		
Α	В	E	0	1
В	Α	Ε	1	0
С	Α	D	0	1
D	С	Ε	1	1
Е	С	D	1	0

The non-trivial SP partitions are:

$$P_1 = (A B) (C) (D) (E)$$

$$P_2 = (ABC)(DE)$$

$$P_3 = (ADE)(BC)$$

$$P_4 = (A) (BC) (DE)$$

$$P_5 = (A)(B)(C)(DE)$$

$$P_6 = (A B) (C) (D E)$$

- a) (30) For output column z_1 , reduce the system to one with a minimum number of states. Show the reduced state table and list all of the non-trivial SP partitions of the reduced system.
- b) (10) For output column z_2 , show a state assignment that will likely lead to a solution with a minimum amount of logic. Explain briefly how you chose it. (For example, I chose q_2 according to an SP partition)