

## CHAPTER 8 - SECOND-ORDER CIRCUITS

List of topics for this chapter :

- Finding Initial Values
- The Source-Free Series RLC Circuit
- The Source-Free Parallel RLC Circuit
- Step Response of a Series RLC Circuit
- Step Response of a Parallel RLC Circuit
- General Second-Order Circuits
- Second-Order Op Amp Circuits

### FINDING INITIAL VALUES

**Problem 8.1** Given the circuit shown in Figure 8.1, which has existed for a long time, find  $v_{C1}(0)$ ,  $v_{C2}(0)$ ,  $i_{L1}(0)$ , and  $i_{L2}(0)$ .



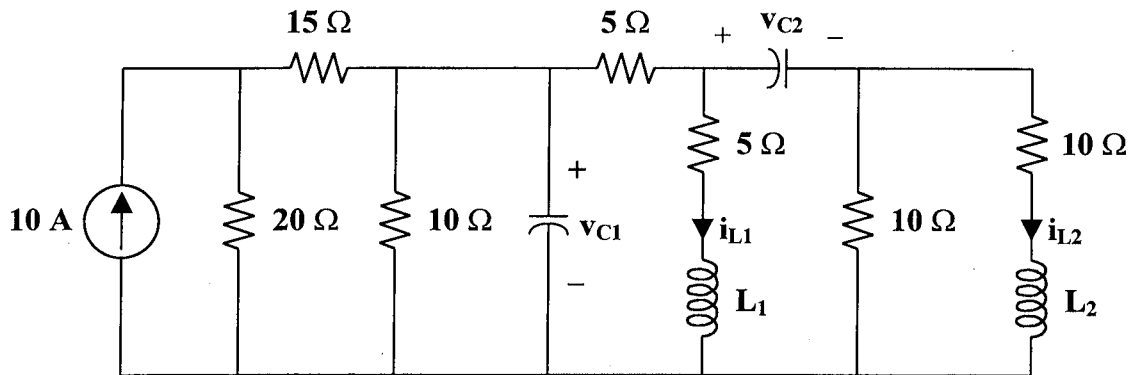


Figure 8.1

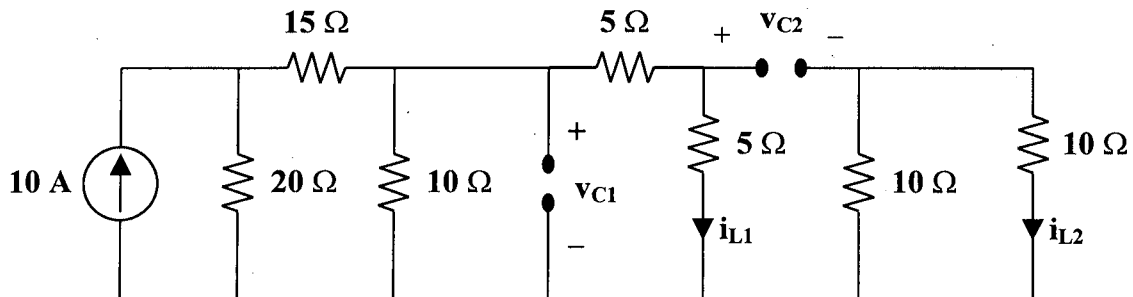When a circuit reaches steady state, an inductor looks like a short circuit and a capacitor looks like an open circuit. So, use the following circuit to find the initial values.



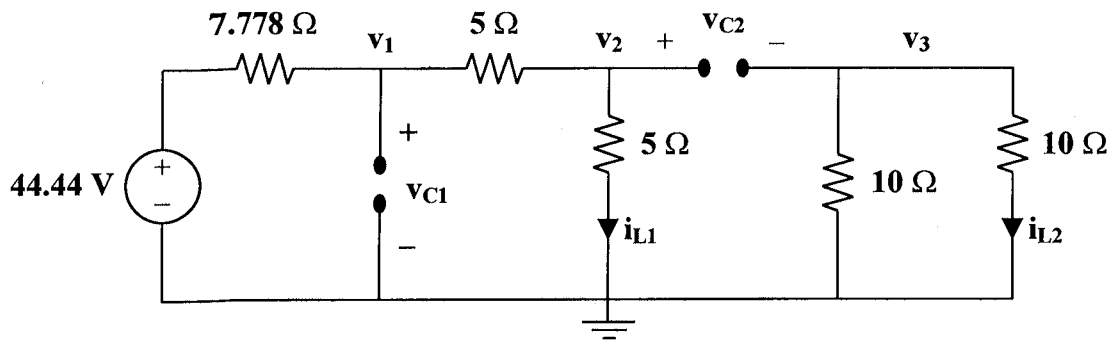Use source transformations to simplify the circuit.



Now, it is evident that

$$v_{C1}(0) = v_1 \qquad i_{L1}(0) = \frac{v_2}{5}$$

$$v_{C2}(0) = v_2 - v_3 \qquad i_{L2}(0) = \frac{v_3}{10}$$

Use nodal analysis to find  $v_1$ ,  $v_2$ , and  $v_3$ .

At node 1 :

$$\frac{v_1 - 44.44}{7.778} + \frac{v_1 - v_2}{5} = 0$$

$$5(v_1 - 44.44) + 7.778(v_1 - v_2) = 0$$

$$12.778v_1 - 7.778v_2 = 222.2$$

At node 2 :

$$\frac{v_2 - v_1}{5} + \frac{v_2}{5} = 0$$

$$-v_1 + 2v_2 = 0$$

$$v_2 = \frac{v_1}{2}$$

At node 3 :

$$\frac{v_3}{10} + \frac{v_3}{10} = 0$$

$$2v_3 = 0$$

$$v_3 = 0 \text{ volts}$$

Substitute the equation from node 2 into the equation for node 1.

$$12.778v_1 - 7.778 \frac{v_1}{2} = 222.2$$

$$8.889v_1 = 222.2$$

$$v_1 = 25 \text{ volts}$$

Then,

$$v_2 = \frac{v_1}{2} = \frac{25}{2} = 12.5 \text{ volts}$$

Therefore,

$$v_{C1}(0) = \underline{25 \text{ volts}}$$

$$i_{L1}(0) = \underline{2.5 \text{ amps}}$$

$$v_{C2}(0) = \underline{12.5 \text{ volts}}$$

$$i_{L2}(0) = \underline{0 \text{ amps}}$$

**Problem 8.2** Given the circuit shown in Figure 8.2, which has existed for a long time, find  $i_L(0)$  and  $v_C(0)$ .

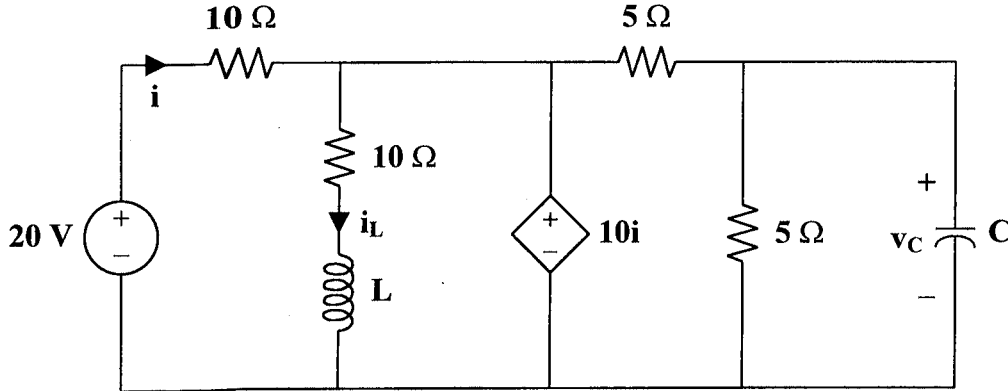


Figure 8.2

$$i_L(0) = \underline{1 \text{ amp}}$$

$$v_C(0) = \underline{5 \text{ volts}}$$

### THE SOURCE-FREE SERIES RLC CIRCUIT

**Problem 8.3** Given the circuit in Figure 8.3, which has reached steady state before the switch closes, find  $i(t)$  for all  $t > 0$ .

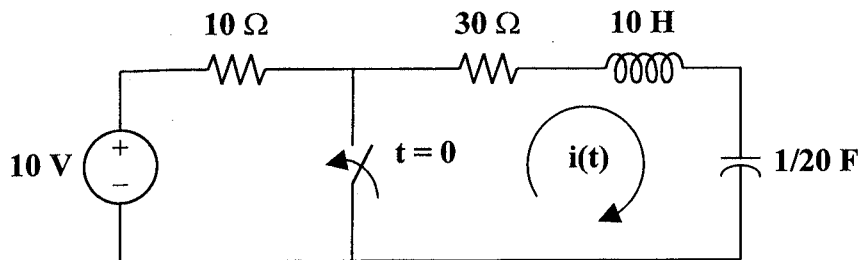


Figure 8.3

Use KVL to write a loop equation for  $t > 0$ .

$$Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt = 0$$

Multiply by  $1/L$  and differentiate with respect to time.

$$\frac{R}{L} \frac{di(t)}{dt} + \frac{d^2i(t)}{dt^2} + \frac{1}{LC} i(t) = 0$$

Rearranging the terms and inserting the values for R, L, and C,

$$\frac{d^2i(t)}{dt^2} + 3 \frac{di(t)}{dt} + 2i(t) = 0$$

Assume a solution of  $Ae^{st}$ .

$$s^2 Ae^{st} + 3sAe^{st} + 2Ae^{st} = 0$$

$$(s^2 + 3s + 2)Ae^{st} = 0$$

Thus,


$$(s+1)(s+2) = 0$$

which gives real and unequal roots at  $s_1 = -1$  and  $s_2 = -2$ .

Hence,

$$i(t) = A_1 e^{-t} + A_2 e^{-2t}$$

At  $t = 0^+$ , the circuit is

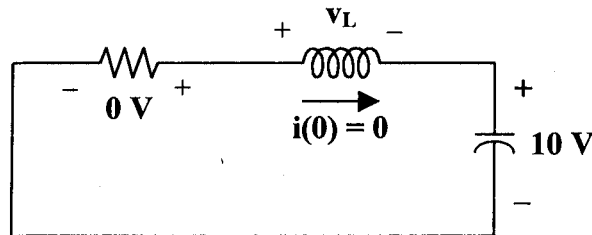

So,

$$i(0) = 0 = A_1 + A_2 \quad \text{or} \quad A_2 = -A_1$$

Also,

$$v_L(0^+) = 10 \frac{di(0)}{dt} = -10 \text{ volts} \quad \text{or} \quad \frac{di(0)}{dt} = -1$$

and

$$\frac{di(0)}{dt} = -A_1 e^0 - 2A_2 e^0 = -A_1 - 2A_2$$

So,

$$-1 = -A_1 - 2A_2 = -A_1 + 2A_1 = A_1$$

Hence,

$$A_1 = -1 \quad \text{and} \quad A_2 = 1$$

Therefore,

$$i(t) = \underline{(-e^{-t} + e^{-2t}) \text{ amps } \forall t > 0}$$

**Problem 8.4** Given the circuit in Figure 8.4, which has reached steady state before the switch closes, find  $i(t)$  for all  $t > 0$ .

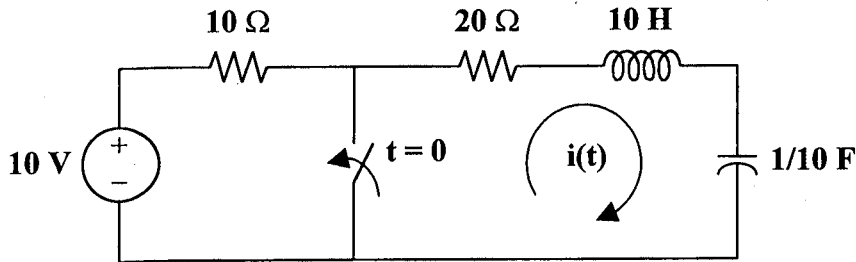


Figure 8.4

At  $t = 0^-$ ,

$$i(0^-) = i(0^+) = 0 \text{ amps} \quad \text{and} \quad v_C(0^-) = v_C(0^+) = 10 \text{ volts}$$

For  $t > 0$ ,

$$20i(t) + 10 \frac{di(t)}{dt} + \frac{1}{1/10} \int i(t) dt = 0$$

Multiply by  $1/10$ , differentiate with respect to time, and rearrange the terms.

$$\frac{d^2i(t)}{dt^2} + 2 \frac{di(t)}{dt} + i(t) = 0$$

Again, using a solution of  $Ae^{st}$ ,

$$s^2 Ae^{st} + 2sAe^{st} + Ae^{st} = 0$$

$$(s^2 + 2s + 1)Ae^{st} = 0$$

Thus,

$$(s+1)^2 = 0$$

which gives a real and repeated root at  $s_{1,2} = -1$ .

A repeated root gives the following solution,

$$i(t) = A_1 e^{-t} + A_2 t e^{-t}$$

At  $t = 0$ ,

$$i(0) = 0 = A_1 e^0 + A_2(0)e^0 = A_1 \quad \text{or} \quad A_1 = 0$$

Also,

$$v_L(0) = 10 \frac{di(0)}{dt} = -10 \quad \text{or} \quad \frac{di(0)}{dt} = -1$$

and 
$$\frac{di(0)}{dt} = 0 + A_2 e^0 - A_2(0) e^0 = A_2$$

Hence,

$$A_2 = -1$$

Therefore,

$$i(t) = \underline{(-te^{-t}) \text{ amps } \forall t > 0}$$

**Problem 8.5** Given the circuit in Figure 8.5, which has reached steady state before the switch closes, find  $i(t)$  for all  $t > 0$ .

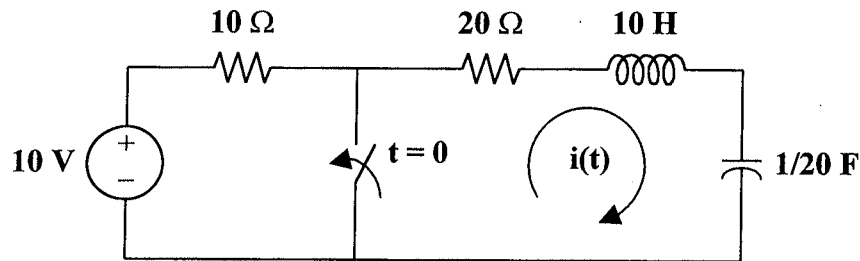


Figure 8.5

Writing a loop equation for  $t > 0$  gives,

$$20i(t) + 10 \frac{di(t)}{dt} + \frac{1}{1/20} \int i(t) dt = 0$$

Multiply by  $1/10$ , differentiate with respect to time, and rearrange the terms.

$$\frac{d^2 i(t)}{dt^2} + 2 \frac{di(t)}{dt} + 2i(t) = 0$$

Again, using a solution of  $Ae^{st}$ ,

$$\begin{aligned} s^2 Ae^{st} + 2sAe^{st} + 2Ae^{st} &= 0 \\ (s^2 + 2s + 2)Ae^{st} &= 0 \end{aligned}$$

Thus,

$$(s+1+j)(s+1-j) = 0$$

which gives complex roots at  $s_{1,2} = -1 \mp j$ .

Hence, we have a solution

$$i(t) = A_1 e^{(-1-j)t} + A_2 e^{(-1+j)t}$$

At  $t = 0$ ,

$$i(0) = 0 = A_1 e^0 + A_2 e^0 = A_1 + A_2 \quad \text{or} \quad A_2 = -A_1$$

Also,

$$\frac{di(0)}{dt} = -1 = (-1 - j)A_1 e^0 + (-1 + j)A_2 e^0$$

Using  $A_2 = -A_1$ , we get

$$-1 = (-1 - j)A_1 + (-1 + j)(-A_1)$$

$$-1 = (-1 - j + 1 - j)A_1 = -2jA_1$$

or  $A_1 = \frac{1}{2j}$  and  $A_2 = \frac{-1}{2j}$

Therefore,

$$i(t) = \frac{1}{2j} e^{(-1-j)t} + \frac{-1}{2j} e^{(-1+j)t}$$

$$i(t) = -e^{-t} \left\{ \frac{e^{jt} - e^{-jt}}{2j} \right\}$$

$$i(t) = \underline{(-e^{-t} \sin(t)) \text{ amps } \forall t > 0}$$

---



---

### THE SOURCE-FREE PARALLEL RLC CIRCUIT

**Problem 8.6** Given the circuit in Figure 8.6, find  $v_C(t)$  for all  $t > 0$ .

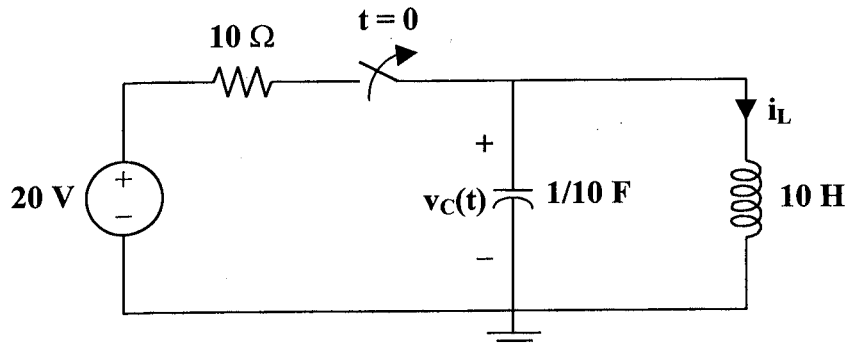


Figure 8.6


➤ **Carefully DEFINE the problem.**

Each component is labeled, indicating the value and polarity. The problem is clear.

➤ **PRESENT everything you know about the problem.**

The goal of the problem is to find  $v_C(t)$  for all  $t > 0$ .

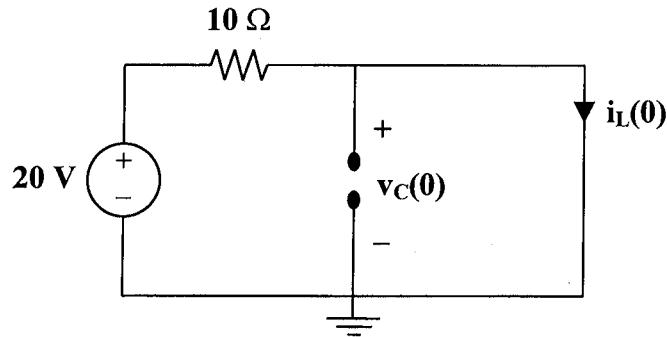
There is a switch which opens at  $t = 0$ . So, there are two circuits. The first circuit, when the switch is closed, is used to find the initial values of the capacitor and inductor. Note that there is a dc source. At dc, a capacitor is an open circuit and an inductor is a short circuit. Thus, we have the following circuit.



Recall that the voltage of a capacitor cannot change instantaneously and the current through an inductor cannot change instantaneously.

$$v_C(0) = v_C(0^-) = v_C(0^+) \quad \text{and} \quad i_L(0) = i_L(0^-) = i_L(0^+)$$

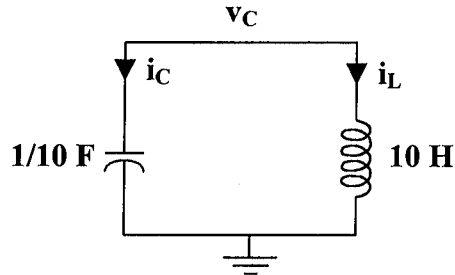The second circuit, after the switch opens, is used to find the final solution.



➤ **Establish a set of ALTERNATIVE solutions and determine the one that promises the greatest likelihood of success.**

The first circuit was simplified by applying the characteristics of capacitors and inductors with a dc source. Ohm's law should provide the answer you need when the circuit consists of a dc voltage source and a resistor.


For the second circuit, there is only one node or one loop. In this case, the use of KCL or KVL should provide the desired equation to find the solution to the problem. Because the components are in parallel, the voltage across each component is the same. So, use KCL to find the currents in terms of the voltage  $v_C$ .

➤ **ATTEMPT a problem solution.**

Begin by finding the initial values of the capacitor and inductor.



At  $t = 0$ ,

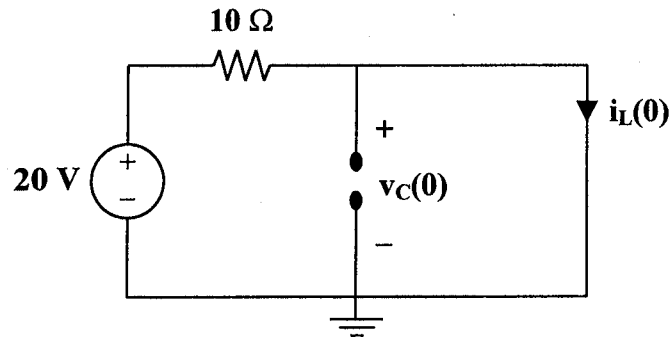


It is evident from the circuit that

$$v_C(0) = 0 \text{ volts.}$$

Using Ohm's law,

$$i_L(0) = 20/10 = 2 \text{ amps}$$

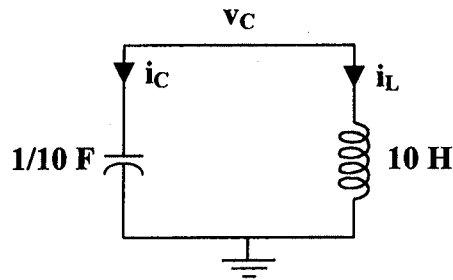After the switch opens, the circuit becomes



Using KCL,

$$i_C + i_L = 0$$
$$\frac{1}{10} \frac{d(v_C - 0)}{dt} + \frac{1}{10} \int (v_C - 0) dt = 0$$

Multiply both sides of the equation by 10 and differentiate both sides with respect to time.

$$\frac{d^2 v_C}{dt^2} + v_C = 0$$

but  $Ae^{st}$  must be a solution.

Substituting,

$$\frac{d^2(Ae^{st})}{dt^2} + Ae^{st} = 0$$
$$s^2 Ae^{st} + Ae^{st} = 0$$
$$(s^2 + 1)Ae^{st} = 0$$

Thus,

$$(s^2 + 1) = (s - j)(s + j) = 0$$

which gives complex roots at  $s_1, s_2 = \pm j$

So, we have a solution

$$v_C(t) = A_1 e^{jt} + A_2 e^{-jt}$$

Now, to solve for  $A_1$  and  $A_2$ .

$$v_C(0) = A_1 + A_2 = 0 \quad \text{or} \quad A_2 = -A_1$$

Now,

$$v_C(t) = A_1 e^{jt} - A_1 e^{-jt}$$

$$i_C(0) = -i_L(0) = -2 \text{ amps}$$

$$i_C(0) = \frac{1}{10} \frac{dv_C(0)}{dt} = \frac{1}{10} (jA_1 e^0 + jA_1 e^0)$$

or 
$$\frac{j2A_1}{10} = -2$$

Hence,

$$A_1 = \frac{-20}{j2} = \frac{-10}{j} = j10$$

Therefore,

$$\begin{aligned} v_C(t) &= j10e^{jt} - j10e^{-jt} \\ v_C(t) &= 10 [e^{j90^\circ} e^{jt} + e^{-j90^\circ} e^{-jt}] \\ v_C(t) &= 10 [e^{j(t+90^\circ)} + e^{-j(t+90^\circ)}] \\ v_C(t) &= 10 [2 \cos(t+90^\circ)] \\ v_C(t) &= 20 \cos(t+90^\circ) \text{ volts } \forall t > 0 \end{aligned}$$

➤ **EVALUATE the solution and check for accuracy.**

The circuit must satisfy the conservation of energy. In this case, the energy supplied from one component is absorbed by the other component.

Recall, from Chapter 6 – Capacitors and Inductors, that the energy stored in a capacitor is

$$w = \frac{1}{2} C v^2$$

and the energy stored in an inductor is

$$w = \frac{1}{2} L i^2$$

Thus,

$$w = \frac{1}{2} C v^2 = \left(\frac{1}{2}\right)\left(\frac{1}{10}\right)(20)^2 = 20 \text{ joules}$$

and

$$w = \frac{1}{2} L i^2 = \left(\frac{1}{2}\right)(10)(2)^2 = 20 \text{ joules}$$

These two answers match. This circuit satisfies conservation of energy.

- **Has the problem been solved SATISFACTORILY? If so, present the solution; if not, then return to “ALTERNATIVE solutions” and continue through the process again.** This problem has been solved satisfactorily.

$$v_c(t) = \underline{20 \cos(t + 90^\circ) \text{ volts } \forall t > 0}$$

**Problem 8.7** [8.23] In the circuit in Figure 8.7, calculate  $i_o(t)$  and  $v_o(t)$  for  $t > 0$ .


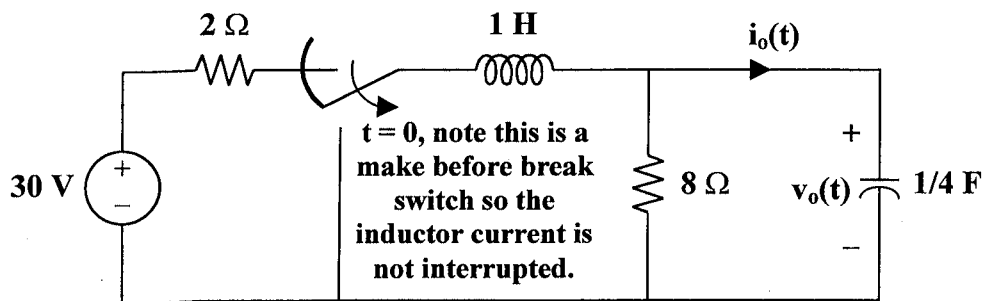



Figure 8.7

At  $t = 0$ ,

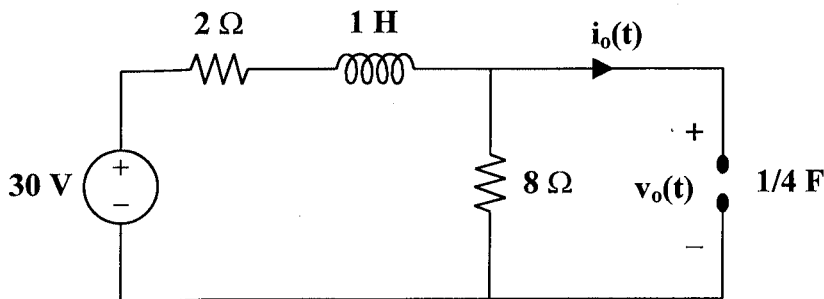

$$v_o(0) = \frac{8}{2+8} (30) = 24 \quad \text{and} \quad i_o(0) = 0$$

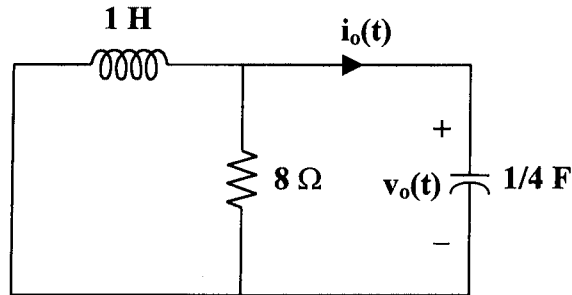For  $t > 0$ , we have a source-free parallel RLC circuit.



$$\alpha = \frac{1}{2RC} = \frac{1}{(2)(8)(1/4)} = \frac{1}{4}$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1)(1/4)}} = 2$$

Since  $\alpha$  is less than  $\omega_o$ , we have an underdamped response with a damping frequency of

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2} = \sqrt{4 - (1/16)} = 1.9843$$

and the natural response is

$$v_o(t) = (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)) e^{-\alpha t}$$

Use the initial values to find the unknowns.

$$v_o(0) = 24 = A_1$$

Also,

$$i_o(0) = C \frac{dv_o(0)}{dt} = 0$$

where  $\frac{dv_o}{dt} = -\alpha(A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)) e^{-\alpha t} + (-\omega_d A_1 \sin(\omega_d t) + \omega_d A_2 \cos(\omega_d t)) e^{-\alpha t}$

So,

$$\frac{dv_o(0)}{dt} = 0 = -\alpha A_1 + \omega_d A_2$$

Thus,

$$A_2 = \frac{\alpha}{\omega_d} A_1 = \frac{(1/4)(24)}{1.9843} = 3.024$$

Therefore,

$$v_o(t) = \underline{\underline{[(24 \cos(\omega_d t) + 3.024 \sin(\omega_d t)) e^{-t/4}] \text{ volts } \forall t > 0}}$$

**Problem 8.8** Given the circuit in Figure 8.8, which has reached steady state before the switch closes, find  $v(t)$  for all  $t > 0$ .

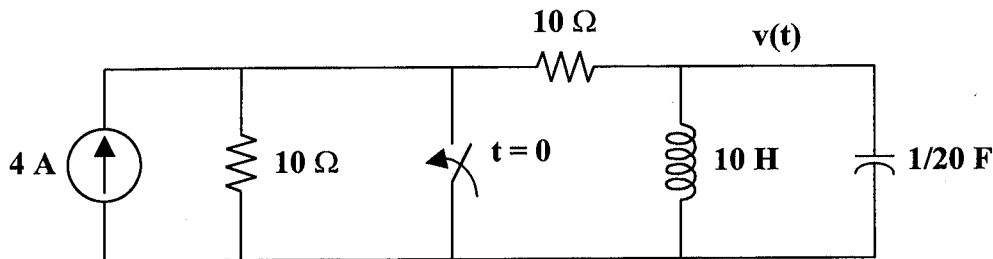


Figure 8.8

$$\underline{v(t) = 40e^{-t} \cos(t + 90^\circ) \text{ volts } \forall t > 0}$$

### STEP RESPONSE OF A SERIES RLC CIRCUIT

**Problem 8.9** [8.25] A branch voltage in a series RLC circuit is described by

$$\frac{d^2v}{dt^2} + 4 \frac{dv}{dt} + 8v = 24$$

If the initial conditions are  $v(0) = 0 = \frac{dv(0)}{dt}$ , find  $v(t)$ .

Recall the general loop equation for a series RLC circuit.

$$L \frac{di}{dt} + Ri + v = V_s$$

where  $i = C dv/dt$ . Then,

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}$$

The complete response of this circuit has a forced response and a natural response. To find the forced response, realize that  $8V_s = 24$  which means that  $V_s = 3$ . This is the forced response.

Now, to find the natural response, let  $V_s = 0$  and

$$\begin{aligned} \frac{d^2v}{dt^2} + 4 \frac{dv}{dt} + 8v &= 0 \\ (s^2 + 4s + 8)v &= 0 \end{aligned}$$

Thus,

$$s^2 + 4s + 8 = 0$$

which gives complex roots at  $s_{1,2} = \frac{-4 \pm \sqrt{16 - 32}}{2} = -2 \pm j2$ .

So, we have the solution

$$v(t) = V_s + (A_1 \cos(2t) + A_2 \sin(2t))e^{-2t}$$

Solve for the unknowns.

$$v(0) = 0 = V_s + A_1 = 3 + A_1 \quad \text{or} \quad A_1 = -3$$


$$\frac{dv}{dt} = -2(A_1 \cos(2t) + A_2 \sin(2t))e^{-2t} + (-2A_1 \sin(2t) + 2A_2 \cos(2t))e^{-2t}$$

$$\frac{dv(0)}{dt} = 0 = -2A_1 + 2A_2 \quad \text{or} \quad A_2 = A_1 = -3$$

Therefore,

$$v(t) = \underline{[3 - 3(\cos(2t) + \sin(2t))e^{-2t}] \text{ volts}}$$

**Problem 8.10** [8.31] Calculate  $i(t)$  for  $t > 0$  using the circuit in Figure 8.9.

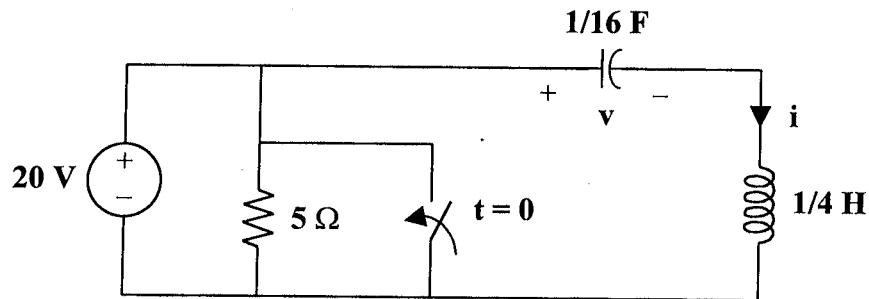


**Figure 8.9**

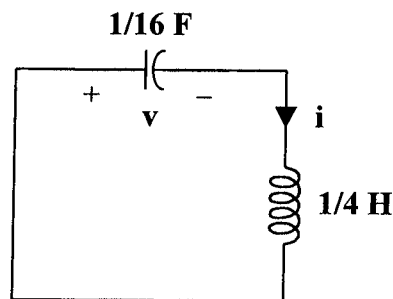Before  $t = 0$ , the capacitor acts like an open circuit while the inductor acts like a short circuit.

$$i(0) = 0 \text{ amps and } v(0) = 20 \text{ volts}$$

For  $t > 0$ , the LC circuit is disconnected from the voltage source as shown below.



This is a lossless, source-free series RLC circuit.

$$\alpha = \frac{R}{2L} = 0 \quad \omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1/16) + (1/4)}} = 8$$

$$s = -\alpha \pm j\omega_d = -\alpha \pm j\sqrt{\omega_o^2 - \alpha^2} = \pm j\omega_o = \pm j8$$

Since  $\alpha$  is equal to zero, we have an undamped response. Hence,

$$i(t) = A_1 \cos(8t) + A_2 \sin(8t)$$

where  $i(0) = 0 = A_1$ .

So,

$$i(t) = A_2 \sin(8t)$$

To solve for  $A_2$ , we know that

$$\frac{di(0)}{dt} = \frac{1}{L} v_L(0) = \frac{-1}{L} v(0) = (-4)(20) = -80$$

However,

$$\frac{di}{dt} = 8A_2 \cos(8t)$$

and  $\frac{di(0)}{dt} = -80 = 8A_2$

which leads to  $A_2 = -10$ .

Therefore,

$$i(t) = \underline{-10 \sin(8t) \text{ amps } \forall t > 0}$$

---

## STEP RESPONSE OF A PARALLEL RLC CIRCUIT

---

**Problem 8.11** Given the circuit in Figure 8.10, find  $v(t)$  for all  $t > 0$ .

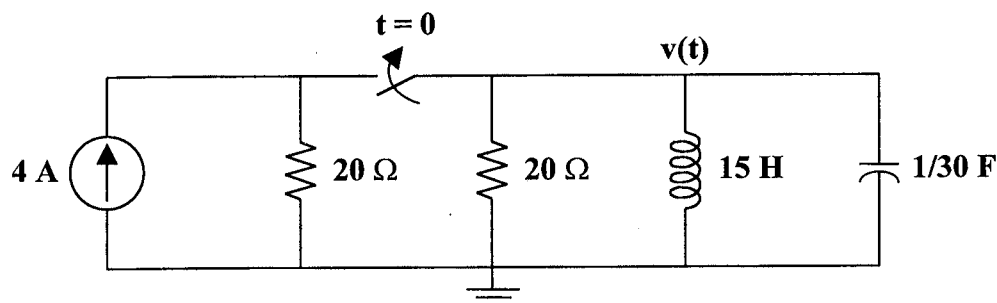


Figure 8.10

$$v(t) = (120e^{-t} - 120e^{-2t}) \text{ volts } \forall t > 0$$

**Problem 8.12** Given the circuit in Figure 8.11, find  $v(t)$  for all  $t > 0$ .

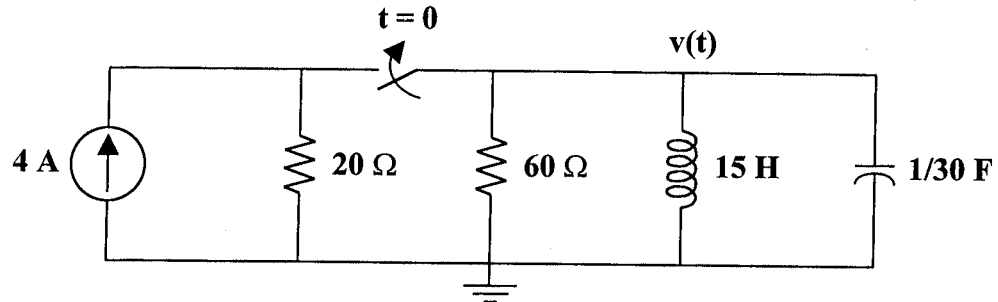


Figure 8.11

At  $t = 0^-$ ,  
 $v_C(0) = 0$  volts and  $i_L(0) = 0$  amps.

At  $t = 0^+$ ,  
 $v_C = v_L = v_R = 0$  volts


So, the 4 amp current source must all go through the capacitor or  
 $i_C(0^+) = 4$  amps.

Hence,

$$C \frac{dv(0^+)}{dt} = i_C(0^+) = 4$$

or 
$$\frac{dv(0^+)}{dt} = \frac{4}{C} = \frac{4}{1/30} = 120 \text{ volts/sec}$$

For  $t > 0$ , the circuit becomes

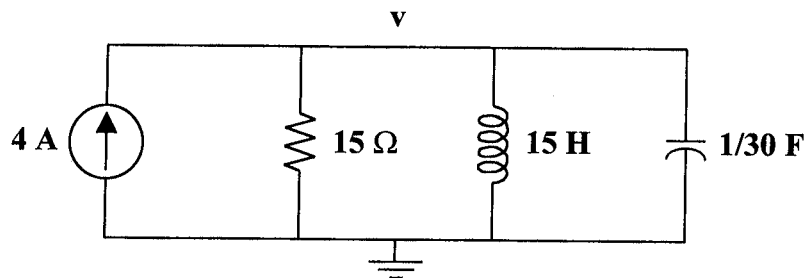

where the 20 ohm resistor in parallel with the 60 ohm resistor is equivalent to a 15 ohm resistor.



Using nodal analysis,

$$-4 + \frac{v-0}{15} + \frac{1}{15} \int (v-0) dt + \frac{1}{30} \frac{d(v-0)}{dt} = 0$$

Multiplying by 30 and differentiating with respect to time yields

$$\frac{d^2v}{dt^2} + 2 \frac{dv}{dt} + 2v = 0$$

Substituting the solution of  $Ae^{st}$  produces

$$\begin{aligned} s^2 Ae^{st} + 2sAe^{st} + 2Ae^{st} &= 0 \\ (s^2 + 2s + 2)Ae^{st} &= 0 \end{aligned}$$

Hence,

$$s^2 + 2s + 2 = (s+1+j)(s+1-j) = 0$$

which gives complex roots at  $s_{1,2} = -1 \mp j$ .

So, we have the solution

$$v(t) = A_1 e^{-(1+j)t} + A_2 e^{-(1-j)t}$$

At  $t = 0$ ,

$$v(0) = A_1 e^0 + A_2 e^0 = A_1 + A_2 = 0 \quad \text{or} \quad A_2 = -A_1$$

Also,

$$\begin{aligned} \frac{dv(0)}{dt} &= [-(1+j)] A_1 - [-(1-j)] A_1 = 120 \\ -A_1 - jA_1 + A_1 - jA_1 &= -2jA_1 = 120 \\ A_1 &= \frac{120}{-2j} = 60j = 60e^j \quad \text{and} \quad A_2 = -A_1 = 60e^{-j} \end{aligned}$$


Therefore,

$$\begin{aligned} v(t) &= 60e^j e^{-(1+j)t} + 60e^{-j} e^{-(1-j)t} \\ &= 60e^{-t} \{ e^{-jt+j} + e^{jt-j} \} \\ &= 60e^{-t} [2 \cos(t - 90^\circ)] \\ v(t) &= \underline{120e^{-t} \cos(t - 90^\circ) \text{ volts } \forall t > 0} \end{aligned}$$

The answer can also be written as

$$v(t) = \underline{120e^{-t} \sin(t) \text{ volts } \forall t > 0}$$

**Problem 8.13** Given the circuit in Figure 8.12, find  $v(t)$  for all  $t > 0$ .

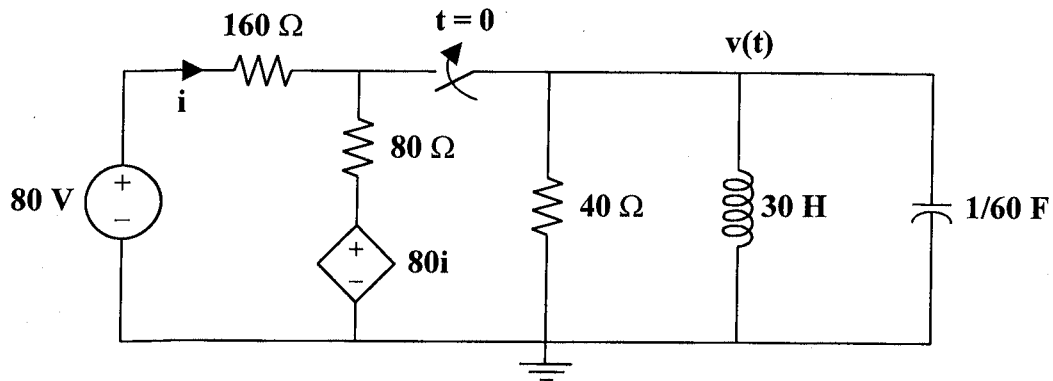


**Figure 8.12**

At  $t = 0$ ,

$$i_L(0) = 0 \text{ amps} \quad \text{and} \quad v_C(0) = 0 \text{ volts}$$

For complicated circuits that can be simplified using either a Thevenin or Norton equivalent, do so immediately!

Solving for  $V_{oc}$ ,

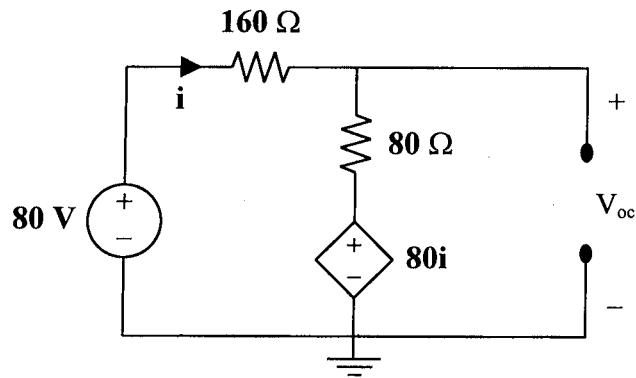

Using nodal analysis,

$$\frac{V_{oc} - 80}{160} + \frac{V_{oc} - 80i}{80} = 0$$

$$(V_{oc} - 80) + 2(V_{oc} - 80i) = 0$$

$$3V_{oc} - 80 - 160i = 0$$

where  $i = \frac{80 - V_{oc}}{160}$ .

Hence,


$$3V_{oc} = 80 + 160 \left( \frac{80 - V_{oc}}{160} \right)$$

$$3V_{oc} = 80 + (80 - V_{oc})$$

$$4V_{oc} = 160$$

$$V_{oc} = 40 \text{ volts}$$

Solving for  $I_{sc}$ ,

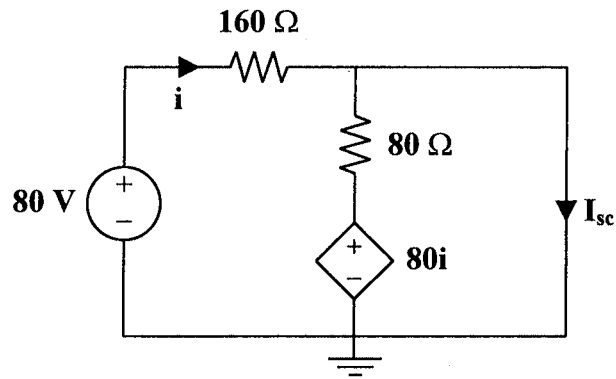

Using KCL,

$$I_{sc} = \frac{80 - 0}{160} + \frac{80i - 0}{80}$$

where  $i = \frac{80 - 0}{160} = \frac{1}{2}$  amp

Hence,

$$I_{sc} = \frac{80}{160} + \frac{80i}{80} = \frac{1}{2} + i = \frac{1}{2} + \frac{1}{2} = 1 \text{ amp}$$


Finding a Norton equivalent circuit,

$$I_N = I_{sc} = 1 \text{ amp}$$


and

$$R_{eq} = R_N = \frac{V_{oc}}{I_{sc}} = \frac{40}{1} = 40 \text{ ohms}$$

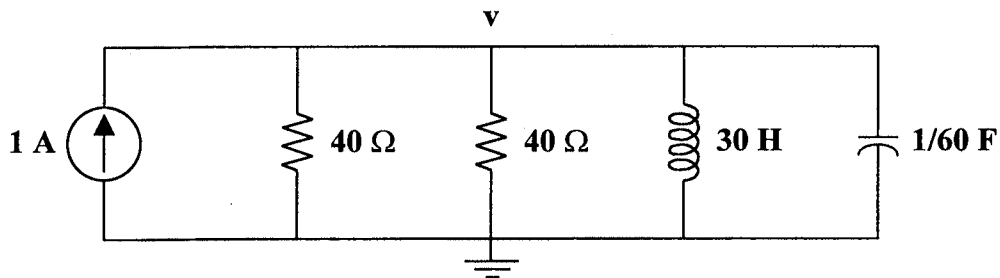Now, we can work with the following simplified circuit,



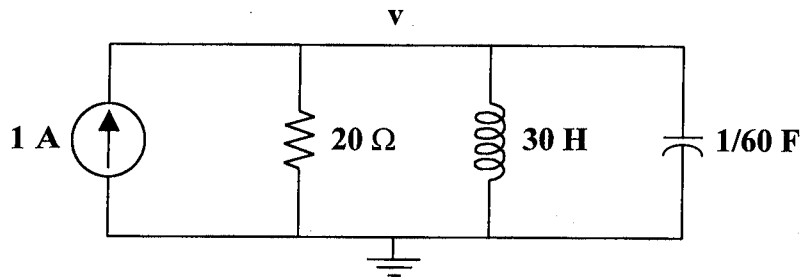The two 40 ohm resistors in parallel convert to a 20 ohm resistor, so we can simplify the circuit further to become



Writing a single node equation results in

$$-1 + \frac{v-0}{20} + \frac{1}{30} \int (v-0) dt + \frac{1}{60} \frac{d(v-0)}{dt} = 0$$

Multiplying by 60 and differentiating with respect to time leads to

$$\frac{d^2v}{dt^2} + 3 \frac{dv}{dt} + 2v = 0$$

Substituting the solution  $Ae^{st}$ , we get

$$\begin{aligned} s^2 Ae^{st} + 3sAe^{st} + 2Ae^{st} &= 0 \\ (s^2 + 3s + 2)Ae^{st} &= 0 \end{aligned}$$

Hence,

$$s^2 + 3s + 2 = (s+1)(s+2) = 0$$

which gives real and unequal roots at  $s_1 = -1$  and  $s_2 = -2$ .

So, we have the solution

$$v(t) = A_1 e^{-t} + A_2 e^{-2t}$$

At  $t = 0$ ,

$$v(0) = 0 \text{ volts} \quad \text{and} \quad i_L(0) = 0 \text{ amps.}$$

Since  $v(0) = 0$  volts,

$$v_R = 0 \text{ volts} \quad \text{and} \quad i_R = 0 \text{ amps.}$$

Hence, the entire 1 amp of current flows through the capacitor. So, we have

$$i_c(0) = 1 \text{ amp} \quad \text{and} \quad i_c(0) = C \frac{dv(0)}{dt}$$

Thus,

$$\frac{dv(0)}{dt} = \frac{1}{C} i_c(0) = \frac{1}{1/60} (1) = 60 \text{ volts/sec}$$

$$\text{but} \quad \frac{dv(0)}{dt} = -A_1 e^0 - 2A_2 e^0 = -A_1 - 2A_2 = 60$$

Also,

$$v(0) = A_1 e^0 + A_2 e^0 = A_1 + A_2 = 0$$

implies that  $A_2 = -A_1$ .

So,

$$-A_1 - 2A_2 = 60$$

or  $-A_1 + 2A_1 = A_1 = 60$

Hence,

$$A_1 = 60 \quad \text{and} \quad A_2 = -60.$$

Therefore,

$$v(t) = \underline{(60e^{-t} - 60e^{-2t}) \text{ volts } \forall t > 0}$$

The power of using a Norton equivalent circuit is clearly demonstrated by this problem.

---

---

## GENERAL SECOND-ORDER CIRCUITS

**Problem 8.14** Given the circuit in Figure 8.13, find  $v_c(t)$  for all  $t > 0$ .

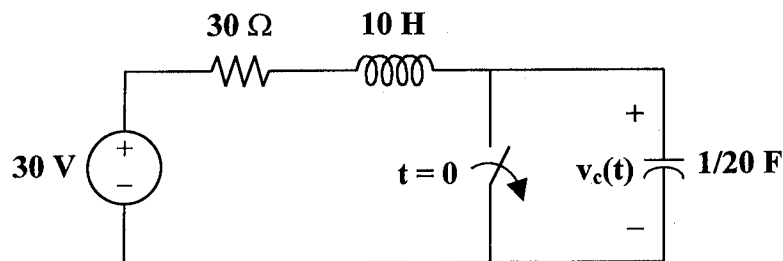


Figure 8.13

This is a second-order circuit with a forced response and a natural response.

Solve for initial conditions.

At  $t = 0$ ,

$$v_c(0^-) = v_c(0^+) = 0 \quad \text{and} \quad i_L(0^-) = i_L(0^+) = \frac{30}{30} = 1 \text{ amp.}$$

Hence,

$$i_c(0^+) = C \frac{dv_c(0^+)}{dt} = 1 \text{ amp}$$


or 
$$\frac{dv_c(0^+)}{dt} = \frac{1}{C} i_c(0^+) = \frac{1}{1/20}(1) = 20 \text{ volts/sec}$$

Solving for final values,

$$i_c(\infty) = 0 \text{ amps} \quad \text{and} \quad v_c(\infty) = 30 \text{ volts}$$
  
 which is also the forced response,

$$v_{c_f} = 30 \text{ volts.}$$

Solving for the natural response,

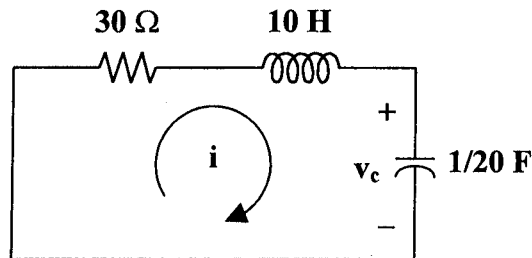

The loop equation is

$$Ri + L \frac{di}{dt} + v_c = 0$$

where  $i = C \frac{dv_c}{dt}$ .

So, we now have,

$$RC \frac{dv_c}{dt} + LC \frac{d^2v_c}{dt^2} + v_c = 0$$

Substituting for the values of R, L, and C

$$\frac{30}{20} \frac{dv_c}{dt} + \frac{10}{20} \frac{d^2v_c}{dt^2} + v_c = 0$$

Simplifying and rearranging the terms,

$$\frac{d^2v_c}{dt^2} + 3 \frac{dv_c}{dt} + 2v_c = 0$$

Substituting a solution  $v_c = Ae^{st}$  yields

$$s^2 Ae^{st} + 3sAe^{st} + 2Ae^{st} = 0$$

$$(s^2 + 3s + 2)Ae^{st} = 0$$

Thus,

$$s^2 + 3s + 2 = (s+1)(s+2) = 0$$

which gives real and unequal roots at  $s_1 = -1$  and  $s_2 = -2$ .

Hence, the natural response is

$$v_{C_n} = Ae^{-t} + Be^{-2t}$$

and the complete response is

$$v_C = v_{C_r} + v_{C_n} = 30 + Ae^{-t} + Be^{-2t}$$

Now, we need to solve for the unknowns, A and B.

$$v_C(0) = 30 + Ae^0 + Be^0 = 0$$

$$A + B = -30 \quad \text{or} \quad B = -A - 30$$

Also,

$$\frac{dv_C(0)}{dt} = 0 + (-A)e^0 + (-2B)e^0 = -A - 2B = 20$$

Now,

$$A + 2B = -20$$

which leads to

$$A + (2)(-A - 30) = -20$$

Hence,

$$-A - 60 = -20 \quad \text{or} \quad A = -40$$


Then,

$$B = -(-40) - 30 = 10$$

Therefore,

$$v_C(t) = \underline{(30 - 40e^{-t} + 10e^{-2t}) \text{ volts } \forall t > 0}$$

**Problem 8.15** Given the circuit shown in Figure 8.14, find  $i_L(t)$  for all  $t > 0$ .

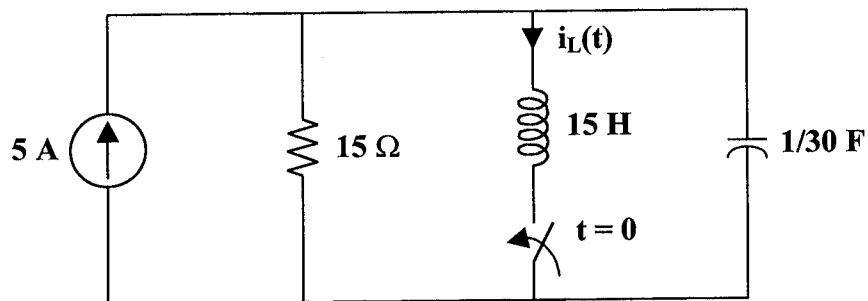

**Figure 8.14**


➤ **Carefully DEFINE the problem.**

Each component is labeled, indicating the value and polarity. The problem is clear.

➤ **PRESENT everything you know about the problem.**

The goal of the problem is to find  $i_L(t)$  for all  $t > 0$ .

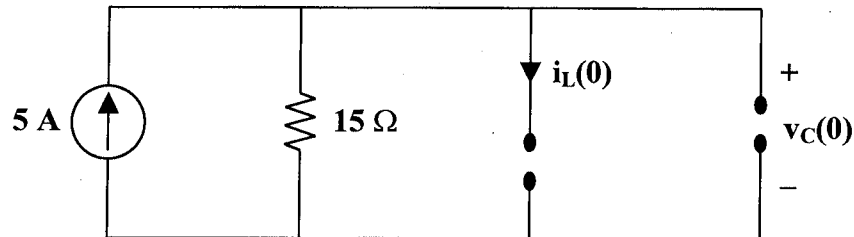
There is a switch in the circuit. So, we will need to look at two different circuits. The first circuit, when the switch is open, is used to find the initial values of the capacitor and inductor. Note that there is a dc source. At dc, a capacitor is an open circuit and an inductor is a short circuit. Thus, we have the following circuit.



Recall that the voltage of a capacitor cannot change instantaneously and the current through an inductor cannot change instantaneously.

$$v_C(0) = v_C(0^-) = v_C(0^+) \quad \text{and} \quad i_L(0) = i_L(0^-) = i_L(0^+)$$

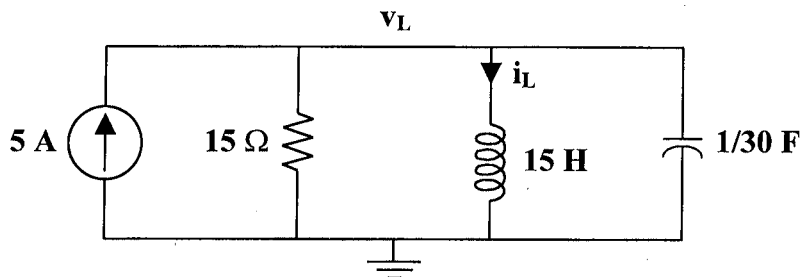The second circuit, after the switch opens is used to find the final solution.




➤ **Establish a set of ALTERNATIVE solutions and determine the one that promises the greatest likelihood of success.**

This is a second-order circuit with a forced response and a natural response. The forced response is the response due to the current source at steady state. The natural response is the response of the parallel RLC circuit without the current source.

For simple resistive circuits such as the one used to find the initial values and final values, we will use observation and Ohm's law. For the parallel RLC circuit, use nodal analysis. There will be only one equation with this technique versus three equations with mesh analysis.

➤ **ATTEMPT a problem solution.**

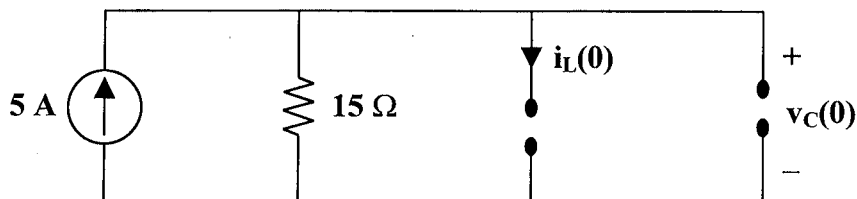Solve for initial conditions using the circuit below.





At  $t = 0$ ,

$$v_C(0^-) = v_C(0^+) = (5)(15) = 75 \text{ volts}$$


$$i_L(0^-) = i_L(0^+) = 0$$

$$v_L(0^+) = v_C(0^+) = 75 \text{ volts}$$

Thus,


$$\frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{75}{15} = 5 \text{ amp/sec}$$

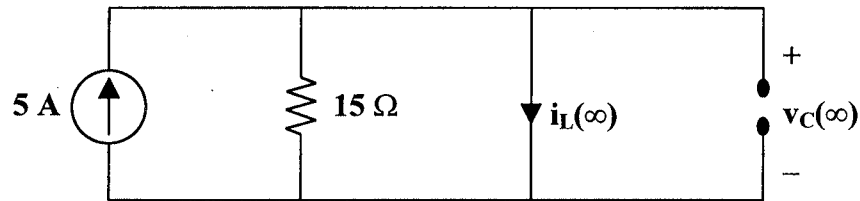Solving for final values, the forced response,



$$i_L(\infty) = i_{L_f} = 5 \text{ amps}$$

Now, solve for the natural response.

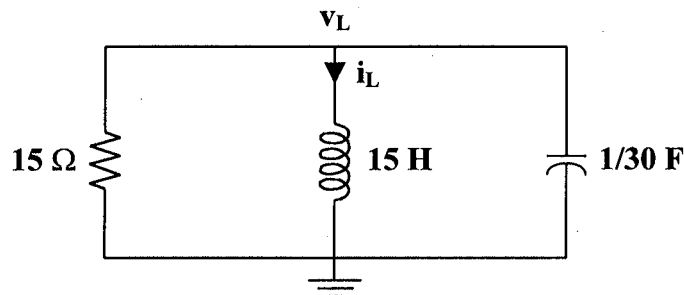

Writing the node equation,

$$\frac{v_L - 0}{15} + i_L + \frac{1}{30} \frac{d(v_L - 0)}{dt} = 0$$

where  $v_L = 15 \frac{di_L}{dt}$

So,

$$\frac{15}{15} \frac{di_L}{dt} + i_L + \frac{15}{30} \frac{d^2 i_L}{dt^2} = 0$$

Simplifying and rearranging the terms,

$$\frac{d^2 i_L}{dt^2} + 2 \frac{di_L}{dt} + 2i_L = 0$$

Substituting the solution  $i_L = Ae^{st}$  yields

$$s^2 Ae^{st} + 2sAe^{st} + 2Ae^{st} = 0$$
$$(s^2 + 2s + 2)Ae^{st} = 0$$

Thus,

$$(s^2 + 2s + 2) = (s + 1 + j)(s + 1 - j) = 0$$

which gives complex roots at  $s_{1,2} = -1 \mp j$ .

Hence,

$$i_{L_n} = Ae^{-(1+j)t} + Be^{-(1-j)t}$$

This means that the complete response is

$$i_L = i_{L_r} + i_{L_n} = 5 + Ae^{-(1+j)t} + Be^{-(1-j)t}$$

At  $t = 0$ ,

$$i_L(0) = 5 + Ae^0 + Be^0 = 5 + A + B = 0$$
$$A + B = -5 \quad \text{or} \quad B = -A - 5$$

Also,

$$\frac{di_L(0)}{dt} = 0 - (1+j)A - (1-j)B = 5$$
$$-A - jA - B + jB = 5$$
$$-A - jA - (-A - 5) + j(-A - 5) = 5$$
$$-2jA + 5 - j5 = 5$$
$$A = \frac{5 - 5 + j5}{-2j} = \frac{-5}{2}$$

Then,

$$B = -A - 5 = \frac{5}{2} - 5 = \frac{-5}{2}$$

Therefore,

$$i_L = 5 + (-5/2)e^{-(1+j)t} + (-5/2)e^{-(1-j)t}$$
$$i_L(t) = 5 - 5e^{-t} \left[ \frac{e^{-jt} + e^{jt}}{2} \right]$$
$$i_L(t) = [5 - 5e^{-t} \cos(t)] \text{ amps } \forall t > 0$$

➤ **EVALUATE the solution and check for accuracy.**

Check to see if the answer satisfies the initial conditions.

$$i_L(0) = 5 - 5e^{-0} \cos(0) = 5 - 5 = 0 \text{ amps}$$

This matches the initial condition that

$$i_L(0^-) = i_L(0^+) = 0 \text{ amps}$$

$$\frac{di_L(t)}{dt} = 0 + 5e^{-t} \sin(t) + 5e^{-t} \cos(t)$$

$$\frac{di_L(0)}{dt} = 5e^{-0} \sin(0) + 5e^{-0} \cos(0) = 0 + 5 = 5 \text{ amps/sec}$$

This matches the initial condition that

$$\frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{75}{15} = 5 \text{ amp/sec}$$

- **Has the problem been solved SATISFACTORILY? If so, present the solution; if not, then return to "ALTERNATIVE solutions" and continue through the process again.**  
This problem has been solved satisfactorily.

$$i_L(t) = \underline{[5 - 5e^{-t} \cos(t)] \text{ amps } \forall t > 0}$$

## SECOND-ORDER OP AMP CIRCUITS

**Problem 8.16** Given the circuit shown in Figure 8.15, find  $v_o$  in terms of  $v_i$ .

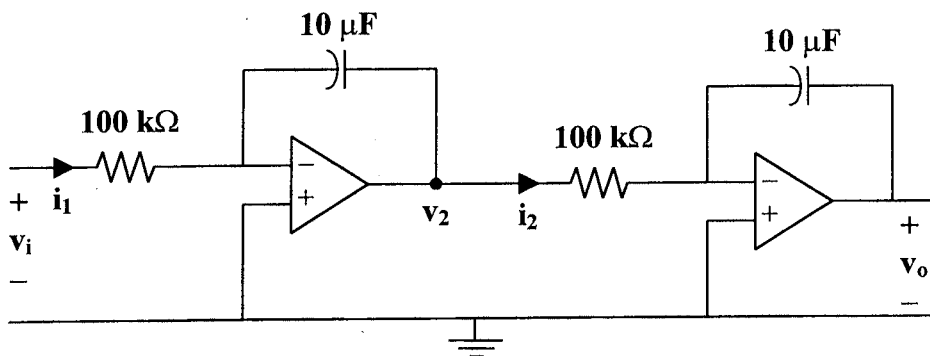


Figure 8.15

Clearly,

$$i_1 = \frac{v_i}{R_1}$$

and

$$v_2 = \frac{-1}{C_1} \int \frac{v_i}{R_1} dt = \frac{-1}{R_1 C_1} \int v_i dt$$

where  $R_1 C_1 = (10^5)(10^{-5}) = 1$ .

Hence,

$$v_2 = - \int v_i dt$$

Also,

$$i_2 = \frac{v_2}{R_2}$$

and

$$v_o = \frac{-1}{C_2} \int \frac{v_2}{R_2} dt = \frac{-1}{R_2 C_2} \int v_2 dt$$

where  $R_2 C_2 = (10^5)(10^{-5}) = 1$ .

So,

$$v_o = - \int v_2 dt$$

Therefore,

$$v_o = \underline{\int \int v_i dt^2}$$

Circuits like these have many applications, especially in analog computers.