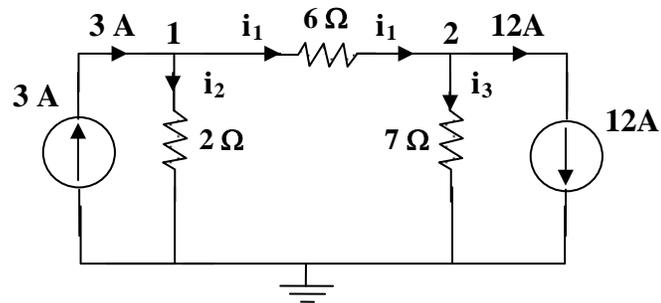


CHAPTER 3**P.P.3.1**

At node 1,

$$-3 + i_1 + i_2 = 0 \text{ or } \frac{v_1 - v_2}{6} + \frac{v_1 - 0}{2} = 3$$

$$\text{or } 4v_1 - v_2 = 18 \quad (1)$$


At node 2,

$$-i_1 + i_3 + 12 = 0 \text{ or } i_1 = 12 + i_3 \text{ or } \frac{v_1 - v_2}{6} = 12 + \frac{v_2 - 0}{7}$$

$$\text{or } 7v_1 - 13v_2 = 504 \quad (2)$$

Solving (1) and (2) gives

$$v_1 = -6 \text{ V}, v_2 = -42 \text{ V}$$

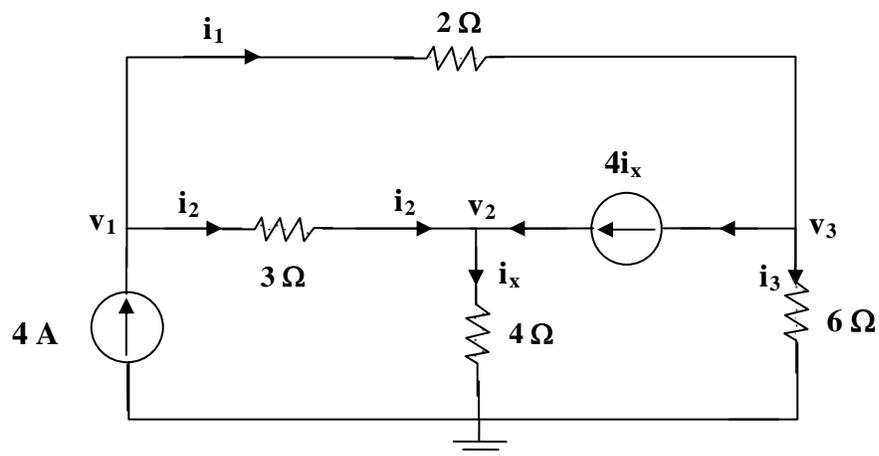P.P.3.2

At node 1,

$$-4 + i_1 + i_2 = 0 = -4 + \frac{v_1 - v_3}{2} + \frac{v_1 - v_2}{3}$$

$$\text{or } 5v_1 - 2v_2 - 3v_3 = 24 \quad (1)$$

At node 2,

$$-i_2 + i_x - 4i_x = 0 = -i_2 - 3i_x = 0 \text{ where } i_x = [(v_2 - 0)/4] \text{ or}$$

$$\frac{v_1 - v_2}{3} + 3\frac{v_2}{4} = 0 \text{ which leads to } 4v_1 + 5v_2 = 0 \quad (2)$$

At node 3,



$$-i_1 + i_3 + 4i_x = 0 = \frac{v_3 - v_1}{2} + \frac{v_3 - 0}{6} + 4\frac{v_2}{4}$$

$$\text{or } -3v_1 + 6v_2 + 4v_3 = 0 \quad (3)$$

Solving (1) to (3) gives

$$v_1 = \mathbf{32 \text{ V}}, v_2 = \mathbf{-25.6 \text{ V}}, v_3 = \mathbf{62.4 \text{ V}}$$

P.P.3.3

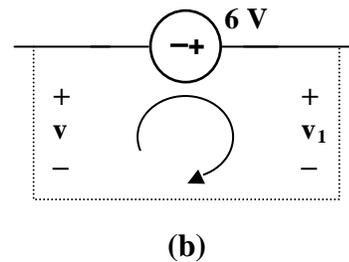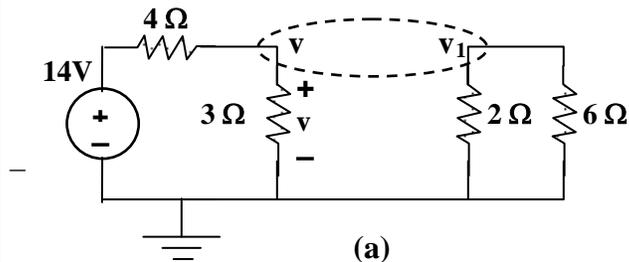

At the supernode in Fig. (a),

$$\frac{14 - v}{4} = \frac{v}{3} + \frac{v_1}{2} + \frac{v_1}{6}$$

$$\text{or } 42 = 7v + 8v_1 \quad (1)$$

Applying KVL to the loop in Fig. (b),

$$-v - 6 + v_1 = 0 \longrightarrow v_1 = v + 6 \quad (2)$$


Solving (1) and (2),

$$v = -400 \text{ mV}$$


$$v_1 = v + 6 = 5.6, i_1 = \frac{v_1}{2} = 2.8$$

$$i_1 = 2.8 \text{ A}$$

P.P.3.4

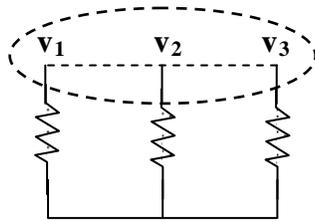

(a)

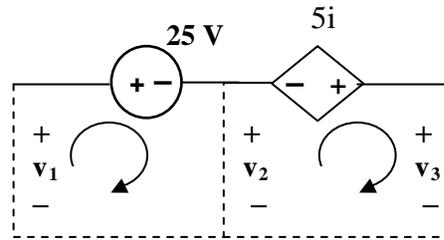

(b)

From Fig. (a),

$$\frac{v_1}{2} + \frac{v_2}{4} + \frac{v_3}{3} = 0 \longrightarrow 6v_1 + 3v_2 + 4v_3 = 0 \quad (1)$$

From Fig. (b),

$$-v_1 + 25 + v_2 = 0 \longrightarrow v_1 = v_2 + 25 \quad (2)$$

$$-v_2 - 5i + v_3 = 0 \longrightarrow v_3 = v_2 + 2.5v_1 \quad (3)$$

Solving (1) to (3), we obtain

$$v_1 = 7.608 \text{ V}, v_2 = -17.39 \text{ V}, v_3 = 1.6305 \text{ V}$$

P.P.3.5 We apply KVL to the two loops and obtain

$$-45 + 2i_1 + 12(i_1 - i_2) + 4i_1 = 0 \text{ or}$$

$$-45 + 18i_1 - 12i_2 = 0 \text{ which leads to } 3i_1 - 2i_2 = 7.5 \quad (1)$$

$$12(i_2 - i_1) + 9i_2 + 30 + 3i_2 = 0 \text{ or}$$

$$30 + 24i_2 - 12i_1 = 0 \text{ which leads to } -3i_1 + 6i_2 = -7.5 \quad (2)$$

From (1) and (2) we get

$$i_1 = 2.5 \text{ A}, i_2 = 0 \text{ A}$$

P.P.3.6 For mesh 1,

$$-16 + 6i_1 - 2i_2 - 4i_3 = 0 \longrightarrow 3i_1 - i_2 - 2i_3 = 8 \quad (1)$$

For mesh 2,

$$10i_2 - 2i_1 - 8i_3 - 10i_0 = 0 = -i_1 + 5i_2 - 9i_3 \quad (2)$$

But $i_0 = i_3$,

$$18i_3 - 4i_1 - 8i_2 = 0 \longrightarrow -2i_1 - 4i_2 + 9i_3 = 0 \quad (3)$$

From (1) to (3),

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 5 & -9 \\ -2 & -4 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 8 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 3 & -1 & -2 \\ -1 & 5 & -9 \\ -2 & -4 & 9 \end{vmatrix} = 135 - 8 - 18 - 20 - 108 - 9 = -28$$

$$\Delta_1 = \begin{vmatrix} 8 & -1 & -2 \\ 0 & 5 & -9 \\ 0 & -4 & 9 \end{vmatrix} = 360 - 288 = 72$$



$$\Delta_2 = \begin{vmatrix} 3 & 8 & -2 \\ -1 & 0 & -9 \\ -2 & 0 & 9 \end{vmatrix} = 144 + 72 = 216$$

$$\Delta_3 = \begin{vmatrix} 3 & -1 & 8 \\ -1 & 5 & 0 \\ 3 & -1 & 8 \\ -1 & 5 & 0 \end{vmatrix} = 32 + 80 = 112$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{72}{-28} = -2.571, \quad i_2 = \frac{\Delta_2}{\Delta} = \frac{216}{-28} = -7.714, \quad i_3 = \frac{\Delta_3}{\Delta} = \frac{112}{-28} = -4 \text{ A}$$

$$I_o = i_3 = -4 \text{ A}$$

P.P.3.7

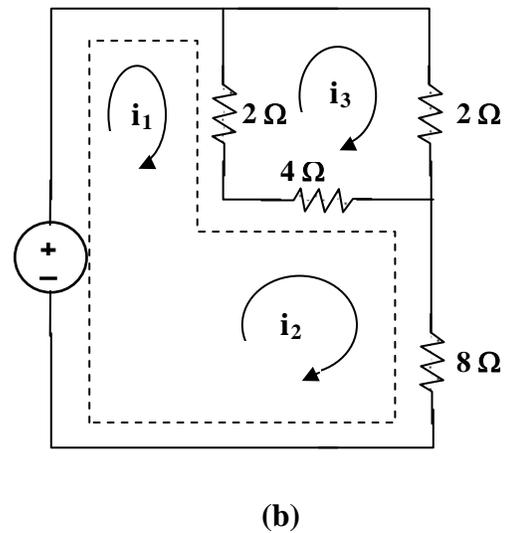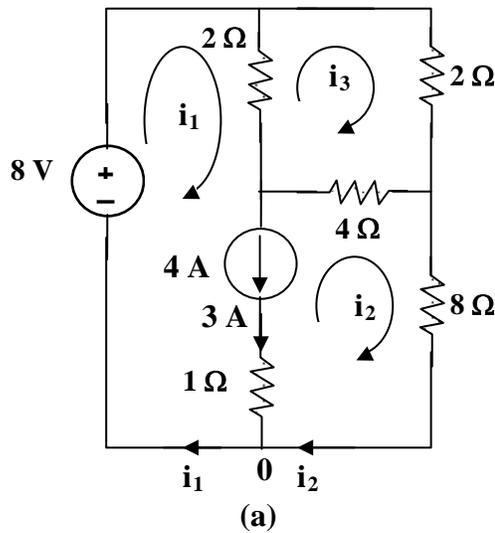

For the supermesh,

$$-8 + 2i_1 - 2i_3 + 12i_2 - 4i_3 = 0 \text{ or } i_1 + 6i_2 - 3i_3 = 4 \quad (1)$$

For mesh 3,

$$8i_3 - 2i_1 - 4i_2 = 0 \text{ or } -i_1 - 2i_2 + 4i_3 = 0 \quad (2)$$

At node 0 in Fig. (a),

$$i_1 = 4 + i_2 \longrightarrow i_1 - i_2 = 4$$

Solving (1) to (3) yields

$$i_1 = 4.632 \text{ A}, \quad i_2 = 631.6 \text{ mA}, \quad i_3 = 1.4736 \text{ A}$$

P.P.3.8 $G_{11} = 1/(1) + 1/(20) + 1/(5) = 1.25$, $G_{12} = -1/(5) = -0.2$,
 $G_{33} = 1/(4) + 1 = 1.25$, $G_{44} = 1/(1) + 1/(4) = 1.25$,
 $G_{12} = -1/(5) = -0.2$, $G_{13} = -1$, $G_{14} = 0$,
 $G_{21} = -0.2$, $G_{23} = 0 = G_{26}$,
 $G_{31} = -1$, $G_{32} = 0$, $G_{34} = -1/4 = -0.25$,
 $G_{41} = 0$, $G_{42} = 0$, $G_{43} = 0.25$,
 $i_1 = 0$, $i_2 = 3+2 = 5$, $i_3 = -3$, $i_4 = 2$.

Hence,

$$\begin{bmatrix} 1.25 & -0.2 & -1 & 0 \\ -0.2 & 0.2 & 0 & 0 \\ -1 & 0 & 1.25 & -0.25 \\ 0 & 0 & -0.25 & 1.25 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 5 \\ -3 \\ 2 \end{bmatrix}$$


P.P.3.9 $R_{11} = 50 + 20 + 80 = 150$, $R_{22} = 20 + 30 + 15 = 65$,
 $R_{33} = 30 + 20 = 50$, $R_{44} = 15 + 80 = 95$,
 $R_{55} = 20 + 60 = 80$, $R_{12} = -40$, $R_{13} = 0$, $R_{14} = -80$,
 $R_{15} = 0$, $R_{21} = -40$, $R_{23} = -30$, $R_{24} = -15$, $R_{25} = 0$,
 $R_{31} = 0$, $R_{32} = -30$, $R_{34} = 0$, $R_{35} = -20$,
 $R_{41} = -80$, $R_{42} = -15$, $R_{43} = 0$, $R_{45} = 0$,
 $R_{51} = 0$, $R_{52} = 0$, $R_{53} = -20$, $R_{54} = 0$,
 $v_1 = 30$, $v_2 = 0$, $v_3 = -12$, $v_4 = 20$, $v_5 = -20$

Hence the mesh-current equations are

$$\begin{bmatrix} 150 & -40 & 0 & -80 & 0 \\ -40 & 65 & -30 & -15 & 0 \\ 0 & -30 & 50 & 0 & -20 \\ -80 & -15 & 0 & 95 & 0 \\ 0 & 0 & -20 & 0 & 80 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 30 \\ 0 \\ -12 \\ 20 \\ -20 \end{bmatrix}$$


P.P.3.10 The schematic is shown below. It is saved and simulated by selecting Analysis/Simulate. The results are shown on the viewpoints:
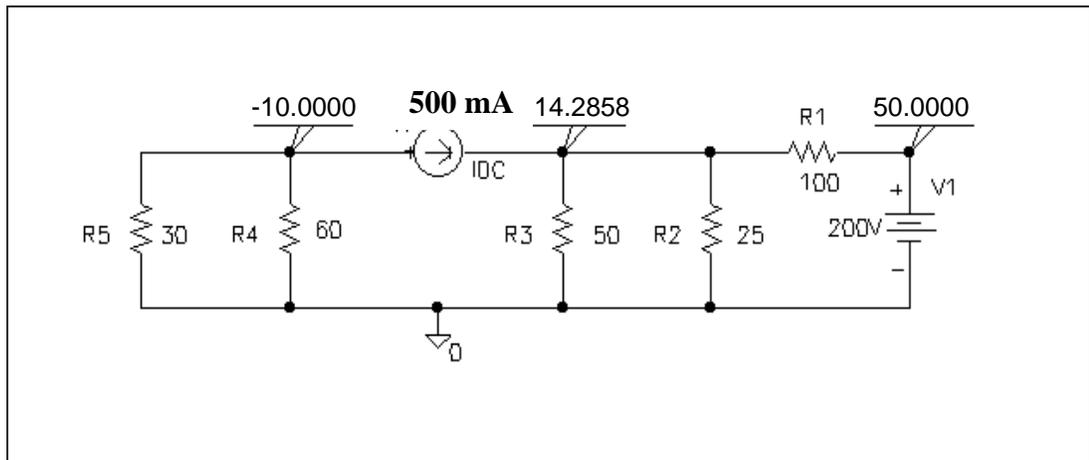
$$v_1 = -10 \text{ V}, v_2 = 14.286 \text{ V}, v_3 = 50 \text{ V}$$



P.P.3.11 The schematic is shown below. After saving it, it is simulated by choosing Analysis/Simulate. The results are shown on the IPROBES.
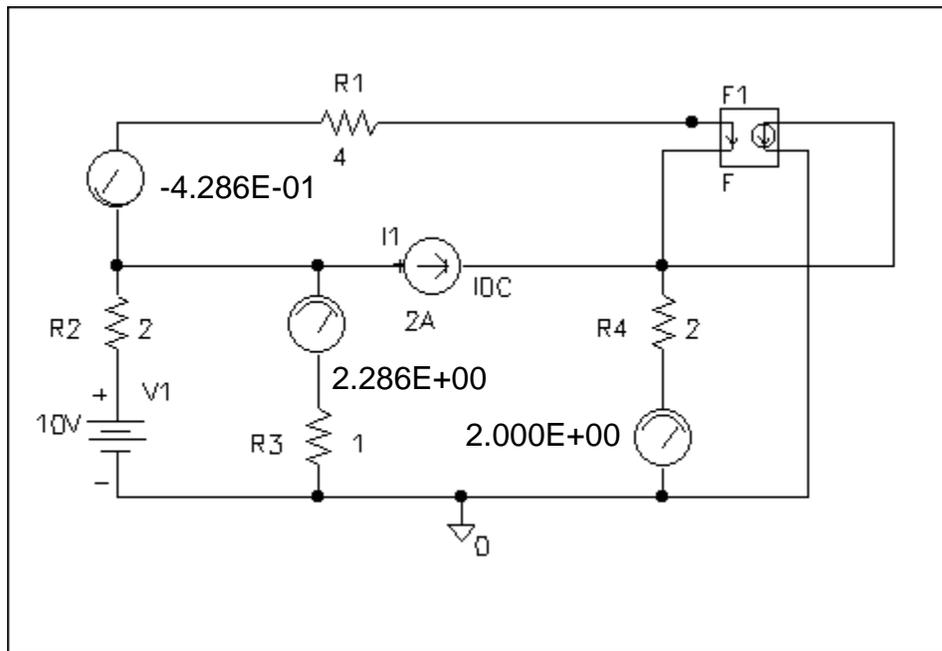
$$i_1 = -428.6 \text{ mA}, i_2 = 2.286 \text{ A}, i_3 = 2 \text{ A}$$



P.P.3.12 For the input loop,

$$-5 + 10 \times 10^3 I_B + V_{BE} + V_0 = 0 \quad (1)$$

For the outer loop,

$$-V_0 - V_{CE} - 500 I_0 + 12 = 0 \quad (2)$$

But $V_0 = 200 I_E \quad (3)$

Also $I_C = \beta I_B = 100 I_B, \alpha = \beta / (1 + \beta) = 100 / (101)$

$$I_C = \alpha I_E \longrightarrow I_E = I_C / (\alpha) = \beta I_B / (\alpha)$$

$$I_E = 100 (101 / (100)) I_B = 101 I_B \quad (4)$$

From (1), (3) and (4),

$$10,000 I_B + 200(101) I_B = 5 - V_{BE}$$

$$I_B = \frac{5 - 0.7}{10,000 + 20,000} = 142.38 \mu\text{A}$$


$$V_0 = 200 I_E = 20,000 I_B = \mathbf{2.876 \text{ V}}$$

From (2),

$$V_{CE} = 12 - V_0 - 500 I_C = 9.124 - 500 \times 100 \times 142.38 \times 10^{-6}$$

$$V_{CE} = \mathbf{1.984 \text{ V}} \text{ \{often, this is rounded to 2.0 volts\}}$$

P.P.3.13

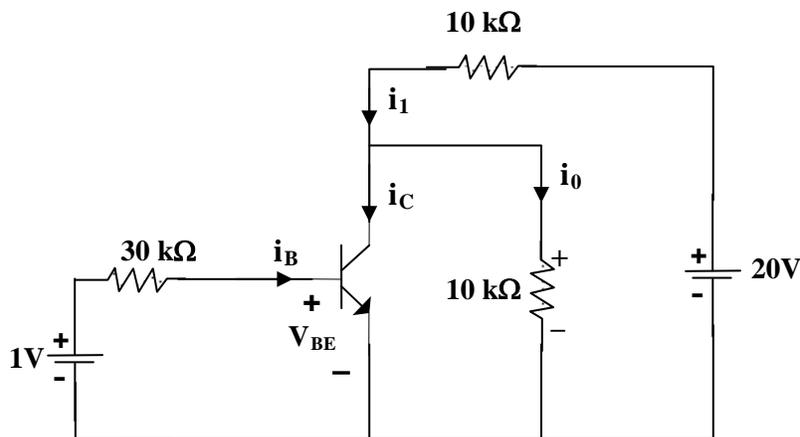

$$i_B = \frac{1-0.7}{30k} = 10\mu\text{A}, \quad i_C = \beta i_B = 0.8 \text{ mA}$$

$$i_1 = i_C + i_0 \quad (1)$$

Also, $-10ki_0 - 10ki_1 + 20 = 0 \longrightarrow i_1 = 2 \text{ mA} - i_0 \quad (2)$

Equating (1) and (2),

$$2 \text{ mA} - i_0 = 0.8 \text{ mA} + i_0 \longrightarrow i_0 = \mathbf{600 \mu\text{A}}$$

$$v_0 = 20 ki_0 = 20 \times 10^3 \times 600 \times 10^{-6} = \mathbf{12 \text{ V}}$$