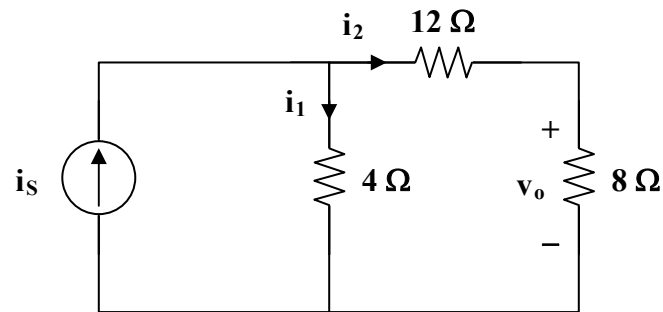



CHAPTER 4**P.P.4.1**

By current division, $i_2 = \frac{4}{4+12+8}i_s = \frac{1}{6}i_s$

$$v_o = 8i_2 = \frac{4}{3}i_s$$

When $i_s = 30$ A, $v_o = \frac{4}{3}(30) = \mathbf{40$ V

When $i_s = 45$ A, $v_o = \frac{4}{3}(45) = \mathbf{60$ V

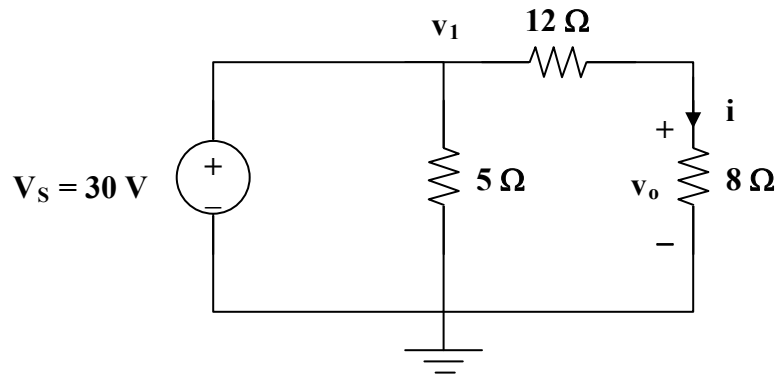
P.P.4.2

Let $v_o = 1$ volt. Then $i = \frac{1}{8}$ and $v_1 = \frac{1}{8}(12 + 8) = 2.5$


giving $v_s = 2.5$ V.

If $v_s = 40$ V, then $v_o = (40/2.5)(1) = \mathbf{16$ V

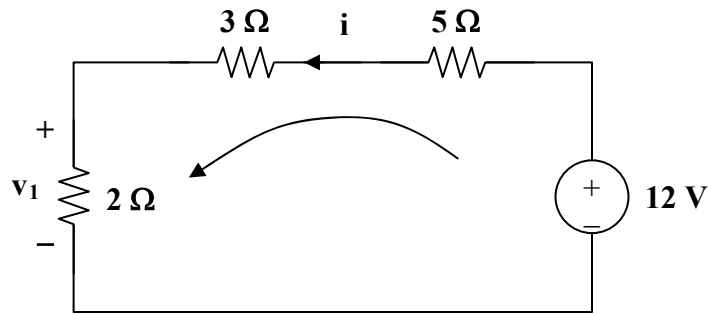P.P.4.3 Let $v_0 = v_1 + v_2$, where v_1 and v_2 are contributions to the 12-V and 5-A sources respectively.



(a)

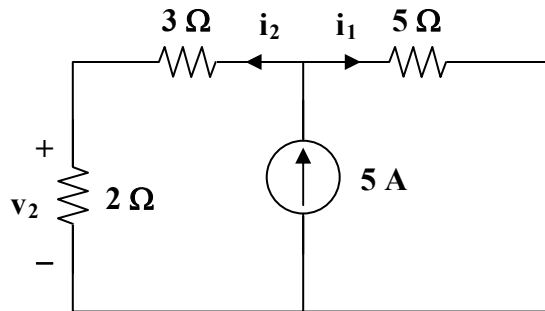

(b)

To get v_1 , consider the circuit in Fig. (a).

$$(2 + 3 + 5)i - 12 = 0 \text{ or } i = 12/(10) = 1.2 \text{ A}$$

$$v_1 = 2i = 2.4 \text{ V}$$

To get v_2 , consider the circuit in Fig. (b).


Since the resistors are equal ($5 = 2 + 3$) then the current divides equally and

$$i_1 = i_2 = 5/2 = 2.5 \text{ and } v_2 = 2i_2 = 5 \text{ V}$$

Thus,

$$v = v_1 + v_2 = 2.4 + 5 = 7.4 \text{ V}$$

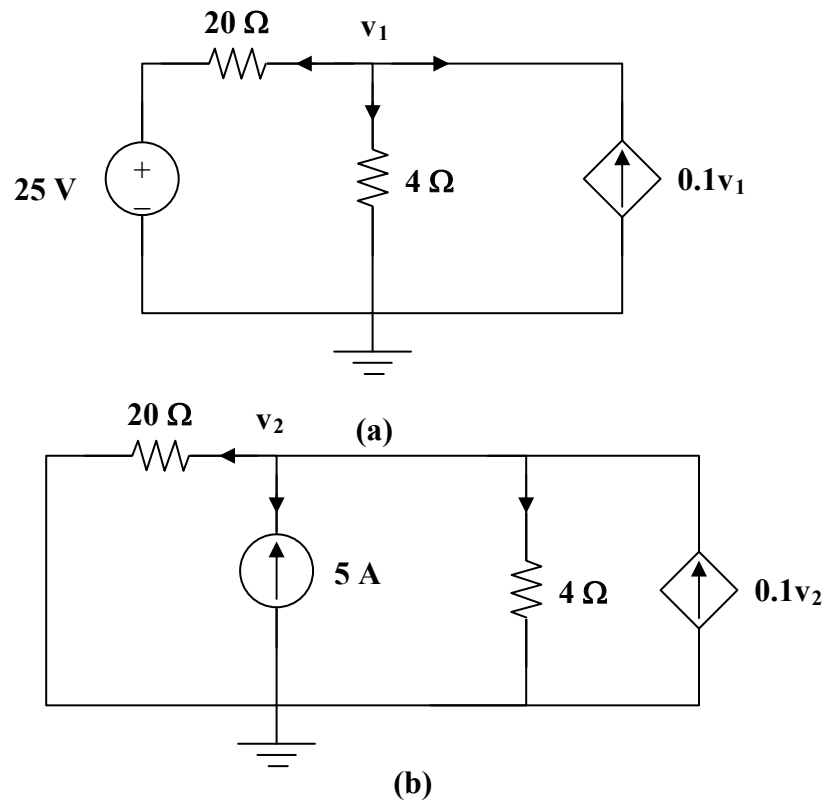P.P.4.4 Let $v_x = v_1 + v_2$, where v_1 and v_2 are due to the 25-V and 5-A sources respectively.



To obtain v_1 , consider Fig. (a).

$$-0.1v_1 + \frac{v_1 - 25}{20} + \frac{v_1 - 0}{4} = 0 \quad \text{or} \quad 0.2v_1 = 25/20 = 1.25 \quad \text{or} \quad v_1 = 6.25 \text{ V}$$


For v_2 , consider Fig. (b).

$$-5 - 0.1v_2 + \frac{v_2 - 0}{20} + \frac{v_2 - 0}{4} = 0 \quad \text{or} \quad 0.2v_2 = 5 \quad \text{or} \quad v_2 = 25 \text{ V}$$

$$v_x = v_1 + v_2 = \mathbf{31.25 \text{ V}}$$

P.P.4.5 Let $i = i_1 + i_2 + i_3$

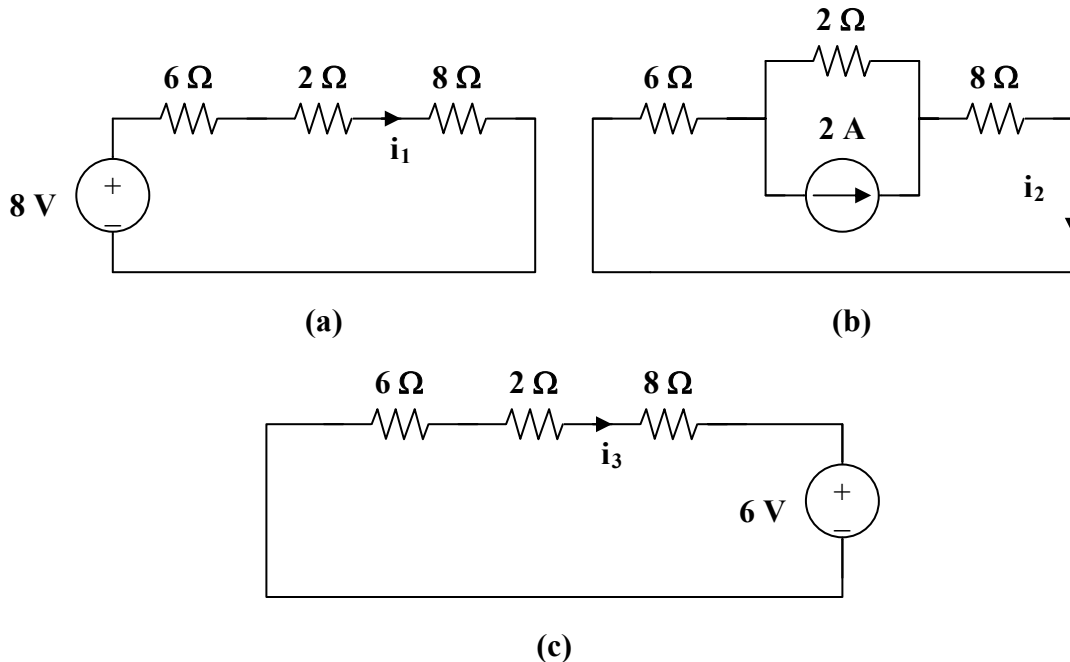where i_1 , i_2 , and i_3 are contributions due to the 8-V, 2-A, and 6-V sources respectively.



For i_1 , consider Fig. (a), $i_1 = \frac{8}{6+2+8} = 0.5 \text{ A}$


For i_2 , consider Fig. (b). By current division, $i_2 = \frac{2}{2+14}(2) = 0.25$

For i_3 , consider Fig. (c), $i_3 = \frac{-6}{16} = -0.375 \text{ A}$


Thus, $i = i_1 + i_2 + i_3 = 0.5 + 0.25 - 0.375 = \mathbf{375 \text{ mA}}$

P.P.4.6 Combining the 6- Ω and 3- Ω resistors in parallel gives $6 \parallel 3 = \frac{6 \times 3}{9} = 2 \Omega$.

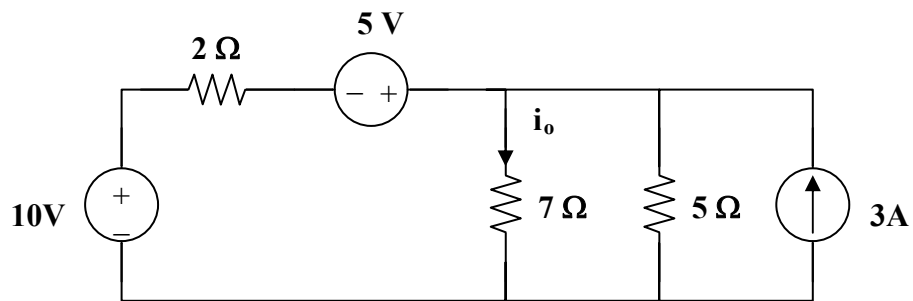
Adding the 1- Ω and 4- Ω resistors in series gives $1 + 4 = 5 \Omega$. Transforming the left current source in parallel with the 2- Ω resistor gives the equivalent circuit as shown in Fig. (a).



(a)

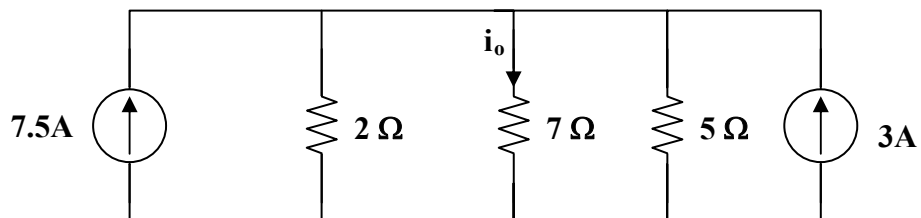

(b)

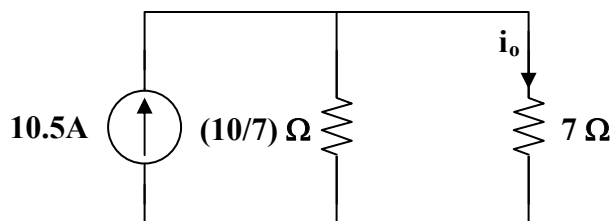


(c)

Adding the 10-V and 5-V voltage sources gives a 15-V voltage source. Transforming the 15-V voltage source in series with the 2-Ω resistor gives the equivalent circuit in Fig. (b). Combining the two current sources and the 2-Ω and 5-Ω resistors leads to the circuit in Fig. (c). Using circuit division,


$$i_o = \frac{\frac{10}{7}}{\frac{10}{7} + 7} (10.5) = 1.78 \text{ A}$$

P.P.4.7 We transform the dependent voltage source as shown in Fig. (a). We combine the two current sources in Fig. (a) to obtain Fig. (b). By the current division principle,
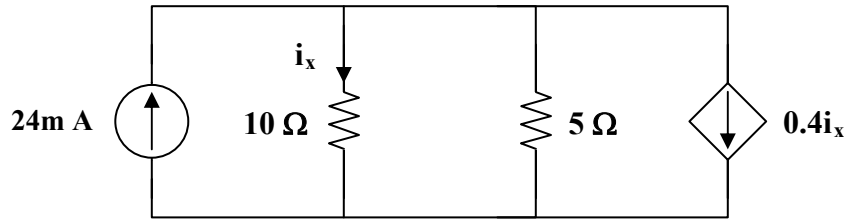
$$i_x = \frac{5}{15} (0.024 - 0.4i_x) \longrightarrow i_x = 7.059 \text{ mA}$$




(a)

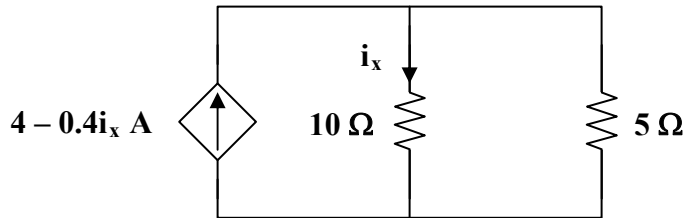


(b)

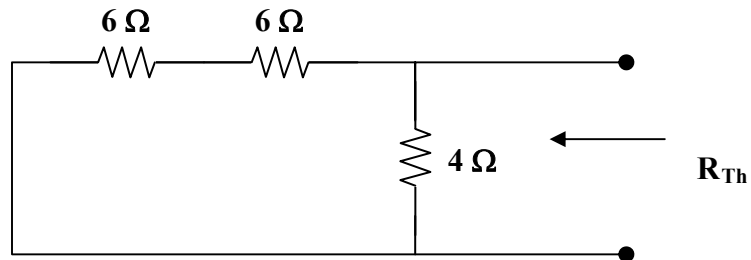P.P.4.8 To find R_{Th} , consider the circuit in Fig. (a).




(a)

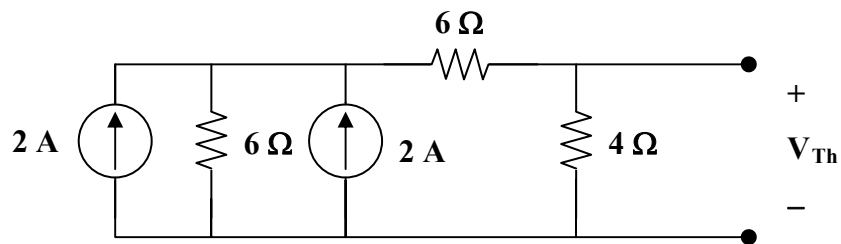

(b)

$$R_{Th} = (6 + 6) \parallel 4 = \frac{12 \times 4}{18} = 3 \Omega$$

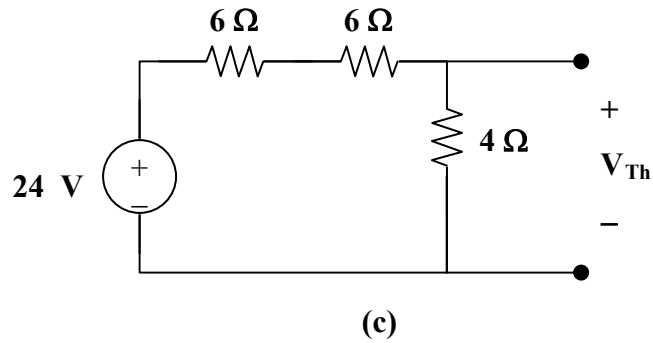To find V_{Th} , we use source transformations as shown in Fig. (b) and (c).





Using current division in Fig. (c),

$$V_{Th} = \frac{4}{4+12}(24) = 6 \text{ V}$$

$$i = \frac{V_{Th}}{R_{Th} + 1} = \frac{6}{3+1} = 1.5 \text{ A}$$

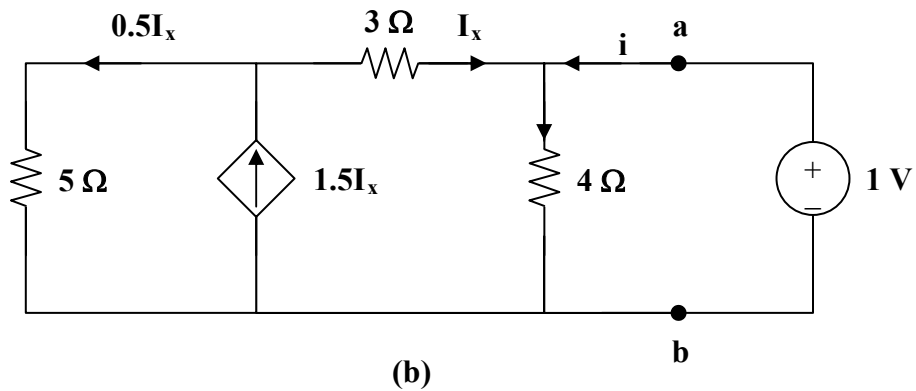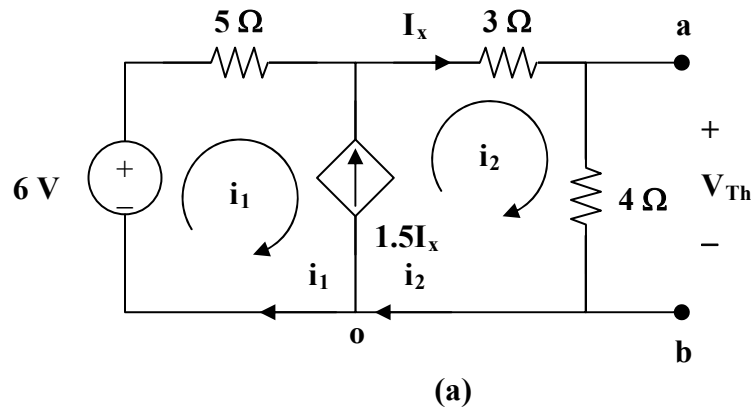P.P.4.9 To find V_{Th} , consider the circuit in Fig. (a).



$$I_x = i_2$$

$$i_2 - i_1 = 1.5I_x = 1.5i_2 \longrightarrow i_2 = -2i_1 \quad (1)$$

$$\text{For the supermesh, } -6 + 5i_1 + 7i_2 = 0 \quad (2)$$

From (1) and (2), $i_2 = 4/3\text{A}$

$$V_{Th} = 4i_2 = \mathbf{5.333V}$$


To find R_{Th} , consider the circuit in Fig. (b). Applying KVL around the outer loop,

$$5(0.5I_x) - 1 - 3I_x = 0 \longrightarrow I_x = -2$$


$$i = \frac{1}{4} - I_x = 2.25$$

$$R_{Th} = \frac{1}{i} = \frac{1}{2.25} = \mathbf{444.4 \text{ m}\Omega}$$

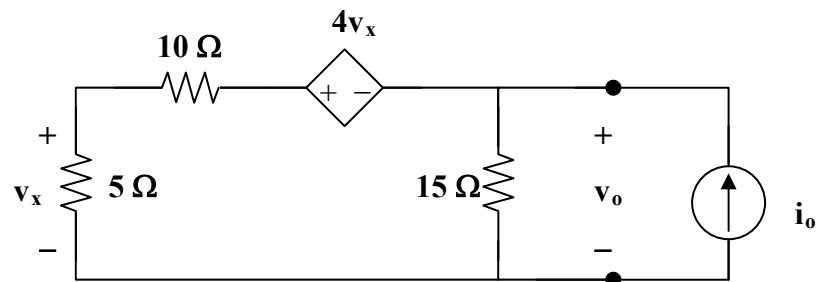P.P.4.10 Since there are no independent sources, $V_{Th} = \mathbf{0}$



(a)

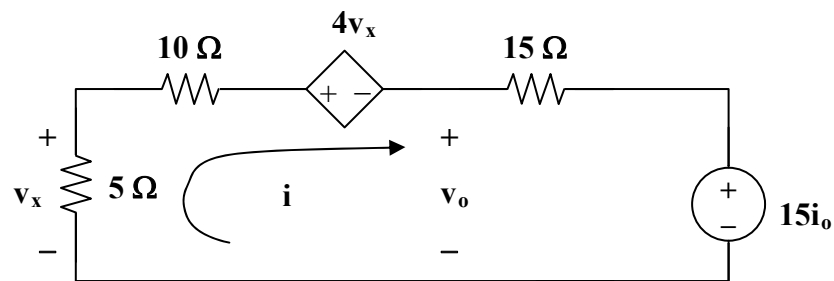

(b)


To find R_{Th} , consider Fig.(a). Using source transformation, the circuit is transformed to that in Fig. (b). Applying KVL, .

But $v_x = -5i$. Hence, $30i - 20i + 15i_o = 0 \longrightarrow 10i = -15i_o$


$v_o = (15i + 15i_o) = 15(-1.5i_o + i_o) = -7.5i_o$

$R_{Th} = v_o/i_o = -7.5\Omega$ It needs to be noted that this negative resistance indicates we must have an active source (a dependent source).

P.P.4.11

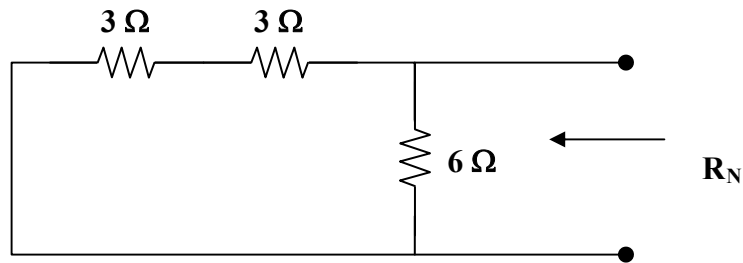


(a)

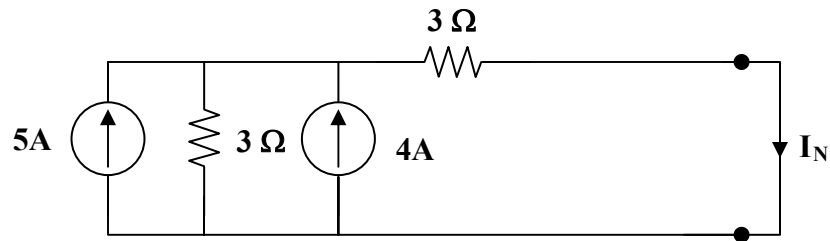


(b)

From Fig. (a), $R_N = (3 + 3) \parallel 6 = 3\Omega$

From Fig. (b), $I_N = \frac{1}{2}(5 + 4) = 4.5A$

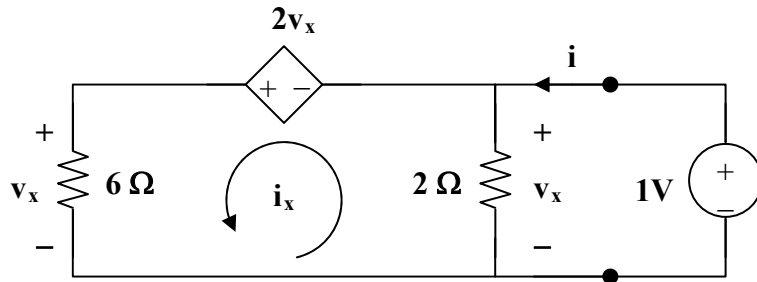P.P.4.12

(a)

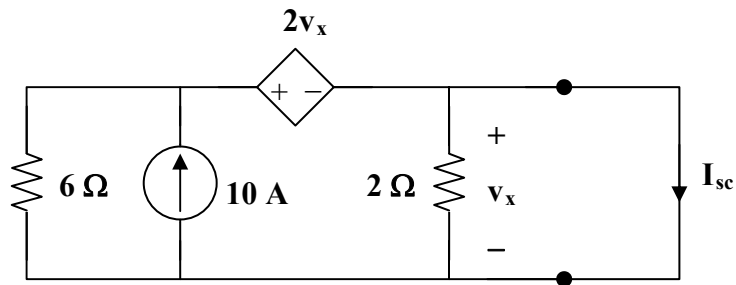

(b)

To get R_N consider the circuit in Fig. (a). Applying KVL, $6i_x - 2v_x - 1 = 0$


But $v_x = 1$, $6i_x = 3 \longrightarrow i_x = 0.5$

$$i = i_x + \frac{v_x}{2} = 0.5 + 0.5 = 1$$


$$R_N = R_{Th} = \frac{1}{i} = 1\Omega$$

To find I_N , consider the circuit in Fig. (b). Because the 2Ω resistor is shorted, $v_x = 0$ and the dependent source is inactive. Hence, $I_N = i_{sc} = 10A$.

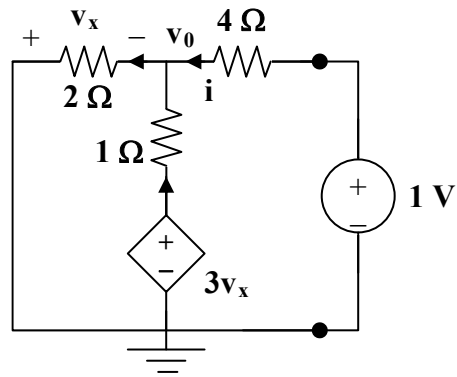P.P.4.13 We first need to find R_{Th} and V_{Th} . To find R_{Th} , we consider the circuit in Fig. (a).



(a)

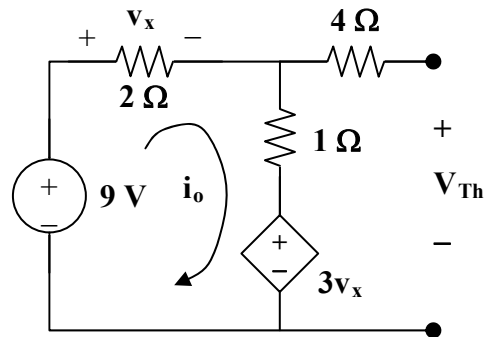

(b)

Applying KCL at the top node gives

$$\frac{1 - v_o}{4} + \frac{3v_x - v_o}{1} = \frac{v_o}{2}$$

But $v_x = -v_o$. Hence

$$\frac{1 - v_o}{4} - 4v_o = \frac{v_o}{2} \longrightarrow v_o = 1/(19)$$

$$i = \frac{1 - v_o}{4} = \frac{1 - \frac{1}{19}}{4} = \frac{9}{38}$$

$$R_{Th} = 1/i = 38/(9) = 4.222\Omega$$

To find V_{Th} , consider the circuit in Fig. (b),

$$-9 + 2i_o + i_o + 3v_x = 0$$

But $v_x = 2i_o$. Hence,

$$9 = 3i_o + 6i_o = 9i_o \longrightarrow i_o = 1A$$


$$V_{Th} = 9 - 2i_o = 7V$$

$$R_L = R_{Th} = 4.222\Omega$$


$$P_{max} = \frac{V_{Th}^2}{4R_L} = \frac{49}{4(4.222)} = 2.901W$$

P.P.4.14
find V_{Th} and R_{th} .

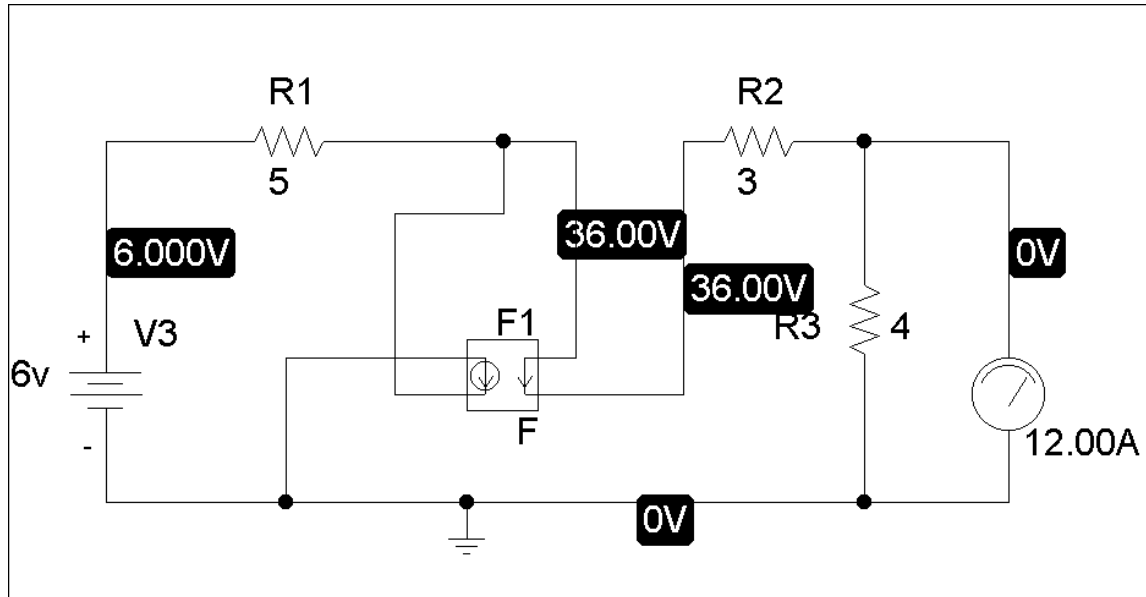We will use PSpice to find V_{oc} and I_{sc} which then can be used to




Clearly $I_{sc} = 12\text{ A}$

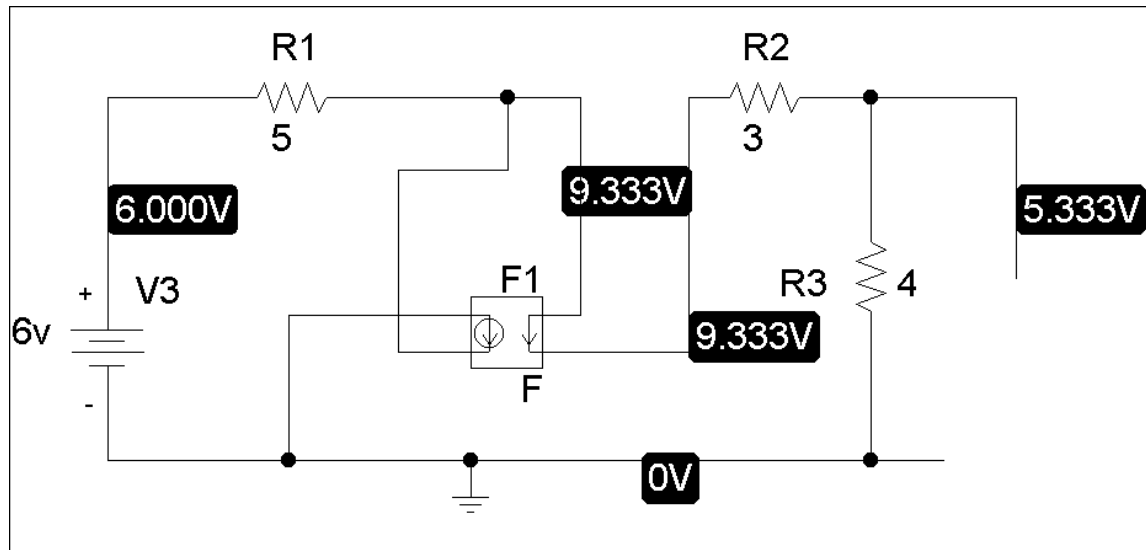


Clearly $V_{Th} = I_{oc} = 5.333\text{ volts}$. $R_{Th} = V_{oc}/I_{sc} = 5.333/12 = 444.4\text{ m}\Omega$.

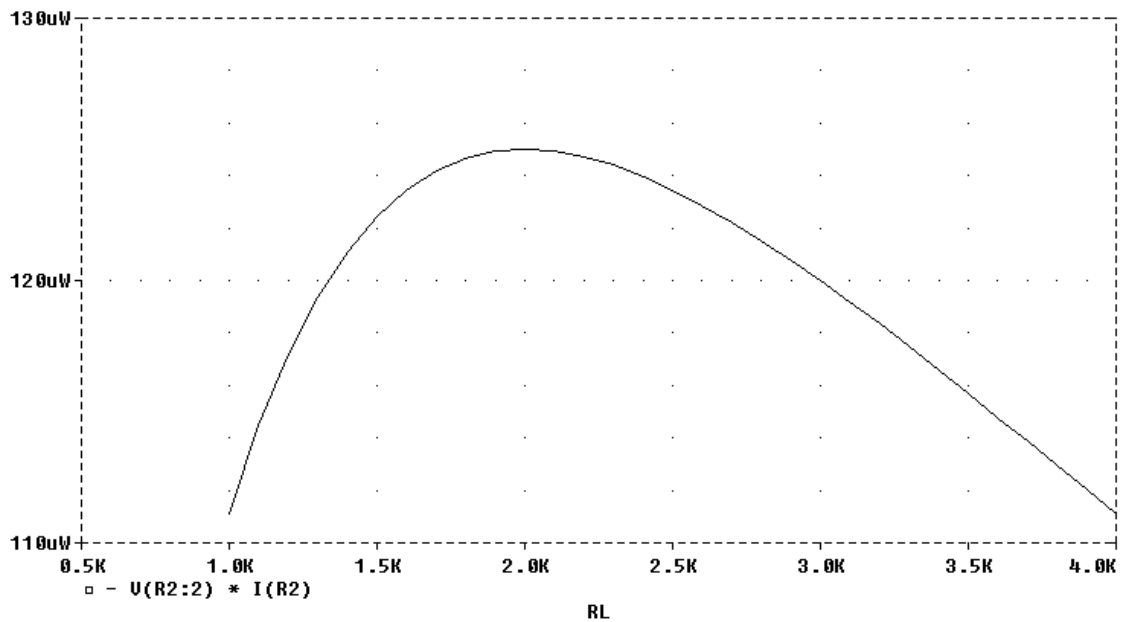P.P.4.15 The schematic is the same as that in Fig. 4.56 except that the 1-k Ω resistor is replaced by 2-k Ω resistor. The plot of the power absorbed by R_L is shown in the figure below. From the plot, it is clear that the maximum power occurs when $R_L = 2\text{k}\Omega$ and it is $125\ \mu\text{W}$.



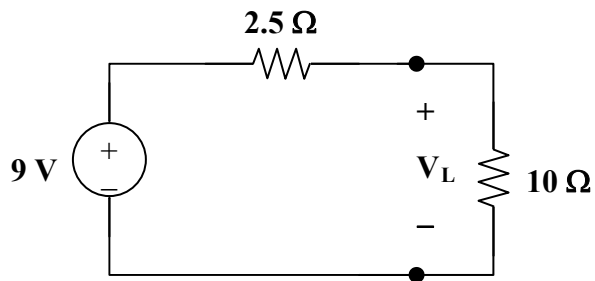P.P.4.16 $V_{Th} = 9\text{V}$, $R_{Th} = (v_{oc} - V_L) \frac{R_L}{V_L} = (9 - 1) \frac{20}{8} = 2.5\Omega$




$$V_L = \frac{10}{10 + 2.5} (9) = 7.2\text{ V}$$

P.P.4.17 $R_1 = R_3 = 1\text{k}\Omega$, $R_2 = 3.2\text{k}\Omega$


$$R_x = \frac{R_3}{R_1} R_2 = R_2 = 3.2 \text{ k}\Omega$$

P.P.4.18 We first find R_{Th} and V_{Th} . To get R_{Th} , consider the circuit in Fig. (a).
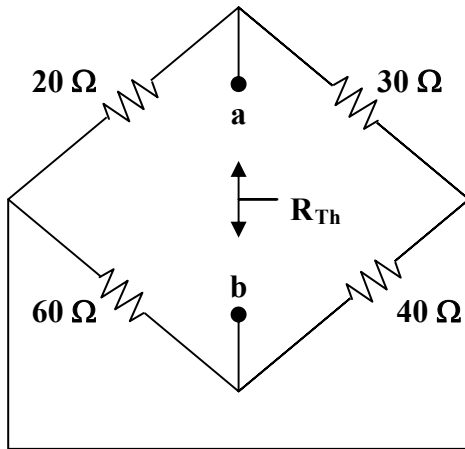
$$\begin{aligned} R_{Th} &= 20 \parallel (30 + 60) \parallel 40 = \frac{20 \times 30}{50} + \frac{60 \times 40}{100} \\ &= 12 + 24 = 36\Omega \end{aligned}$$



(a)

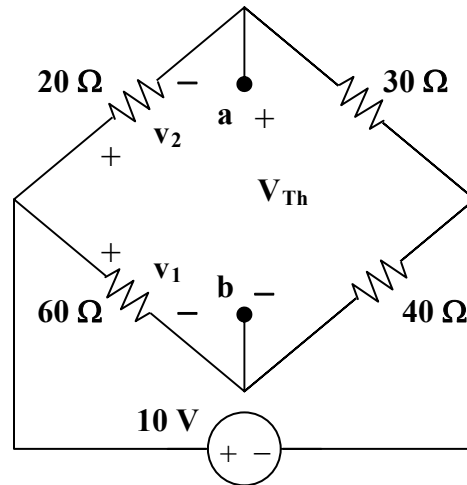

(b)

To find V_{Th} , we use Fig. (b). Using voltage division,

$$v_1 = \frac{60}{100}(16) = 9.6, \quad v_2 = \frac{20}{50}(16) = 6.4$$

$$\text{But } -v_1 + v_2 + v_{Th} = 0 \quad \longrightarrow \quad v_{Th} = v_1 - v_2 = 9.6 - 6.4 = 3.2\text{V}$$

$$I_G = \frac{V_{Th}}{R_{Th} + R_m} = \frac{3.2}{3.6 + 1.4} = 64\text{mA}$$