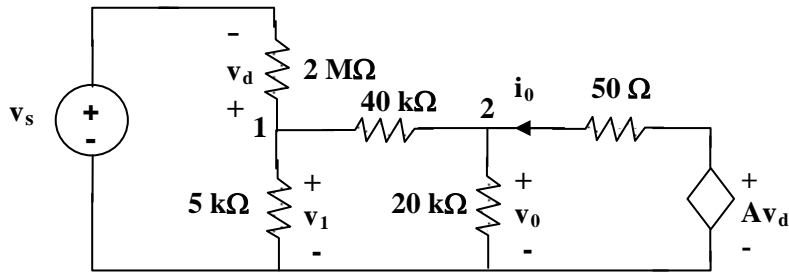


CHAPTER 5

P.P.5.1 The equivalent circuit is shown below:



$$\text{At node 1, } \frac{v_s - v_1}{2 \times 10^6} = \frac{v_1}{5 \times 10^3} + \frac{v_1 - v_0}{40 \times 10^3} \longrightarrow v_1 = \frac{v_s + 50v_0}{451} \quad (1)$$

$$\text{At node 2, } \frac{Av_d - v_0}{50} + \frac{v_1 - v_0}{40 \times 10^3} = \frac{v_0}{20 \times 10^3}$$

But $v_d = v_1 - v_s$.

$$[2 \times 10^5 (v_1 - v_s) - v_0] \frac{4000}{5} + v_1 - v_0 = 2v_0$$

$$1600 \times 10^5 (v_s - v_1) + 803v_0 \cong 0 \quad (2)$$

Substituting v_1 in (1) into (2) gives


$$1.5914523 \times 10^8 v_s - 17737556v_0 = 0$$

$$\frac{v_0}{v_s} = \frac{1.5964523 \times 10^8}{17737556} = \mathbf{9.00041}$$

If $v_s = 1 \text{ V}$, $v_0 = 9.00041 \text{ V}$, $v_1 = 1.0000455$

$$v_d = v_s - v_1 = -4.545 \times 10^{-5}$$

$$Av_d = -9.0909, \quad i_0 = \frac{Av_d - v_0}{50} = \mathbf{657 \mu A}$$

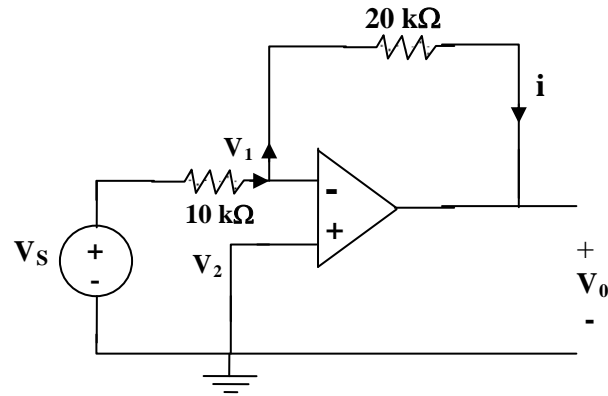P.P.5.2

At node 1, $\frac{v_s - v_1}{10} = \frac{v_1 - v_o}{20}$

But $v_1 = v_2 = 0$,

$$\frac{v_s}{10} = -\frac{v_o}{20} \longrightarrow \frac{v_o}{v_s} = -2$$


$$i_0 = \frac{0 - v_o}{20 \times 10^3} = -\frac{v_o}{20 \times 10^3}$$

When $v_s = 2\text{V}$, $v_o = -4$, $i_0 = \frac{4 \times 10^{-3}}{20} = 200 \mu\text{A}$

P.P.5.3 $v_o = -\frac{R_2}{R_1} v_i = \frac{-280}{4} (45\text{mV}) = -3.15 \text{ V}$

$$i = \frac{0 - v_o}{120\text{k}} = 26.25 \mu\text{A}$$

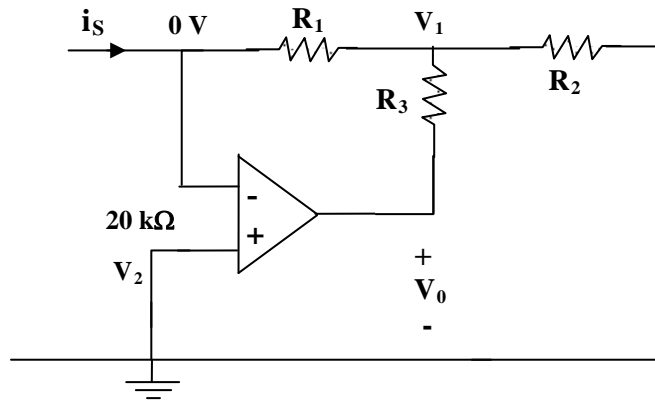P.P.5.4 (a) $i_s = \frac{0 - v_o}{R} \longrightarrow \frac{v_o}{i_s} = -R$



(b) At node 2, $i_s = \frac{0 - v_1}{R_1} \longrightarrow v_1 = -i_s R_1$ (1)

At node 1, $\frac{0 - v_1}{R_1} = \frac{v_1 - 0}{R_2} + \frac{v_1 - v_0}{R_3}$

$$-v_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{-v_0}{R_3}$$

$$v_0 = -i_s R_1 R_3 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{v_0}{i_s} = -R_1 \left(1 + \frac{R_3}{R_1} + \frac{R_3}{R_2} \right)$$

P.P.5.5 By voltage division

$$v_1 = \frac{8}{4+8}(3) = 2\text{V}$$

where v_1 is the voltage at the top end of the $8\text{k}\Omega$ resistor. Using the formula for noninverting amplifier,

$$v_0 = \left(1 + \frac{5}{2} \right) (2) = 7\text{V}$$

P.P.5.6 This is a summer.

$$v_o = -\left[\frac{8}{20}(1.5) + \frac{8}{10}(2) + \frac{8}{6}(1.2) \right] = -3.8 \text{ V}$$

$$i_o = \frac{v_o}{8} + \frac{v_o}{4} = -\frac{3.8}{8} - \frac{3.8}{4} = -1.425 \text{ mA}$$

P.P.5.7 If the gain is 7.5, then

$$\frac{R_2}{R_1} = 7.5 \longrightarrow R_2 = 7.5R_1$$

$$\text{But } \frac{R_2}{R_1} = \frac{R_4}{R_3} \longrightarrow R_4 = 7.5R_3$$

If we select $R_1 = R_3 = 20\text{k}\Omega$, then $R_2 = R_4 = 150 \text{ k}\Omega$.

$$\text{P.P.5.8 } v_o = \frac{R_2}{R_1} \left(1 + \frac{2R_3}{R_4} \right) (v_2 - v_1)$$

$R_3 = 0, R_4 = \infty, R_2 = 40\text{k}\Omega, R_1 = 20\text{k}\Omega$

$$v_o = \frac{40}{20}(6.98 - 7) = -0.04 \text{ volts.}$$

$$i_o = \frac{v_o}{50} = \frac{-0.04}{50} = -800 \text{ }\mu\text{A.}$$


P.P.5.9 Due to the voltage follower

$$v_a = 1.2 \text{ V}$$

For the noninverting amplifier,

$$v_o = \left(1 + \frac{200}{50} \right) v_a \quad v_o = (1 + 4)(1.2) = 6 \text{ V.}$$

$$i_o = \frac{v_b}{50} \text{ mA}$$

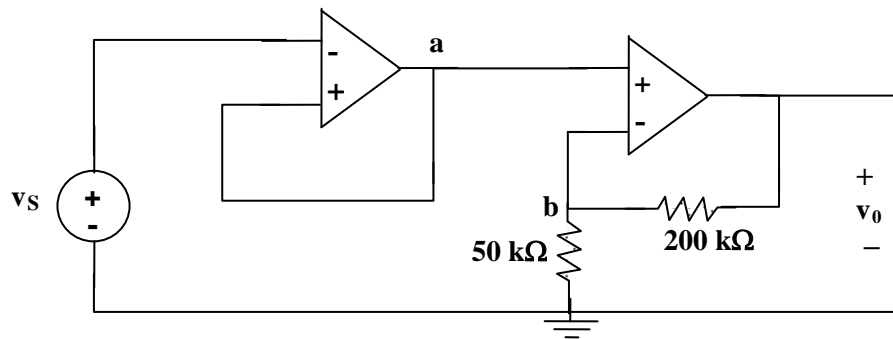

But $v_b = v_a = 4$

$$i_0 = \frac{1.2}{50 \times 10^3} = 24 \mu\text{A}.$$

P.P.5.10 As a voltage follower,

$$v_a = v_1 = 7 \text{ V}$$

where v_a is the voltage at the left end of the 20 kΩ resistor.

As an inverter, $v_b = -\frac{50}{10} v_2 = -15.5 \text{ V}$


Where v_b is the voltage at the right end of the 50 kΩ resistor. As a summer

$$v_0 = -\left[\frac{60}{20} v_a + \frac{60}{30} v_b \right]$$

$$= [-21 + 31] = 10 \text{ V}.$$

P.P.5.11 The schematic is shown below. When it is saved and run, the results are displayed on 1PROBE and VIEWPOINT as shown. By making $v_s = 1 \text{ V}$, we obtain
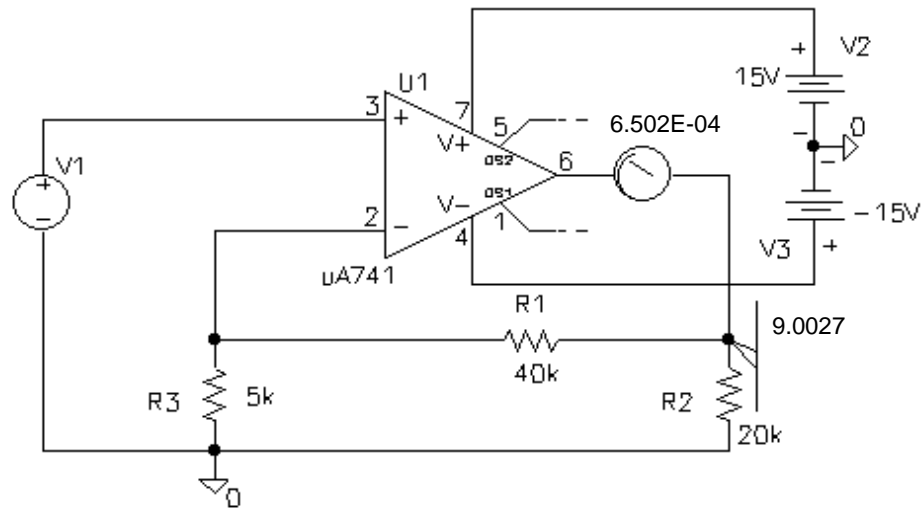
$$v_0 = 9.0027 \text{ V} \text{ and } i_0 = 650.2 \mu\text{A}$$



P.P.5.12
$$-V_0 = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3$$

or
$$|V_0| = V_1 + 0.5V_2 + 0.25V_3$$

- (a) If $[V_1 V_2 V_3] = [010]$, $|V_0| = \mathbf{0.5V}$
 (b) If $[V_1 V_2 V_3] = [110]$, $|V_0| = 1 + 0.5 = \mathbf{1.5V}$
 (c) If $|V_0| = 1.25$, then $V_1 = 1$, $V_2 = 0$, $V_3 = 1$, i.e.
 $[V_1 V_2 V_3] = \mathbf{[101]}$
 (d) $|V_0| = 1.75$, then $V_1 = 1$, $V_2 = 1$, $V_3 = 1$, i.e.
 $[V_1 V_2 V_3] = \mathbf{[111]}$

P.P.5.13
$$A_v = 1 + \frac{2R}{R_G} \longrightarrow R_G = \frac{2R}{A_v - 1}$$

$$R_G = \frac{2 \times 25 \times 10^3}{142 - 1} = \mathbf{354.6 \Omega}$$