 


## CHAPTER 7

**P.P.7.1** The circuit in Fig. (a) is equivalent to the one shown in Fig. (b).



$$R_{eq} = 8 + 12 \parallel 6 = 12 \Omega$$

$$\tau = R_{eq}C = (12)(1/3) = 4 \text{ s}$$


$$v_c = v_c(0)e^{-t/\tau} = 60e^{-t/4} = 60e^{-0.25t} \text{ V}$$

$$v_x = \frac{4}{4+8}v_c = 20e^{-0.25t} \text{ V}$$

$$v_x = v_o + v_c \longrightarrow v_o = v_x - v_c = -40e^{-0.25t} \text{ V}$$


$$i_o = \frac{v_o}{8} = -5e^{-0.25t} \text{ A.}$$

 **P.P.7.2** When  $t < 0$ , the switch is closed as shown in Fig. (a).



$$R_{eq} = 4 \parallel 12 = 3 \Omega \qquad v_c(0) = \frac{3}{3+6}(24) = 8 \text{ V}$$

 When  $t > 0$ , the switch is open as shown in Fig. (b).




$$\tau = R_{eq}C = (3)(1/6) = 1/2 \text{ s}$$

$$v(t) = v_c(0)e^{-t/\tau} = 8e^{-2t} \text{ V}$$

$$w_c(0) = \frac{1}{2}Cv_c^2(0) = \frac{1}{2} \times \frac{1}{6} \times 64 = 5.333\text{J}$$

**P.P.7.3** This can be solved in two ways.

 Method 1: Find  $R_{th}$  at the inductor terminals by inserting a voltage source.



Applying mesh analysis gives

$$\begin{aligned} \text{Loop 1:} \quad -1 + 3i_1 - 2i_2 + 2v_x &= 0, & \text{where } v_x &= li_1 \\ 5i_1 - 2i_2 &= 1 & (1) \end{aligned}$$

$$\begin{aligned} \text{Loop 2:} \quad 8i_2 - 2i_1 - 2v_x &= 0 = 8i_2 - 2i_1 - 2i_1 \\ i_2 &= \frac{1}{2}i_1 & (2) \end{aligned}$$


From (1) and (2),  $5i_1 - 1i_1 = 1$  or

$$i_o = i_1 = (1/4) \text{ A}$$

$$R_{th} = \frac{v_o}{i_o} = 4 \Omega, \quad \tau = \frac{L}{R} = \frac{2}{4} = \frac{1}{2} \text{ s}$$

$$i(t) = 12e^{-2t} \text{ A}$$

 Method 2: We can obtain  $i$  using mesh analysis.



Applying KVL to the loops, we obtain

$$\begin{aligned} \text{Loop 1:} \quad 2 \frac{di_1}{dt} + 3i_1 - 2i_2 + 2v_x &= 0 & \text{where } v_x = li_1 \\ 2 \frac{di_1}{dt} + 5i_1 - 2i_2 &= 0 & (3) \end{aligned}$$

$$\begin{aligned} \text{Loop 2:} \quad 8i_2 - 2i_1 - 2v_x &= 0 \\ i_2 &= \frac{1}{2}i_1 & (4) \end{aligned}$$

Substituting (4) into (3) yields

$$\begin{aligned} 2 \frac{di_1}{dt} + 5i_1 - li_1 &= 0 \\ \text{or } \frac{di_1}{dt} + 2i_1 &= 0 \\ i_1 &= Ae^{-2t} \end{aligned}$$

$$\begin{aligned} i &= -i_1 = Be^{-2t} \\ i(0) &= 12 = B \end{aligned}$$

$$i(t) = 12e^{-2t} \text{ A}$$


Therefore,

$$i(t) = 12e^{-2t} \text{ A}$$


and  $v_x(t) = -1i(t) = -12e^{-2t} \text{ V}$  for all  $t > 0$ .

 **P.P.7.4**

For  $t < 0$ , the equivalent circuit is shown in Fig. (a).



(a)

 

(b)

$$i(0) = 15 \left[ \frac{1}{\left\{ \frac{1}{24} + \frac{1}{12} + \frac{1}{8} \right\}} \right] / 12 = (15 \times 24 / 6) / 12 = 5 \text{ A}$$


For  $t > 0$ , the current source and 24-ohm is cut off and the RL circuit is shown in Fig. (b).

$$R_{eq} = (12 + 8) \parallel 5 = 20 \parallel 5 = 4 \Omega, \quad \tau = \frac{L}{R_{eq}} = \frac{2}{4} = 0.5$$


$$i(t) = i(0)e^{-2t} = 5e^{-2t} \text{ amps, for all } t > 0.$$

 **P.P.7.5**

For  $t < 0$ , the switch is closed. The inductor acts like a short so the equivalent circuit is shown in Fig. (a).



(a)

 

(b)

$$i = \frac{4}{4+2}(24) = 16 \text{ A}, \quad i_o = 24 - 16 = 8 \text{ A}, \quad v_o = 2i = 32 \text{ V}$$

For  $t > 0$ , the current source is cut off so that the circuit becomes that shown in Fig. (b). The Thevenin equivalent resistance at the inductor terminals is

$$R_{th} = (4 + 2) \parallel 3 = 2 \Omega, \quad \tau = \frac{L}{R_{th}} = \frac{1}{2}$$

$$i_o = \frac{3(-i)}{6+3} = \frac{-1}{3}i = -5.333e^{-2t} \text{ A} \quad \text{and} \quad v_o = -2i_o = 10.667e^{-2t} \text{ V}$$

Thus,

$$i = \begin{cases} 16 \text{ A} & t < 0 \\ 16e^{-2t} \text{ A} & t > 0 \end{cases} \quad i_o = \begin{cases} 8 \text{ A} & t < 0 \\ -5.333e^{-2t} \text{ A} & t > 0 \end{cases} \quad v_o = \begin{cases} 32 \text{ V} & t < 0 \\ 10.667e^{-2t} \text{ V} & t > 0 \end{cases}$$

**P.P.7.6**

$$i(t) = \begin{cases} 0 & t < 0 \\ 10 & 0 < t < 2 \\ -10 & 2 < t < 4 \end{cases}$$

$$i(t) = 10[u(t) - u(t-2)] - 10[u(t-2) - u(t-4)]$$

$$i(t) = \mathbf{10[u(t) - 2u(t-2) + u(t-4)]A}$$

Let  $I = \int_{-\infty}^t i \, dt$ .

For  $t < 0$ ,  $I = 0$ .

For  $0 < t < 2$ ,  $I = \int_0^t 10 \, dt = 10t$

For  $2 < t < 4$ ,  $I = \int_0^2 10 \, dt - 10 \int_2^t dt = 20 - 10t \Big|_2^t = 40 - 10t$


For  $t > 4$ ,  $I = 20 - 10t \Big|_2^4 = 0$

Thus,

$$I = \begin{cases} 0 & t < 0 \\ 10t & 0 < t < 2 \\ 40 - 10t & 2 < t < 4 \\ 0 & t > 4 \end{cases}$$

or  $I = \mathbf{10[r(t) - 2r(t-2) + r(t-4)]A}$

which is sketched below

 

**P.P.7.7**

$$i(t) = \begin{cases} 2 - 2t & 0 < t < 2 \\ -6 + 2t & 2 < t < 3 \\ 0 & \text{otherwise} \end{cases}$$

$$i(t) = (2 - 2t)[u(t) - u(t-2)] + (-6 + 2t)[u(t-2) - u(t-3)]$$

$$i(t) = 2u(t) - 2tu(t) + 4(t-2)u(t-2) - 2(t-3)u(t-3)$$

$$i(t) = [2u(t) - 2r(t) + 4r(t-2) - 2r(t-3)]A$$

Remember the singularity function,  $r(t)$ , is a ramp function equal to  $t$  for all values of  $t > 0$  and equal to zero for all values of  $t < 0$ .

**P.P.7.8**

$$h(t) = -4[u(t) - u(t-2)] + (3t-8)[u(t-2) - u(t-6)]$$

$$h(t) = -4u(t) + 4u(t-2) + 3tu(t-2) - 8u(t-2) - 3tu(t-6) + 8u(t-6)$$

$$h(t) = -4u(t) + (4-8+6)u(t-2) + 3(t-2)u(t-2) - 3(t-6)u(t-6) + (-18+8)u(t-6)$$

$$h(t) = -4u(t) + 2u(t-2) + 3(t-2)u(t-2) - 3(t-6)u(t-6) - 10u(t-6)$$

$$h(t) = -4u(t) + 2u(t-2) + 3r(t-2) - 10u(t-6) - 3r(t-6).$$

**P.P.7.9**

(a) 
$$\int_{-\infty}^{\infty} (t^3 + 5t^2 + 10)\delta(t+3) dt = t^3 + 5t^2 + 10 \Big|_{t=-3}$$

$$= -27 + 45 + 10 = \mathbf{28}$$

(b) 
$$\int_0^{10} \delta(t-\pi)\cos(3t) dt = \cos(3\pi) = \mathbf{-1}$$

**P.P.7.10** For  $t < 0$ , the capacitor acts like an open circuit.

$$v(0^-) = v(0^+) = v(0) = 15$$

For  $t > 0$ ,  $[(v(\infty)-15)/2] + [(v(\infty)-(-7.5))/6] = 0$  or  $(4/6)v(\infty) = 7.5 - 1.25 = 6.25$  or

$$v(\infty) = 9.375 \text{ V}$$

$$R_{th} = 2 \parallel 6 = \frac{3}{2} \Omega, \quad \tau = R_{th}C = \frac{3}{2} \times \frac{1}{3} = \frac{1}{2}$$

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} = 9.375 + (15 - 9.375)e^{-2t}$$

$$v(t) = \mathbf{(9.375 + 5.625e^{-2t}) \text{ V for all } t > 0}$$


At  $t = 0.5$ , 
$$v(0.5) = 6.25 + 3.75e^{-1} = 6.25 + 1.3795 = \mathbf{7.63 \text{ V}}$$

**P.P.7.11** For  $t < 0$ , only the left portion of the circuit is operational at steady state.

$$v(0^-) = v(0^+) = v(0) = 20, \quad i(0) = 0$$

For  $t > 0$ ,  $20u(-t) = 0$  so that the voltage source is replaced by a short circuit.

 Transforming the current source leads to the circuit below.



$$v(\infty) = \frac{5}{15}(30) = 10$$

$$R_{th} = 5 \parallel 10 = \frac{10}{3} \Omega, \quad \tau = R_{th}C = \frac{10}{3} \times 0.2 = \frac{2}{3}$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$v(t) = 10 + (20 - 10)e^{-3t/2}$$


$$v(t) = 10(1 + e^{-1.5t})$$

$$i(t) = \frac{-v(t)}{5} = -2(1 + e^{-1.5t})$$

$$i(t) = \begin{cases} 0 & t < 0 \\ -2(1 + e^{-1.5t}) \text{ A} & t > 0 \end{cases}$$

$$v(t) = \begin{cases} 20 \text{ V} & t < 0 \\ 10(1 + e^{-1.5t}) \text{ V} & t > 0 \end{cases}$$

 **P.P.7.12** Applying source transformation, the circuit is equivalent to the one below.



At  $t < 0$ , the switch is closed so that the 5 ohm resistor is short circuited.

$$i(0^-) = i(0) = \frac{60}{10} = 6 \text{ A}$$

For  $t > 0$ , the switch is open.

$$R_{th} = 10 + 5 = 15, \quad \tau = \frac{L}{R_{th}} = \frac{1.5}{15} = 0.1$$


$$i(\infty) = \frac{60}{10 + 5} = 4 \text{ A}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 4 + (6 - 4)e^{-10t}$$

$$i(t) = (4 + 2e^{-10t}) \text{ A for all } t > 0$$

 **P.P.7.13** For  $0 < t < 2$ , the given circuit is equivalent to that shown below.



Since switch  $S_1$  is open at  $t = 0^-$ ,  $i(0^-) = 0$ . Also, since  $i$  cannot jump,  $i(0) = i(0^-) = 0$ .

$$i(\infty) = \frac{90}{15 + 10 + 20} = 2 \text{ A}$$

$$R_{th} = 45 \Omega, \quad \tau = \frac{L}{R_{th}} = \frac{5}{45} = \frac{1}{9}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 2 + (0 - 2)e^{-9t}$$

$$i(t) = 2(1 - e^{-9t}) \text{ A}$$

When switch  $S_2$  is closed, the 20 ohm resistor is short-circuited.

$$i(2^+) = i(2^-) = 2(1 - e^{-18}) \cong 2$$

This will be the initial current

$$i(\infty) = \frac{90}{15 + 10} = 3.6 \text{ A}$$

$$R_{th} = 25 \Omega, \quad \tau = \frac{5}{25} = \frac{1}{5}$$

$$i(t) = i(\infty) + [i(2^+) - i(\infty)] e^{-(t-2)/\tau}$$

$$i(t) = 3.6 + (2 - 3.6)e^{-5(t-2)}$$

$$i(t) = 3.6 - 1.6e^{-5(t-2)}$$




$$\text{Thus, } i(t) = \begin{cases} 0 & t < 0 \\ 2(1 - e^{-9t}) \text{ A} & 0 < t < 2 \\ 3.6 - 1.6e^{-5(t-2)} \text{ A} & t > 2 \end{cases}$$

$$\text{At } t = 1, \quad i(1) = 2(1 - e^{-9}) = \mathbf{1.9997 \text{ A}}$$

$$\text{At } t = 3, \quad i(3) = 3.6 - 1.6e^{-5} = \mathbf{3.589 \text{ A}}$$

 **P.P.7.14** The op amp circuit is shown below.



Since nodes 1 and 2 must be at the same potential, there is no potential difference across  $R_1$ . Hence, no current flows through  $R_1$ . Applying KCL at node 1,

$$\frac{v}{R_f} + C \frac{dv}{dt} = 0 \quad \longrightarrow \quad \frac{dv}{dt} + \frac{v}{CR_f} = 0$$

which is similar to Eq. (7.4).

Hence,

$$v(t) = v_o e^{-t/\tau}, \quad \tau = R_f C$$

$$v(0) = v_o = 4, \quad \tau = (50 \times 10^3)(10 \times 10^{-6}) = 0.5$$

$$v(t) = 4e^{-2t} \text{ V}, \quad t > 0$$

Alternatively, since no current flows through  $R_1$ , the feedback loop forms a first order RC circuit with  $v(0) = 4$  and  $\tau = R_f C = 0.5$ . Hence,

$$v(t) = 4e^{-2t} \text{ V}, \quad t > 0$$

To get to  $v_o$  from  $v$ , we notice that  $v$  is the potential difference between node 1 and the output terminal, i.e.

$$0 - v_o = v \quad \longrightarrow \quad v_o = -v \quad \text{or} \quad v_o(t) = \mathbf{-4e^{-2t} \text{ V}, \quad t > 0}$$

**P.P.7.15** Let  $v_1$  be the potential at the inverting terminal.

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

where  $\tau = RC = 100 \times 10^3 \times 10^{-6} = 0.1$ ,  $v(0) = 0$

$$v_1 = 0 \text{ for all } t$$

$$v_1 - v_o = v \tag{1}$$

For  $t > 0$ , the switch is closed and the op amp circuit is an inverting amplifier with

$$v_o(\infty) = \frac{-100}{10} (4 \text{ mV}) = -40 \text{ mV}$$

From (1),

$$v(\infty) = 0 - v_o(\infty) = 40 \text{ mV}$$

Thus,

$$v(t) = 40(1 - e^{-10t})u(t) \text{ mV}$$

$$v_o = v_1 - v = -v$$

$$v_o = 40(e^{-10t} - 1)u(t) \text{ mV}$$


**P.P.7.16** This is a noninverting amplifier so that the output of the op amp is

$$v_a = \left(1 + \frac{R_f}{R_1}\right) v_i$$

$$v_{th} = v_a = \left(1 + \frac{R_f}{R_1}\right) v_i = \left(1 + \frac{40}{20}\right) 4.5u(t) = 13.5u(t)$$

To get  $R_{th}$ , consider the circuit shown in Fig. (a), where  $R_o$  is the output resistance of the op amp. For an ideal op amp,  $R_o = 0$  so that

$$R_{th} = R_3 = 10 \text{ k}\Omega$$

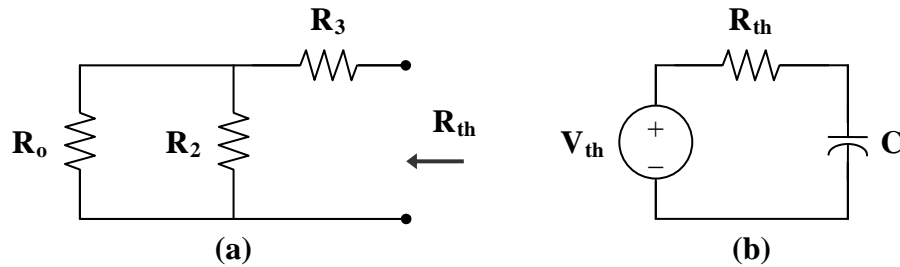

$$\tau = R_{th} C = 10 \times 10^3 \times 2 \times 10^{-6} = \frac{1}{50}$$



The Thevenin equivalent circuit is shown in Fig. (b), which is a first order circuit.

Hence,

$$v_o(t) = 13.5(1 - e^{-t/\tau})u(t)$$



$$v_o(t) = 13.5(1 - e^{-50t})u(t) \text{ V}$$

  **P.P.7.17** The schematic is shown in Fig. (a). Construct and save the schematic. Select Analysis/Setup/Transient to change the Final Time to 5 s. Set the Print Step slightly greater than 0 (20 ns is default). The circuit is simulated by selecting Analysis/Simulate. In the Probe menu, select Trace/Add and display V(R2:2) as shown in Fig. (b).




(b)

**P.P.7.18** The schematic is shown in Fig. (a). While constructing the circuit, rotate L1 counterclockwise through  $270^\circ$  so that current  $i(t)$  enters pin 1 of L1 and set  $IC = 10$  for L1. After saving the schematic, select Analysis/Setup/Transient to change the Final Time to 1 s. Set the Print Step slightly greater than 0 (20 ns is default). The circuit is simulated by selecting Analysis/ Simulate. After simulating the circuit, select Trace/Add in the Probe menu and display  $I(L1)$  as shown in Fig. (b).

 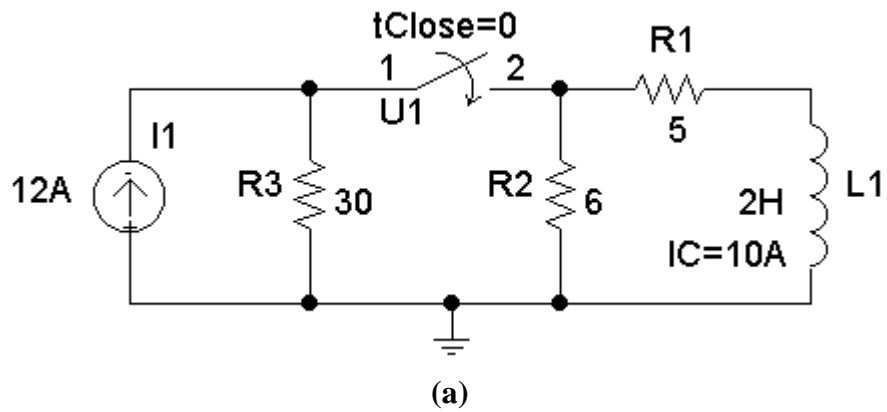

 **P.P.7.19**  $v(0) = 0$ . When the switch is closed, we have the circuit shown below.



We find the Thevenin equivalent at terminals a-b.

$$R_{th} = (R + 4) \parallel 10 = \frac{10(R + 4)}{R + 14}$$

$$v_{th} = v(\infty) = \frac{R + 4}{R + 14}(9)$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}, \quad \tau = R_{th}C$$

$$v(t) = v(\infty)(1 - e^{-t/\tau})$$

Since  $v(0) = 0$ ,

$$i(t) = \frac{v(t)}{R + 4} = \frac{9}{R + 4}(1 - e^{-t/\tau}) \text{ mA}$$

Assuming  $R$  is in  $k\Omega$ ,

$$120 \times 10^{-6} = \frac{9}{R + 14}(1 - e^{-t_0/\tau}) \times 10^{-3}$$

$$(0.12) \frac{R + 14}{9} = 1 - e^{-t_0/\tau}$$

or 
$$e^{-t_0/\tau} = 1 - \frac{0.12R + 1.68}{9} = \frac{7.32 - 0.12R}{9}$$

$$t_0 = \tau \ln\left(\frac{9}{7.32 - 0.12R}\right)$$

$$t_0 = \frac{10(R + 4)}{R + 14} \times 80 \times 10^{-6} \times \ln\left(\frac{9}{7.32 - 0.12R}\right)$$

When  $R = 0$ ,

$$t_0 = \frac{40 \times 80 \times 10^{-6}}{14} \times \ln\left(\frac{9}{7.32}\right) = 0.04723 \text{ s}$$

When  $R = 6 \text{ k}\Omega$ ,

$$t_0 = \frac{100}{20} \times 80 \times 10^{-6} \times \ln\left(\frac{9}{6.6}\right) = 0.124 \text{ s}$$

The time delay is **between 47.23 ms and 124 ms.**

**P.P.7.20**

(a)  $q = CV = (2 \times 10^{-3})(80) = \mathbf{160 \text{ mC}}$

(b)  $W = \frac{1}{2} CV^2 = \frac{1}{2} (2 \times 10^{-3})(6400) = \mathbf{6.4 \text{ J}}$

(c)  $\Delta I = \frac{\Delta q}{\Delta t} = \frac{0.16}{0.8 \times 10^{-3}} = \mathbf{200 \text{ A}}$

(d)  $p = \frac{\Delta w}{\Delta t} = \frac{6.4}{0.8 \times 10^{-3}} = \mathbf{8 \text{ kW}}$

(e)  $\Delta t = \frac{\Delta q}{\Delta I} = \frac{0.16}{5 \times 10^{-3}} = \mathbf{32 \text{ s}}$

**P.P.7.21**  $\tau = \frac{L}{R} = \frac{500 \times 10^{-3}}{200} = 2.5 \text{ ms}$

$$i(0) = 0, \quad i(\infty) = \frac{110}{200} = 550 \text{ mA}$$

$$i(t) = 550(1 - e^{-t/\tau}) \text{ mA}$$

$$350 \text{ mA} = i(t_0) = 550(1 - e^{-t_0/\tau}) \text{ mA}$$

$$\frac{35}{55} = 1 - e^{-t_0/\tau} \longrightarrow e^{-t_0/\tau} = \frac{20}{55}$$

$$e^{t_0/\tau} = \frac{55}{20}$$

$$t_0 = \tau \ln\left(\frac{55}{20}\right) = 2.5 \ln\left(\frac{55}{20}\right) \text{ ms}$$

$$t_0 = \mathbf{2.529 \text{ ms}}$$

**P.P.7.22**

(a)  $t = 5\tau = \frac{5L}{R} = \frac{5 \times 20 \times 10^{-3}}{5} = \mathbf{20 \text{ ms}}$

(b)  $W = \frac{1}{2} LI^2 = \frac{1}{2} (20 \times 10^{-3}) \left(\frac{12}{5}\right)^2 = \mathbf{57.6 \text{ mJ}}$

(c)  $V = L \frac{di}{dt} = 20 \times 10^{-3} \left(\frac{12/5}{2 \times 10^{-6}}\right) = \mathbf{24 \text{ kV}}$

