

CHAPTER 12

P.P.12.1 For the abc sequence, \mathbf{V}_{an} leads \mathbf{V}_{bn} by 120° and \mathbf{V}_{bn} leads \mathbf{V}_{cn} by 120° .

Hence,

$$\mathbf{V}_{an} = 110\angle(30^\circ + 120^\circ) = \mathbf{110}\angle\mathbf{150}^\circ \mathbf{V}$$

$$\mathbf{V}_{cn} = 110\angle(30^\circ - 120^\circ) = \mathbf{110}\angle\mathbf{-90}^\circ \mathbf{V}$$

P.P.12.2

(a) $\mathbf{V}_{ab} = \mathbf{V}_{an} - \mathbf{V}_{bn} = 120\angle 30^\circ - 120\angle -90^\circ$
 $\mathbf{V}_{ab} = (103.92 + j60) + j120$
 $\mathbf{V}_{ab} = \mathbf{207.8}\angle\mathbf{60}^\circ \mathbf{V}$

Alternatively, using the fact that \mathbf{V}_{ab} leads \mathbf{V}_{an} by 30° and has a magnitude of $\sqrt{3}$ times that of \mathbf{V}_{an} ,

$$\mathbf{V}_{ab} = \sqrt{3}(120)\angle(30^\circ + 30^\circ) = \mathbf{207.8}\angle\mathbf{60}^\circ \mathbf{V}$$

Following the abc sequence,

$$\mathbf{V}_{bc} = \mathbf{207.8}\angle\mathbf{-60}^\circ \mathbf{V}$$

$$\mathbf{V}_{ca} = \mathbf{207.8}\angle\mathbf{\pm 180}^\circ \mathbf{V}$$

(b) $\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}}$

$$\mathbf{Z} = (0.4 + j0.3) + (24 + j19) + (0.6 + j0.7)$$

$$\mathbf{Z} = 25 + j20 = 32\angle 38.66^\circ$$

$$\mathbf{I}_a = \frac{120\angle 30^\circ}{32\angle 38.66^\circ} = \mathbf{3.75}\angle\mathbf{-8.66}^\circ \mathbf{A}$$

Following the abc sequence,

$$\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ = \mathbf{3.75}\angle\mathbf{-128.66}^\circ \mathbf{A}$$

$$\mathbf{I}_c = \mathbf{I}_a \angle -240^\circ = \mathbf{3.75}\angle\mathbf{111.34}^\circ \mathbf{A}$$

P.P.12.3

The phase currents are

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_\Delta} = \frac{120\angle -20^\circ}{20\angle 40^\circ} = 6\angle -60^\circ \text{ A}$$

$$\mathbf{I}_{BC} = \mathbf{I}_{AB}\angle -120^\circ = 6\angle 180^\circ \text{ A}$$

$$\mathbf{I}_{CA} = \mathbf{I}_{AB}\angle 120^\circ = 6\angle 60^\circ \text{ A}$$

The line currents are

$$\mathbf{I}_a = \mathbf{I}_{AB}\sqrt{3}\angle -30^\circ = 6\sqrt{3}\angle -90^\circ = 10.392\angle -90^\circ \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_a\angle -120^\circ = 10.392\angle 150^\circ \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_a\angle 120^\circ = 10.392\angle 30^\circ \text{ A}$$

P.P.12.4 In a delta load, the phase current leads the line current by 30° and has a magnitude $\frac{1}{\sqrt{3}}$ times that of the line current. Hence,

$$\mathbf{I}_{AB} = \frac{\mathbf{I}_a}{\sqrt{3}}\angle 30^\circ = \frac{9.609}{\sqrt{3}}\angle 65^\circ = 5.548\angle 65^\circ \text{ A}$$

$$\mathbf{Z}_\Delta = 18 + j12 = 21.63\angle 33.69^\circ \Omega$$

$$\mathbf{V}_{AB} = \mathbf{I}_{AB}\mathbf{Z}_\Delta = (5.548\angle 65^\circ)(21.63\angle 33.69^\circ)$$

$$\mathbf{V}_{AB} = 120\angle 98.69^\circ \text{ V}$$

P.P.12.5 $\mathbf{Z}_Y = 12 + j15 = 19.21\angle 51.34^\circ$

After converting the Δ -connected source to a Y-connected source,

$$\mathbf{V}_{an} = \frac{240}{\sqrt{3}}\angle(150^\circ - 30^\circ) = 138.56\angle -15^\circ$$

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y} = \frac{138.56\angle -15^\circ}{19.21\angle 51.34^\circ} = 7.21\angle -66.34^\circ \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_a\angle -120^\circ = 7.21\angle 173.66^\circ \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_a\angle 120^\circ = 7.21\angle 53.66^\circ \text{ A}$$

P.P.12.6

For the source,

$$\begin{aligned}\mathbf{S} &= 3 \mathbf{V}_p \mathbf{I}_p^* = (3)(120 \angle 30^\circ)(3.75 \angle 8.66^\circ) \\ \mathbf{S} &= -1350 \angle 38.66^\circ = [-1.054.2 - j0.8433] \text{ kVA}\end{aligned}$$

For the load,

$$\mathbf{S} = 3 |\mathbf{I}_p|^2 \mathbf{Z}$$

$$\text{where } \mathbf{Z} = 24 + j19 = 30.61 \angle 38.37^\circ$$

$$\mathbf{I}_p = 3.75 \angle -8.66^\circ$$

$$\mathbf{S} = (3)(3.75)^2 (30.61 \angle 38.37^\circ)$$

$$\mathbf{S} = 1291.36 \angle 38.37^\circ = [1.012 + j0.8016] \text{ kVA}$$

$$\mathbf{P.P.12.7} \quad P = S \cos \theta \longrightarrow S = \frac{P}{\cos \theta} = \frac{30 \times 10^3}{0.85} = 35.29 \text{ kVA}$$

$$S = \sqrt{3} V_L I_L \longrightarrow I_L = \frac{S}{\sqrt{3} V_L} = \frac{35.29 \times 10^3}{\sqrt{3} (440)} = 46.31 \text{ A}$$

Alternatively,

$$P_p = \frac{30 \times 10^3}{3} = 10 \text{ kW}, \quad V_p = \frac{440}{\sqrt{3}} \text{ V}$$

$$P_p = V_p I_p \cos \theta$$

$$I_p = \frac{P_p}{V_p \cos \theta} = \frac{(10 \times 10^3) \sqrt{3}}{(440)(0.85)} = 46.31 \text{ A}$$

P.P.12.8

(a) For load 1,

$$V_p = \frac{V_L}{\sqrt{3}} = \frac{840}{\sqrt{3}}$$

$$\mathbf{I}_{a1} = \frac{\mathbf{V}_a}{\mathbf{Z}_p} = \frac{840 \angle 0^\circ}{\sqrt{3}} \cdot \frac{1}{30 + j40} = 9.7 \angle -53.13^\circ$$

$$\mathbf{S}_1 = \frac{V_{rms}^2}{\mathbf{Z}^*} = \frac{(840)^2}{50 \angle -53.15^\circ} = 14.112 \angle 53.13^\circ \text{ kVA}$$

For load 2,

$$S_2 = \frac{P_2}{\cos \theta_2} = \frac{48}{0.8} = 60 \text{ kVA}$$

$$Q_2 = S_2 \sin \theta_2 = (60)(0.6) = 36 \text{ kVAR}$$

$$\mathbf{S}_2 = 48 + j36 \text{ kVA}$$

$$\mathbf{S} = \mathbf{S}_1 + \mathbf{S}_2 = [56.47 + j47.29] \text{ kVA}$$

$$\mathbf{S} = 73.65 \angle 39.94^\circ \text{ kVA}$$

$$\text{with pf} = \cos(39.94^\circ) = 0.7667$$

(b) $Q_c = P(\tan \theta_{\text{old}} - \tan \theta_{\text{new}})$
 $Q_c = (56.47)(\tan 39.94^\circ - \tan 0^\circ) = 47.29 \text{ kVAR}$

For each capacitor, the rating is **15.76 kVAR**

(c) At unity pf, $\mathbf{S} = P = 56.47 \text{ kVA}$

$$I_L = \frac{\mathbf{S}}{\sqrt{3} V_L} = \frac{56470}{\sqrt{3}(840)} = \mathbf{38.81 A}$$

P.P.12.9

The phase currents are

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{AB}} = \frac{440 \angle 0^\circ}{10 - j5} = 39.35 \angle 26.56^\circ = 35.2 + j17.595$$

$$\mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_{BC}} = \frac{440 \angle -120^\circ}{16} = 27.5 \angle -120^\circ = -13.75 - j23.82$$

$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_{CA}} = \frac{440 \angle 120^\circ}{8 + j6} = 44 \angle 83.13^\circ = 5.263 + j43.68$$

The line currents are

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA} = (35.2 + j17.595) - (5.263 + j43.68) \\ = 29.94 - j26.08 = \mathbf{39.71 \angle -41.06^\circ A.}$$

$$\mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB} = -48.95 - j41.42 = \mathbf{64.12 \angle -139.8^\circ A.}$$

$$\mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC} = 19.013 + j67.5 = \mathbf{70.13 \angle 74.27^\circ A.}$$

P.P.12.10

The phase currents are

$$\mathbf{I}_{AB} = \frac{220\angle 0^\circ}{-j5} = j44$$

$$\mathbf{I}_{BC} = \frac{220\angle 0^\circ}{j10} = 22\angle 30^\circ$$

$$\mathbf{I}_{CA} = \frac{220\angle 120^\circ}{10} = 22\angle -120^\circ$$

The line currents are

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA} = (j44) - (-11 - j19.05)$$

$$\mathbf{I}_a = 11 + j63.05 = \mathbf{64\angle 80.1^\circ A}$$

$$\mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB} = (19.05 + j11) - (j44)$$

$$\mathbf{I}_b = 19.05 - j33 = \mathbf{38.1\angle -60^\circ A}$$

$$\mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC} = (-11 - j19.05) - (19.05 + j11)$$

$$\mathbf{I}_c = -30.05 - j30.05 = \mathbf{42.5\angle 225^\circ A}$$

The real power is absorbed by the resistive load


$$P = |\mathbf{I}_{CA}|^2 (10) = (22)^2 (10) = \mathbf{4.84 \text{ kW}}$$

P.P.12.11 The schematic is shown below. First, use the **AC Sweep** option of the **Analysis Setup**. Choose a *Linear* sweep type with the following *Sweep Parameters*: *Total Pts* = 1, *Start Freq* = 100, and *End Freq* = 100. Once the circuit is saved and simulated, we obtain an output file whose contents include the following results.


FREQ	IM(V_PRINT1)	IP(V_PRINT1)
1.000E+02	8.547E+00	-9.127E+01
FREQ	VM(A,N)	VP(A,N)
1.000E+02	1.009E+02	6.087E+01

From this we obtain,
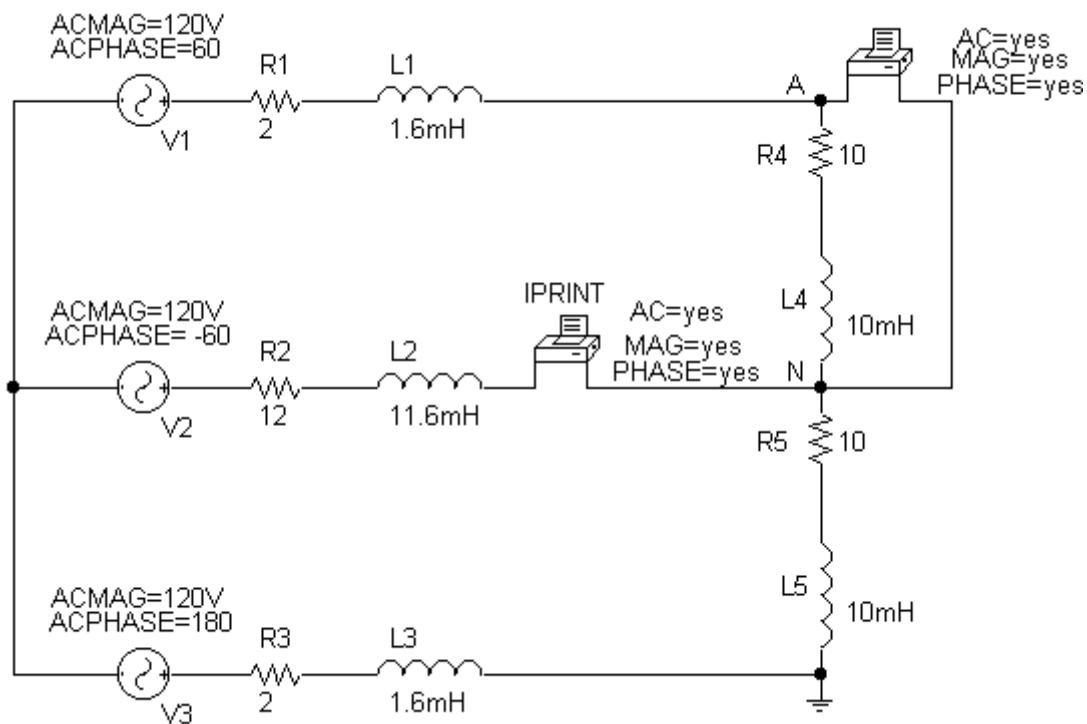
$$\mathbf{V}_{an} = \mathbf{100.9\angle 60.87^\circ V}, \quad \mathbf{I}_{bB} = \mathbf{8.547\angle -91.27^\circ A}$$



P.P.12.12 The schematic is shown below.

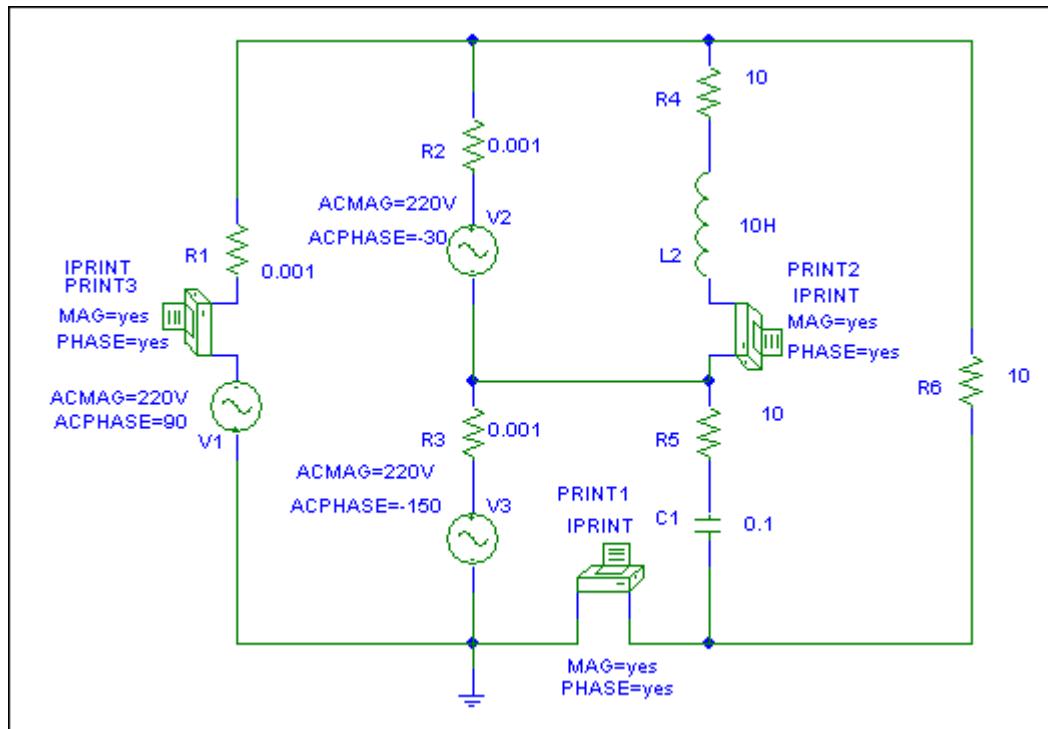

In this case, we may assume that $\omega = 1 \text{ rad/s}$, so that $f = 1/2\pi = 0.1592 \text{ Hz}$. Hence, $L = X_L/\omega = 10$ and $C = 1/\omega X_c = 0.1$.

Use the **AC Sweep** option of the **Analysis Setup**. Choose a *Linear* sweep type with the following *Sweep Parameters* : *Total Pts* = 1, *Start Freq* = 0.1592, and *End Freq* = 0.1592. Once the circuit is saved and simulated, we obtain an output file whose contents include the following results.

FREQ	IM(V_PRINT1)	IP(V_PRINT1)
1.592E-01	3.724E+01	8.379E+01
FREQ	IM(V_PRINT2)	IP(V_PRINT2)
1.592E-01	1.555E+01	-7.501E+01
FREQ	IM(V_PRINT3)	IP(V_PRINT3)
1.592E-01	2.468E+01	-9.000E+01

From this we obtain,

$$\mathbf{I}_{ca} = 24.68 \angle -90^\circ \text{ A} \quad \mathbf{I}_{cC} = 37.25 \angle 83.79^\circ \text{ A} \quad \mathbf{I}_{AB} = 15.55 \angle -75.01^\circ \text{ A}$$

P.P.12.13

- (a) If point o is connected to point B, $\mathbf{P}_2 = \mathbf{0} \text{ W}$
 $P_1 = \text{Re}(\mathbf{V}_{AB} \mathbf{I}_a^*)$
 $P_1 = (440)(39.71)\cos(0^\circ + 41.06^\circ) = \mathbf{13.175 \text{ kW}}$

$$P_3 = \text{Re}(\mathbf{V}_{CB} \mathbf{I}_c^*)$$

$$\text{where } \mathbf{V}_{CB} = -\mathbf{V}_{BC} = 240 \angle (-120^\circ + 180^\circ) = 240 \angle 60^\circ$$

$$P_3 = (440)(70.13)\cos(60^\circ - 74.27^\circ) = \mathbf{29.91 \text{ kW}}$$

- (b) Total power is $= (13.175 + 29.91) \text{ kW} = \mathbf{43.08 \text{ kW}}$.

P.P.12.14 $V_L = 208 \text{ V}$, $P_1 = -560 \text{ W}$, $P_2 = 800 \text{ W}$

(a) $P_T = P_1 + P_2 = -560 + 800 = \mathbf{240 \text{ W}}$

(b) $Q_T = \sqrt{3}(P_2 - P_1) = \sqrt{3}(800 + 560) = \mathbf{2.356 \text{ kVAR}}$

(c) $\tan \theta = \frac{Q_T}{P_T} = \frac{2355.6}{240} = 9.815 \longrightarrow \theta = 84.18^\circ$

$\text{pf} = \cos \theta = \mathbf{0.1014}$ (lagging / inductive)

It is inductive because $P_2 > P_1$

- (d) For a Y-connected load,

$$I_p = I_L, \quad V_p = \frac{V_L}{\sqrt{3}} = \frac{208}{\sqrt{3}} = 120 \text{ V}$$

$$P_p = V_p I_p \cos \theta \longrightarrow I_p = \frac{80}{(120)(0.1014)} = 6.575 \text{ A}$$

$$Z_p = \frac{V_p}{I_p} = \frac{120}{6.575} = 18.25$$

$$Z_p = Z_p \angle \theta = 18.25 \angle 84.18^\circ \Omega$$

The impedance is **inductive**.

$$\textbf{P.P.12.15} \quad Z_\Delta = 30 - j40 = 50 \angle -53.13^\circ$$

The equivalent Y-connected load is

$$Z_Y = \frac{Z_\Delta}{3} = 16.67 \angle -53.13^\circ$$

$$V_p = \frac{440}{\sqrt{3}} = 254 \text{ V}$$

$$I_L = \frac{V_p}{|Z_Y|} = \frac{254}{16.67} = 15.24$$

$$P_1 = V_L I_L \cos(\theta + 30^\circ)$$

$$P_1 = (440)(15.24) \cos(-53.13^\circ + 30^\circ) = \mathbf{6.167 \text{ kW}}$$

$$P_2 = V_L I_L \cos(\theta - 30^\circ)$$

$$P_2 = (440)(15.24) \cos(-53.13^\circ - 30^\circ) = \mathbf{802.1 \text{ W}}$$

$$P_T = P_1 + P_2 = \mathbf{6.969 \text{ kW}}$$

$$Q_T = \sqrt{3}(P_2 - P_1) = \sqrt{3}(802.1 - 6167)$$

$$Q_T = \mathbf{-9.292 \text{ kVAR}}$$