

**CHAPTER 13****P.P. 13.1** For mesh 1,

$$141.42 + j141.42 = 4(1 + j2)\mathbf{I}_1 + j\mathbf{I}_2 \quad (1)$$

For mesh 2,

$$0 = j\mathbf{I}_1 + (10 + j5)\mathbf{I}_2 \quad (2)$$

For the matrix form

$$\begin{bmatrix} 141.42 + j141.42 \\ 0 \end{bmatrix} = \begin{bmatrix} 4 + j8 & j \\ j & 10 + j5 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

$$\Delta = j100, \quad \Delta_2 = 141.42 - j141.42$$

$$\mathbf{I}_2 = \Delta_2 / \Delta = (141.42 - j141.42) / j100$$

$$\mathbf{V}_o = 10\mathbf{I}_2 = 10(-1.4142 - j1.4142) = \mathbf{20\angle-135^\circ V}$$

**P.P. 13.2** Since  $\mathbf{I}_1$  enters the coil with reactance  $2\Omega$  and  $\mathbf{I}_2$  enters the coil with reactance  $6\Omega$ , the mutual voltage is positive. Hence, for mesh 1,

$$100\angle 60^\circ = (5 + j2 + j6 - j3 \times 2)\mathbf{I}_1 - j6\mathbf{I}_2 + j3\mathbf{I}_2$$

or

$$100\angle 60^\circ = (5 + j2)\mathbf{I}_1 - j3\mathbf{I}_2 \quad (1)$$

For mesh 2,

$$0 = (j6 - j4)\mathbf{I}_2 - j6\mathbf{I}_1 + j3\mathbf{I}_1$$

or

$$\mathbf{I}_2 = 1.5\mathbf{I}_1 \quad (2)$$

Substituting this into (1),

$$100\angle 60^\circ = (5 - j2.5)\mathbf{I}_1$$

$$\mathbf{I}_1 = (100\angle 60^\circ) / (5.59\angle -26.57^\circ) = \mathbf{17.889\angle 86.57^\circ A}$$


$$\mathbf{I}_2 = 1.5\mathbf{I}_1 = \mathbf{26.83\angle 86.57^\circ A}$$

**P.P. 13.3** The coupling coefficient is,  $k = m / \sqrt{L_1 L_2} = 1 / \sqrt{2 \times 1} = \mathbf{0.7071}$ 

To obtain the energy stored, we first obtain the frequency-domain circuit shown below.

$$100\cos(\omega t) \text{ becomes } 100\angle 0^\circ, \quad \omega = 2$$

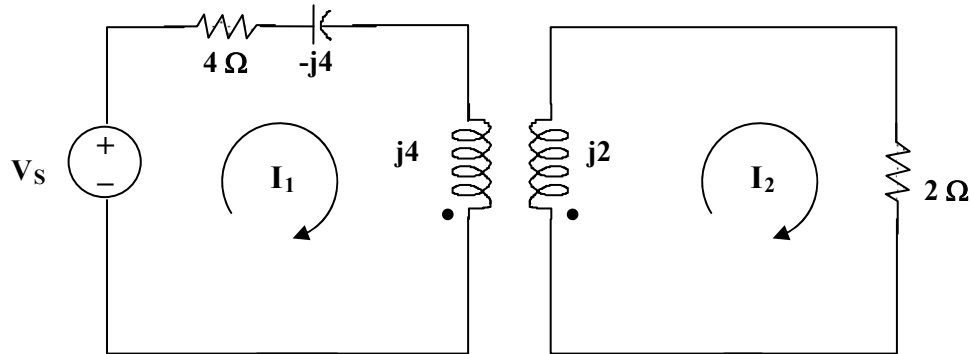$1\text{H}$  becomes  $j\omega 1 = j2$   
 $2\text{H}$  becomes  $j\omega 2 = j4$   
 $(1/8)\text{F}$  becomes  $1/j\omega C = -j4$



For mesh 1,  $100 = (4 - j4 + j4)\mathbf{I}_1 - j2\mathbf{I}_2$   
 or  $50 = 2\mathbf{I}_1 - j\mathbf{I}_2$  (1)

For mesh 2,  $-j2\mathbf{I}_1 + (2 + j2)\mathbf{I}_2 = 0$   
 or  $\mathbf{I}_1 = (1 - j)\mathbf{I}_2$  (2)

Substituting (2) into (1),  $(2 - j3)\mathbf{I}_2 = 50$

$$\mathbf{I}_2 = 50/(2 - j3) = 13.87\angle 56.31^\circ$$

$$\mathbf{I}_1 = 19.658\angle 11.31^\circ$$

In the time domain,  
 $i_1 = 19.658\cos(2t + 11.31^\circ)$   
 $i_2 = 13.87\cos(2t + 56.31^\circ)$

At  $t = 1.5$ ,  $2t = 3 \text{ rad} = 171.9^\circ$

$$i_1 = 19.658\cos(171.9^\circ + 11.31^\circ) = -19.62 \text{ A}$$

$$i_2 = 13.87\cos(171.9^\circ + 56.31^\circ) = -9.25 \text{ A}$$

The total energy stored in the coupled inductors is given by,

$$\begin{aligned}
 W &= 0.5L_1(i_1)^2 + 0.5L_2(i_2)^2 - 0.5M(i_1i_2) \\
 &= 0.5(2)(-19.62)^2 + 0.5(1)(-9.25)^2 - (1)(-19.62)(-9.25) \\
 &= \mathbf{246.2 \text{ J}}
 \end{aligned}$$

**P.P. 13.4**

$$\begin{aligned} \mathbf{Z}_{in} &= 4 + j8 + [3^2/(j10 - j6 + 6 + j4)] \\ &= 4 + j8 + 9/(6 + j8) \\ &= \mathbf{8.58\angle 58.05^\circ \Omega} \end{aligned}$$

The current from the voltage is,

$$\mathbf{I} = \mathbf{V/Z} = 40\angle 0^\circ / 8.58\angle 58.05^\circ = \mathbf{4.662\angle -58.05^\circ \text{ A}}$$

**P.P. 13.5**

$$L_1 = 10, L_2 = 4, M = 2$$


$$L_1 L_2 - M^2 = 40 - 4 = 36$$

$$L_A = (L_1 L_2 - M^2)/(L_2 - M) = 36/(4 - 2) = \mathbf{18 \text{ H}}$$

$$L_B = (L_1 L_2 - M^2)/(L_1 - M) = 36/(10 - 2) = \mathbf{4.5 \text{ H}}$$


$$L_C = (L_1 L_2 - M^2)/M = 36/2 = \mathbf{18 \text{ H}}$$

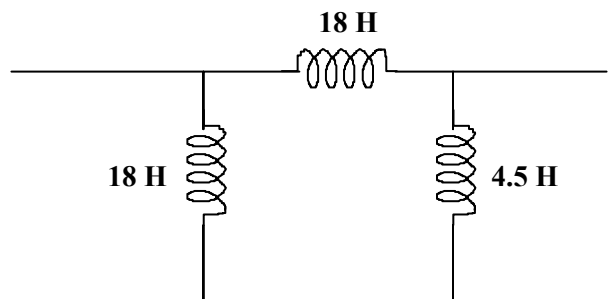Hence, we get the  $\pi$  equivalent circuit as shown below.



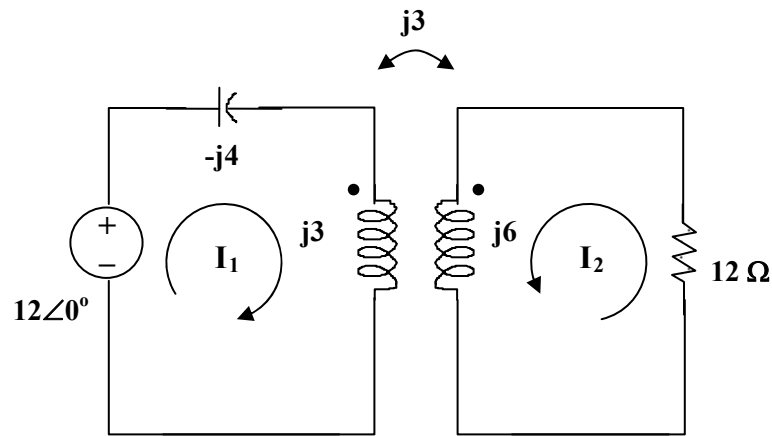**P.P. 13.6**

If we reverse the direction of  $I_2$  so that we replace  $I_2$  by  $-I_2$ , we have the circuit shown in Figure (a).



(a)


We now replace the coupled coil by the T-equivalent circuit and assume  $\omega = 1$ .

$$L_a = 5 - 3 = 2 \text{ H}$$

$$L_b = 6 - 3 = 3 \text{ H}$$

$$L_c = 3 \text{ H}$$

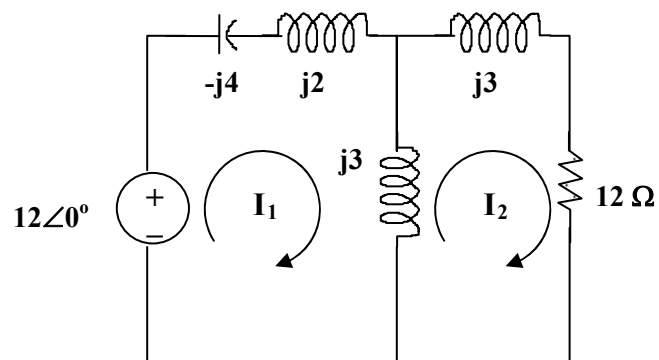Hence the equivalent circuit is shown in Figure (b). We apply mesh analysis.



(b)

$$12 = i_1(-j4 + j2 + j3) + j3i_2$$

$$\text{or } 12 = ji_1 + j3i_2 \quad (1)$$

Loop 2 produces,  $0 = j3i_1 + (j3 + j3 + 12)i_2$

$$\text{or } i_1 = (-2 + j4)i_2 \quad (2)$$

Substituting (2) into (1),  $12 = (-4 + j)i_2$ , which leads to  $i_2 = 12/(-4 + j)$

$$I_2 = -i_2 = 12/(4 - j) = \mathbf{2.91\angle 14.04^\circ \text{ A}}$$

$$I_1 = i_1 = (-2 + j4)i_2 = 12(2 - j4)/(4 - j) = \mathbf{13\angle -49.4^\circ \text{ A}}$$

### P.P. 13.7

(a)  $n = V_2/V_1 = 110/2200 = \mathbf{1/20}$  (a step-down transformer)

(b)  $S = V_1 I_1 = 2200 \times 5 = \mathbf{11 \text{ kVA}}$

(c)  $I_2 = I_1/n = 5/(1/20) = \mathbf{100 \text{ A}}$

### P.P. 13.8

resulting in

The  $16 - j24$ -ohm impedance can be reflected to the primary

$$Z_{in} = 2 + (16 - j24)/16 = 3 - j1.5$$


$$I_1 = 240/(3 - j1.5) = 240/(3.354\angle -26.57^\circ) = 71.56\angle 26.57^\circ$$

$$I_2 = -I_1/n = -17.89\angle 26.57^\circ$$

$$V_o = -j24i_2 = (24\angle -90^\circ)(-17.89\angle 26.57^\circ) = \mathbf{429.4\angle 116.57^\circ \text{ V}}$$

$$S_1 = V_1 I_1 = (240)(71.56\angle 26.57^\circ) = \mathbf{17.174\angle -26.57^\circ \text{ kVA.}}$$

**P.P. 13.9**

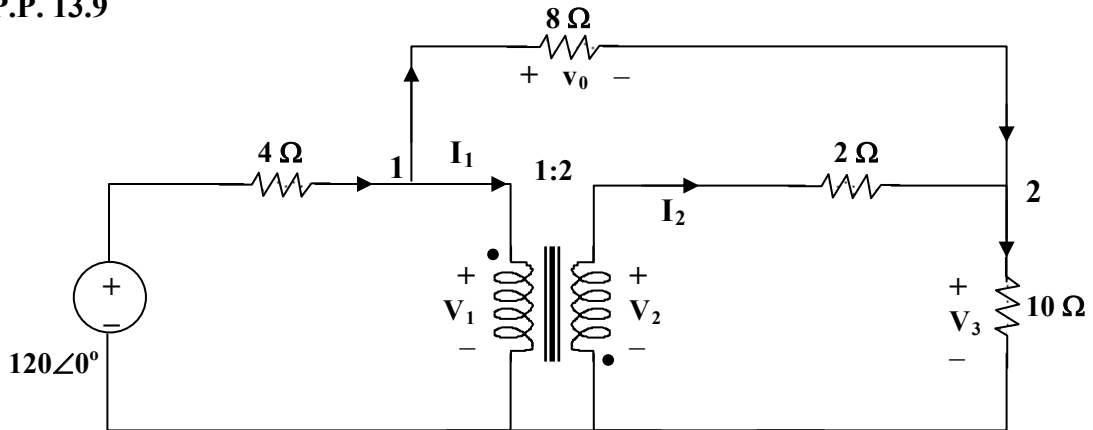

Consider the circuit shown above.

$$\text{At node 1,} \quad (120 - V_1)/4 = I_1 + (V_1 - V_3)/8 \quad (1)$$

$$\text{At node 2,} \quad [(V_1 - V_3)/8] + [(V_2 - V_3)/2] = (V_3)/8 \quad (2)$$

$$\text{At the transformer terminals,} \quad V_2 = -2V_1 \text{ and } I_2 = -I_1/2 \quad (3)$$

$$\text{But } I_2 = (V_2 - V_3)/2 = -I_1/2 \text{ which leads to } I_1 = (V_3 - V_2)/1 = V_3 + 2V_1.$$

Substituting all of this into (1) and (2) leads to,

$$(120 - V_1)/4 = V_3 + 2V_1 + (V_1 - V_3)/8 \text{ which leads } 240 = 19V_1 + 7V_3 \quad (4)$$

$$[(V_1 - V_3)/8] + [(-2V_1 - V_3)/2] = V_3/8 \text{ which leads to } V_3 = -7V_1/6 \quad (5)$$


From (4) and (5),

$$240 = 10.833V_1 \text{ or } V_1 = 22.155 \text{ volts}$$

$$V_3 = -7V_1/6 = -25.85 \text{ volts}$$

$$V_o = V_1 - V_3 = \mathbf{48 \text{ volts}}$$

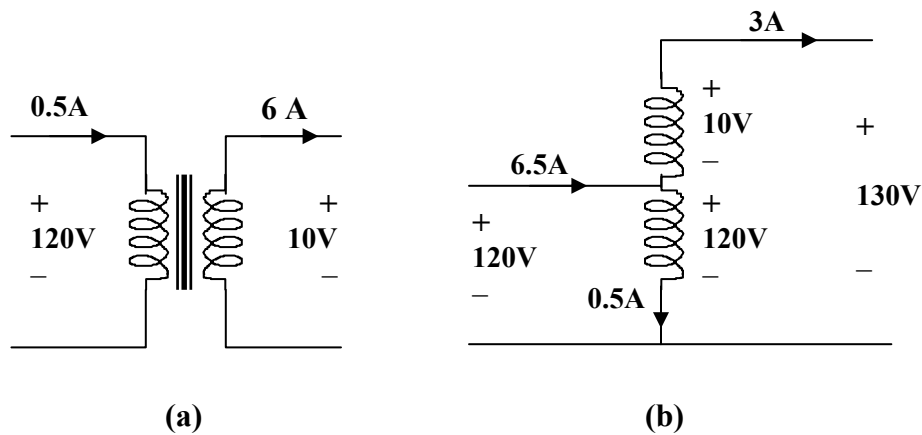**P.P. 13.10** We should note that the current and voltage of each winding of the autotransformer in Figure (b) are the same for the two-winding transformer in Figure (a).



For the two-winding transformer,

$$S_1 = 120 \times 0.5 = 60 \text{ VA}$$

$$S_2 = 6(10) = 60 \text{ VA}$$

For the autotransformer,

$$S_1 = 120(6.5) = 780 \text{ VA}$$

$$S_2 = 130(6) = 780 \text{ VA}$$

**P.P. 13.11**  $(I_2)^* = S_2/V_2 = 16,000/1000 = 16 \text{ A}$

Since  $S_1 = V_1(I_1)^* = V_2(I_2)^* = S_2$ ,  $V_2/V_1 = I_1/I_2$ ,  $1000/2500 = I_1/32$ ,

or  $I_1 = 1000 \times 16 / 2500 = 6.4 \text{ A}$ .

At the top, KCL produces  $I_1 + I_o = I_2$ , or  $I_o = I_2 - I_1 = 16 - 6.4 = 9.6 \text{ A}$ .

**P.P. 13.12**

(a)  $S_T = (\sqrt{3})V_L I_L$ , but  $S_T = P_T/\cos\theta = 40 \times 10^6 / 0.85 = 47.0588 \text{ MVA}$

$$I_{LS} = S_T / (\sqrt{3})V_{LS} = 47.0588 \times 10^6 / [(\sqrt{3})12.5 \times 10^3] = \mathbf{2.174 \text{ kA}}$$


(b)  $V_{LS} = 12.5 \text{ kV}$ ,  $V_{LP} = 625 \text{ kV}$ ,  $n = V_{LS}/V_{LP} = 12.5/625 = \mathbf{0.02}$

(c)  $I_{LP} = nI_{LS} = 0.02 \times 2173.6 = \mathbf{43.47 \text{ A}}$

or  $I_{LP} = S_T / [(\sqrt{3})V_{LP}] = 47.0588 \times 10^6 / [(\sqrt{3})625 \times 10^3] = \mathbf{43.47 \text{ A}}$

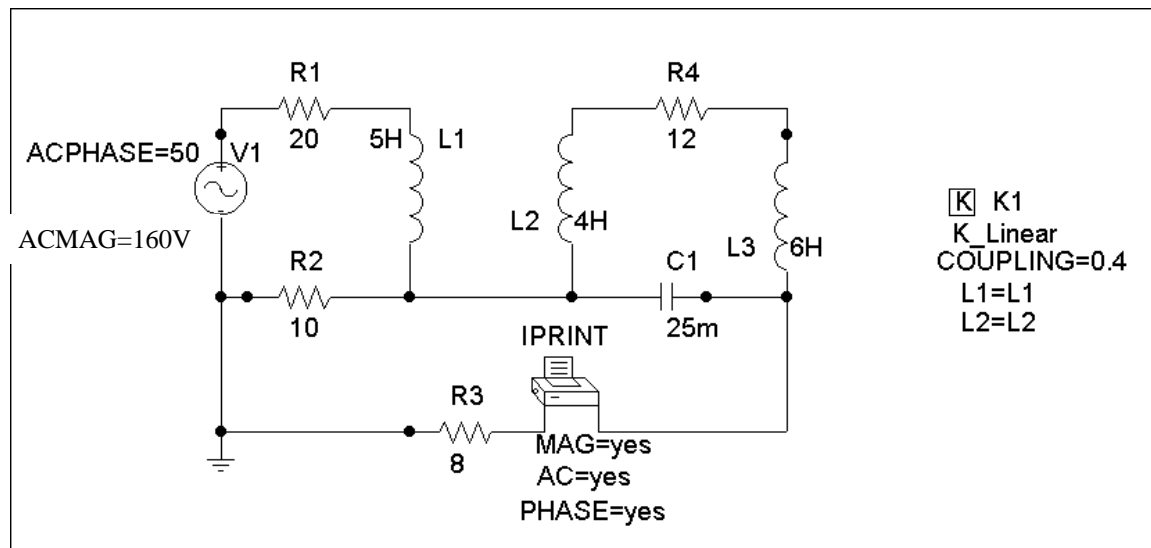(d) The load carried by each transformer is  $(1/3)S_T = \mathbf{15.69 \text{ MVA}}$

**P.P. 13.13** The process is essentially the same as in Example 13.13. We are given the coupling coefficient,  $k = 0.4$ , and can determine the operating frequency from the value of  $\omega = 4$  which implies that  $f = 4/(2\pi) = 0.6366 \text{ Hz}$ .



Saving and then simulating produces,




$$i_o = 2.012\cos(4t + 68.52^\circ) \text{ A}$$

**P.P. 13.14** Following the same basic steps in Example 13.14, we first assume  $\omega = 1$ . This then leads to following determination of values for the inductor and the capacitor.

$$j15 = j\omega L \text{ leads to } L = 15 \text{ H}$$

$$-j16 = 1/(\omega C) \text{ leads to } C = 62.5 \text{ mF}$$

The schematic is shown below.

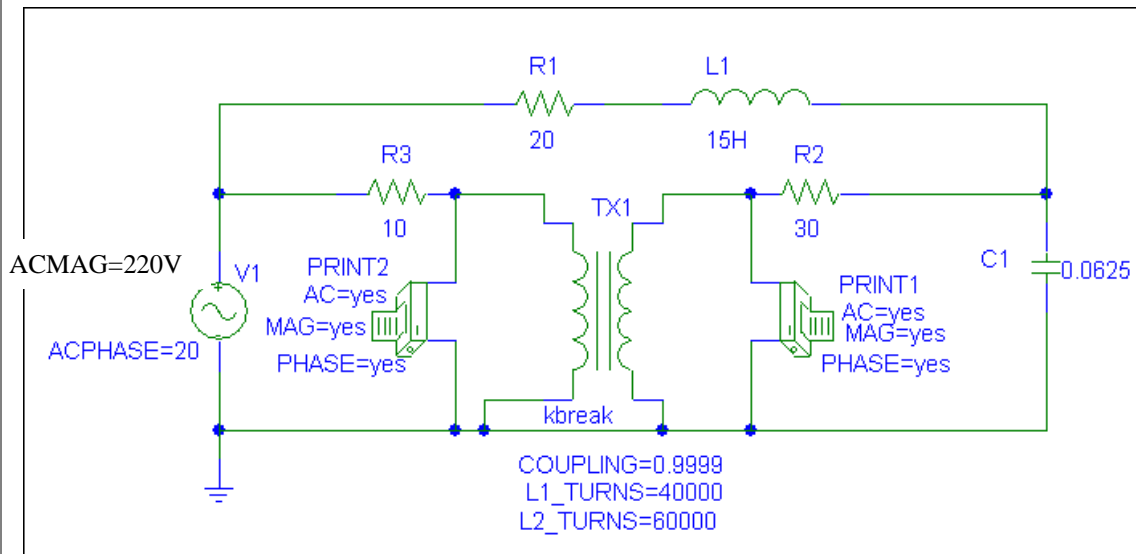

FREQ	VM(\$N_0005,0)	VP(\$N_0005,0)
1.592E-01	1.530E+02	2.185E+00
FREQ	VM(\$N_0001,0)	VP(\$N_0001,0)
1.592E-01	2.302E+02	2.091E+00

Thus,


$$\mathbf{V}_1 = 153\angle 2.18^\circ \text{ V}$$

$$\mathbf{V}_2 = 230.2\angle 2.09^\circ \text{ V}$$

Note, if we divide  $V_2$  by  $V_1$  we get  $1.5046\angle-.09^\circ$  which is in good agreement that the transformer is ideal with a voltage ratio of 1:1.5 (or 2:3)!

**P.P. 13.15**     $V_2/V_1 = 120/13,200 = 1/110 = 1/n$

**P.P. 13.16**

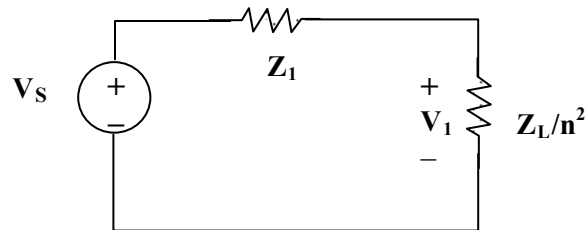

As in Example 13.16,  $n^2 = Z_L/Z_1 = 400/(2.5 \times 10^3) = 4/25$ ,  $n = 0.4$

By voltage division,  $V_1 = V_s/2$  (since  $Z_1 = Z_L/n^2$ ), therefore  $V_1 = 60/2 = 30$  volts, and

$$V_2 = nV_1 = (0.4)(30) = 12 \text{ volts}$$

**P.P. 13.17**

(a)     $S = 12 \times 60 + 350 + 4,500 = 5.57 \text{ kW}$

(b)     $I_P = S/V_P = 5570/2400 = 2.321 \text{ A}$