

CHAPTER 14

P.P.14.1 $\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{j\omega L}{\mathbf{R} + j\omega L}$


$$\mathbf{H}(\omega) = \frac{j\omega L/R}{1 + j\omega L/R} = \frac{j\omega/\omega_0}{1 + j\omega/\omega_0}$$

where $\omega_0 = \frac{R}{L}$.

$$H = |\mathbf{H}(\omega)| = \frac{\omega/\omega_0}{\sqrt{1 + (\omega/\omega_0)^2}} \qquad \phi = \angle \mathbf{H}(\omega) = \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

At $\omega = 0$, $H = 0$, $\phi = 90^\circ$
 As $\omega \rightarrow \infty$, $H = 1$, $\phi = 0^\circ$
 At $\omega = \omega_0$, $H = \frac{1}{\sqrt{2}}$, $\phi = 90^\circ - 45^\circ = 45^\circ$

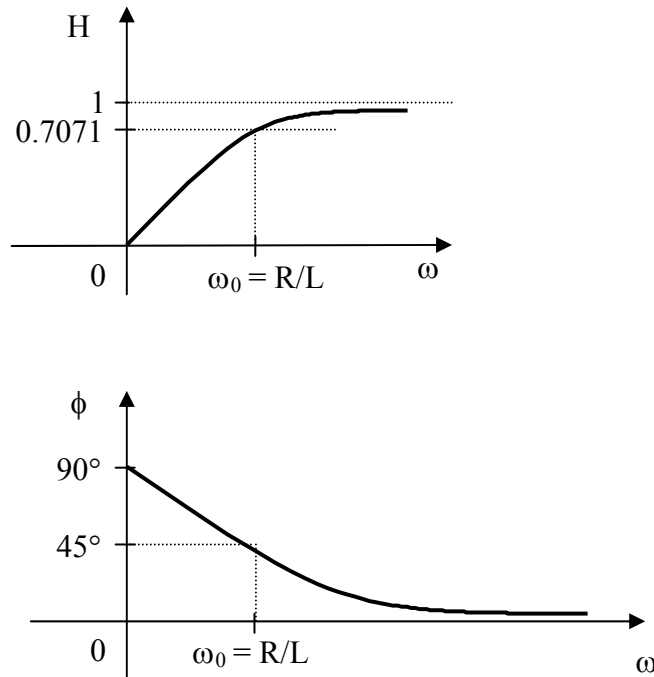Thus, the sketches of H and ϕ are shown below.



P.P.14.2 The desired transfer function is the input impedance.

$$Z_i(s) = \frac{V_o(s)}{I_o(s)} = \left(10 + \frac{1}{s/20} \right) \parallel (6 + 2s)$$

$$Z_i(s) = \frac{(10 + 20/s)(6 + 2s)}{10 + 20/s + 6 + 2s} = \frac{10(s + 2)(s + 3)}{s^2 + 8s + 10}$$

The poles are at

$$p_{1,2} = \frac{-8 \pm \sqrt{64 - 40}}{2} = -1.5505, -6.449$$

The zeros are at

$$z_1 = -2, \quad z_2 = -3.$$

P.P.14.3
$$H(\omega) = \frac{1 + j\omega/2}{(j\omega)(1 + j\omega/10)}$$

$$H_{db} = 20 \log_{10} |1 + j\omega/2| - 20 \log_{10} |j\omega| - 20 \log_{10} |1 + j\omega/10|$$

$$\phi = -90^\circ + \tan^{-1}(\omega/2) - \tan^{-1}(\omega/10)$$

The magnitude and the phase plots are as shown in Fig. 14.14.

P.P.14.4
$$H(\omega) = \frac{(50/400)j\omega}{(1 + j\omega/4)(1 + j\omega/10)^2}$$

$$H_{db} = -20 \log_{10} |8| + 20 \log_{10} |j\omega| - 20 \log_{10} |1 + j\omega/4| - 40 \log_{10} |1 + j\omega/10|$$

$$\phi = 90^\circ - \tan^{-1}(\omega/4) - 2 \tan^{-1}(\omega/10)$$

The magnitude and the phase plots are as shown in Fig. 14.16.

P.P.14.5
$$H(\omega) = \frac{10/400}{(j\omega) \left(1 + \frac{j\omega 8}{40} + \left(\frac{j\omega}{20} \right)^2 \right)}$$

$$H_{db} = -20 \log_{10} |40| - 20 \log_{10} |j\omega| - 20 \log_{10} |1 + j\omega/5 - \omega^2/400|$$

$$\phi = -90^\circ - \tan^{-1} \left(\frac{0.2\omega}{1 - \omega^2/400} \right)$$

The magnitude and the phase plots are as shown in Fig. 14.18.

P.P.14.6

The gain is = 40 db = $20\log_{10}(\text{gain})$ or the gain = 100.

A zero at $\omega = 5$, $1 + j\omega/5$

A pole at $\omega = 10$, $\frac{1}{1 + j\omega/10}$

Two poles at $\omega = 100$, $\frac{1}{(1 + j\omega/100)^2}$

Hence,

$$\mathbf{H(\omega)} = \frac{100(1 + j\omega/5)}{(1 + j\omega/10)(1 + j\omega/100)^2} = \frac{100(1/5)(5 + j\omega)}{(1/100,000)(10 + j\omega)(100 + j\omega)^2}$$

$$\mathbf{H(\omega)} = \frac{2,000,000(s + 5)}{(s + 10)(s + 100)^2}$$

P.P.14.7

$$(a) \quad Q = \frac{\omega_0 L}{R} \longrightarrow \omega_0 = \frac{QR}{L} = \frac{(50)(4)}{25 \times 10^{-3}} = 8 \times 10^3 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \longrightarrow C = \frac{1}{\omega_0^2 L} = \frac{1}{(64 \times 10^6)(25 \times 10^{-3})}$$

$$C = \mathbf{0.625 \mu F}$$

$$(b) \quad B = \frac{\omega_0}{Q} = \frac{8 \times 10^3}{50} = \mathbf{160 \text{ rad/s}}$$

Since $Q > 10$,

$$\omega_1 = \omega_0 - \frac{B}{2} = 8000 - 80 = \mathbf{7920 \text{ rad/s}}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 8000 + 80 = \mathbf{8080 \text{ rad/s}}$$

$$(c) \quad \text{At } \omega = \omega_0, \quad P = \frac{V_{in}^2}{2R} = \frac{100^2}{8} = \mathbf{1.25 \text{ kW}}$$

$$\text{At } \omega = \omega_1, \quad P = 0.5 \cdot \frac{V_{in}^2}{2R} = \mathbf{0.625 \text{ kW}}$$

$$\text{At } \omega = \omega_2, \quad P = 0.5 \cdot \frac{V_{in}^2}{2R} = \mathbf{0.625 \text{ kW}}$$

P.P.14.8 $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(20 \times 10^{-3})(5 \times 10^{-9})}} = 10^5 = \mathbf{100 \text{ krad/s}}$

$$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{(10^5)(20 \times 10^{-3})} = \mathbf{50}$$

$$B = \frac{\omega_0}{Q} = \frac{10^5}{50} = \mathbf{2 \text{ krad/s}}$$

Since $Q > 10$,

$$\omega_1 = \omega_0 - \frac{B}{2} = 100,000 - 1,000 = \mathbf{99 \text{ krad/s}}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100,000 + 1,000 = \mathbf{101 \text{ krad/s}}$$

P.P.14.9 $Z = j\omega 0.01 + 20 \parallel \frac{2000}{j\omega} = j\omega 0.01 + \frac{20}{1 + j\omega/100}$

$$Z = j\omega 0.01 + \frac{20(1 - j\omega/100)}{1 + \omega^2/10^4}$$

$$\text{Im}(Z) = 0 \longrightarrow \omega 0.01 - \frac{0.2\omega}{1 + \omega^2/10^4} = 0$$

$$\omega = \frac{20\omega}{1 + \omega^2/10^4} \longrightarrow 1 + \omega^2/10^4 = 20$$

Clearly, $\omega = \mathbf{435.9 \text{ rad/s}}$

P.P.14.10 $H(s) = \frac{V_o}{V_i} = \frac{R_2 \parallel sL}{R_1 + R_2 \parallel sL}, \quad s = j\omega$

$$H(s) = \frac{sR_2L}{R_1R_2 + sR_1L + sR_2L}$$

$$H(\omega) = \frac{j\omega R_2L}{R_1R_2 + j\omega L(R_1 + R_2)}$$

$$H(0) = 0$$

$$H(\omega) = \lim_{\omega \rightarrow \infty} \frac{jR_2L}{R_1R_2/\omega + jL(R_1 + R_2)} = \frac{R_2}{R_1 + R_2}$$

i.e. a **highpass filter**.

The corner frequency occurs when $H(\omega_c) = \frac{1}{\sqrt{2}} \cdot H(\infty)$.

$$\mathbf{H}(\omega) = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{j\omega L}{j\omega L + R_1 R_2 / (R_1 + R_2)} \right)$$

$$\mathbf{H}(\omega) = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{j\omega}{j\omega + k} \right), \quad \text{where } k = \frac{R_1 R_2}{(R_1 + R_2)L}$$

At the corner frequency,

$$\frac{1}{\sqrt{2}} \cdot \frac{R_2}{R_1 + R_2} = \frac{R_2}{R_1 + R_2} \cdot \left| \frac{j\omega_c}{j\omega_c + k} \right|$$

$$\frac{1}{\sqrt{2}} = \frac{\omega_c}{\sqrt{\omega_c^2 + k^2}} \longrightarrow \omega_c = k = \frac{R_1 R_2}{(R_1 + R_2)L}$$

Hence,
$$\mathbf{H}(\omega) = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{j\omega}{j\omega + \omega_c} \right)$$

and the corner frequency is

$$\omega_c = \frac{(100)(100)}{(100 + 100)(2 \times 10^{-3})} = \mathbf{25 \text{ krad/s}}$$

P.P.14.11 $B = 2\pi(20.3 - 20.1) \times 10^3 = 400\pi$

Assuming high Q,

$$\omega_0 = \frac{\omega_1 + \omega_2}{2} = \frac{(2\pi)(40.4 \times 10^3)}{2} = 40.4\pi \times 10^3 \text{ rad/s}$$

$$Q = \frac{\omega_0}{B} = \frac{40.4\pi \times 10^3}{400\pi} = \mathbf{101}$$

$$B = \frac{R}{L} \longrightarrow L = \frac{R}{B} = \frac{20 \times 10^3}{400\pi} = \mathbf{15.915 \text{ H}}$$

$$Q = \frac{1}{\omega_0 CR} \longrightarrow C = \frac{1}{\omega_0 QR}$$

$$C = \frac{1}{(40.4\pi \times 10^3)(101)(20 \times 10^3)} = \mathbf{3.9 \text{ pF}}$$

P.P.14.12 Given $H(\infty) = 5$ and $f_c = 2 \text{ kHz}$

$$\omega_c = 2\pi f_c = \frac{1}{R_i C_i}$$

$$R_i = \frac{1}{2\pi f_c C_i} = \frac{1}{(2\pi)(2 \times 10^3)(0.1 \times 10^{-3})}$$

$$R_i = 795.8 \cong \mathbf{800 \Omega}$$

$$H(\infty) = \frac{-R_f}{R_i} = -5 \longrightarrow R_f = 5R_i = 3,978 \cong \mathbf{4 k\Omega}$$

P.P.14.13 $Q = 10, \quad \omega_0 = 20 \text{ krad/s}$

$$B = \frac{\omega_0}{Q} = 2 \text{ krad/s}$$

$$\omega_1 = \omega_0 - \frac{B}{2} = 19 \text{ krad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 21 \text{ krad/s}$$

Since $\omega_1 = \frac{1}{C_2 R}$,

$$C_2 = \frac{1}{\omega_1 R} = \frac{1}{(19 \times 10^3)(10 \times 10^3)} = \mathbf{5.263 \text{ nF}}$$

$$C_1 = \frac{1}{\omega_2 R} = \frac{1}{(21 \times 10^3)(10 \times 10^3)} = \mathbf{4.762 \text{ nF}}$$

$$K = \frac{R_f}{R_i} = 5 \longrightarrow R_f = 5R_i = \mathbf{50 k\Omega}$$

P.P.14.14 $K_f = \frac{\omega'_c}{\omega_c} = \frac{2\pi \times 10^4}{1} = 2\pi \times 10^4$

$$C' = \frac{C}{K_m K_f} \longrightarrow K_m = \frac{C}{C' K_f} = \frac{1}{(15 \times 10^{-9})(2\pi \times 10^4)} = \frac{10^4}{3\pi}$$

$$R' = K_m R = \frac{10^4}{3\pi} (1) = 1.061 \text{ k}\Omega$$

$$L' = \frac{K_m}{K_f} L = \frac{10^4}{3\pi} \cdot \frac{2}{2\pi \times 10^4} = 33.77 \text{ mH}$$


Therefore,

$$R'_1 = R'_2 = \mathbf{1.061 k\Omega}$$


$$C_1 = C_2 = 15 \text{ nF}$$


$$L' = 33.77 \text{ mH}$$

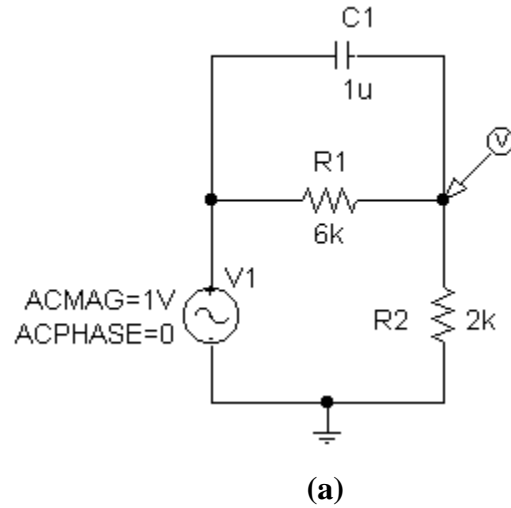P.P.14.15 The schematic is shown in Fig. (a).



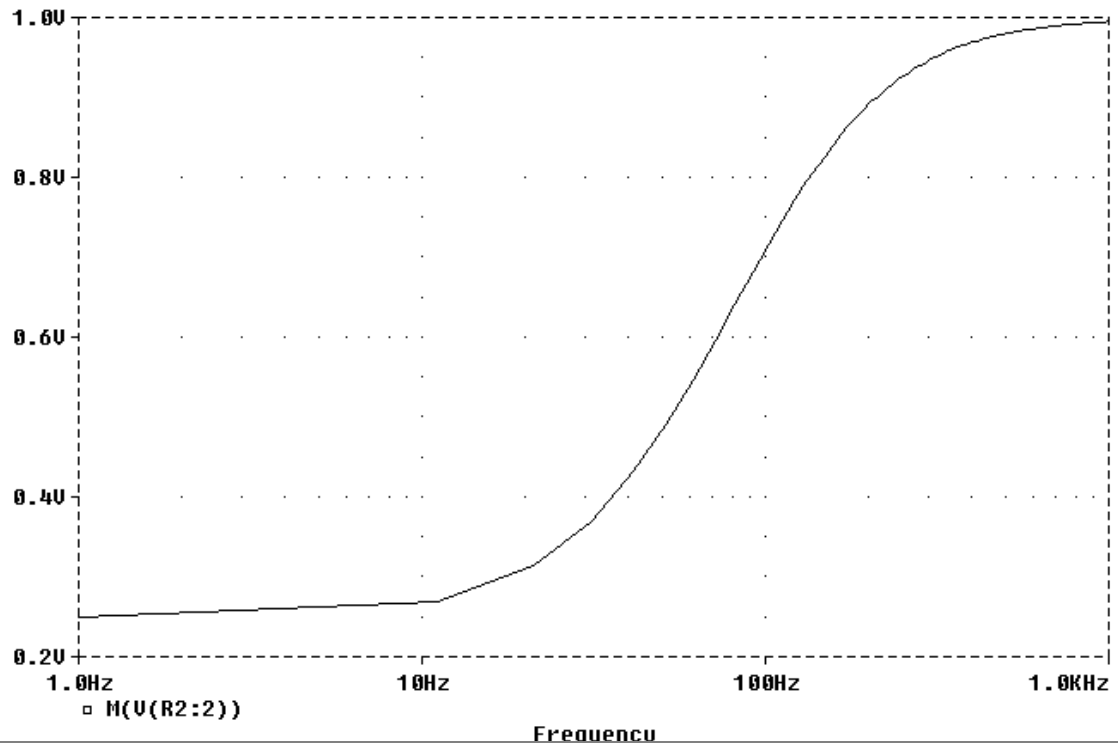
Use the **AC Sweep** option of the **Analysis Setup**. Choose a *Linear* sweep type with the following *Sweep Parameters* : *Total Pts* = 100, *Start Freq* = 1, and *End Freq* = 1K. After saving and simulating the circuit, we obtain **the magnitude and phase plots are shown in Figs. (b) and (c)**.



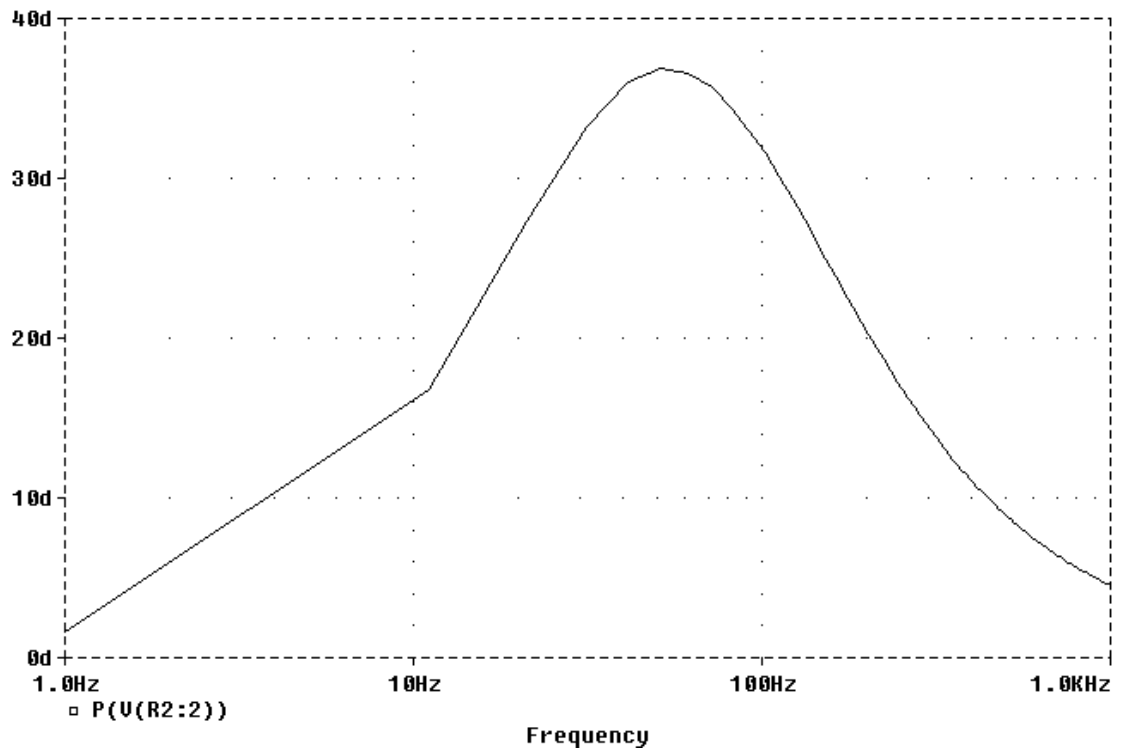

(c)

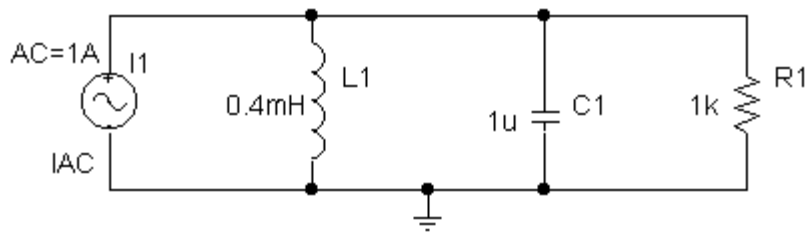
P.P.14.16 The schematic is shown in Fig. (a).




(a)

Use the **AC Sweep** option of the **Analysis Setup**. Choose a *Decade* sweep type with these *Sweep Parameters* : *Pts/Decade* = 20, *Start Freq* = 1K, and *End Freq* = 100K. Save and simulate the circuit.

For the magnitude plot, choose **DB()** from the **Analog Operators and Functions** list. Then, select the voltage **V(R1:1)** and OK. Another option would be to type **DB(V(R1:1))** as the **Trace Expression**. For the phase plot, choose **P()** from the **Analog Operators and Functions** list. Then, select the voltage **V(R1:1)** and OK. Another option would be to type **VP(R1:1)** as the **Trace Expression**. **The resulting magnitude and phase plots are shown in Figs. (b) and (c).**

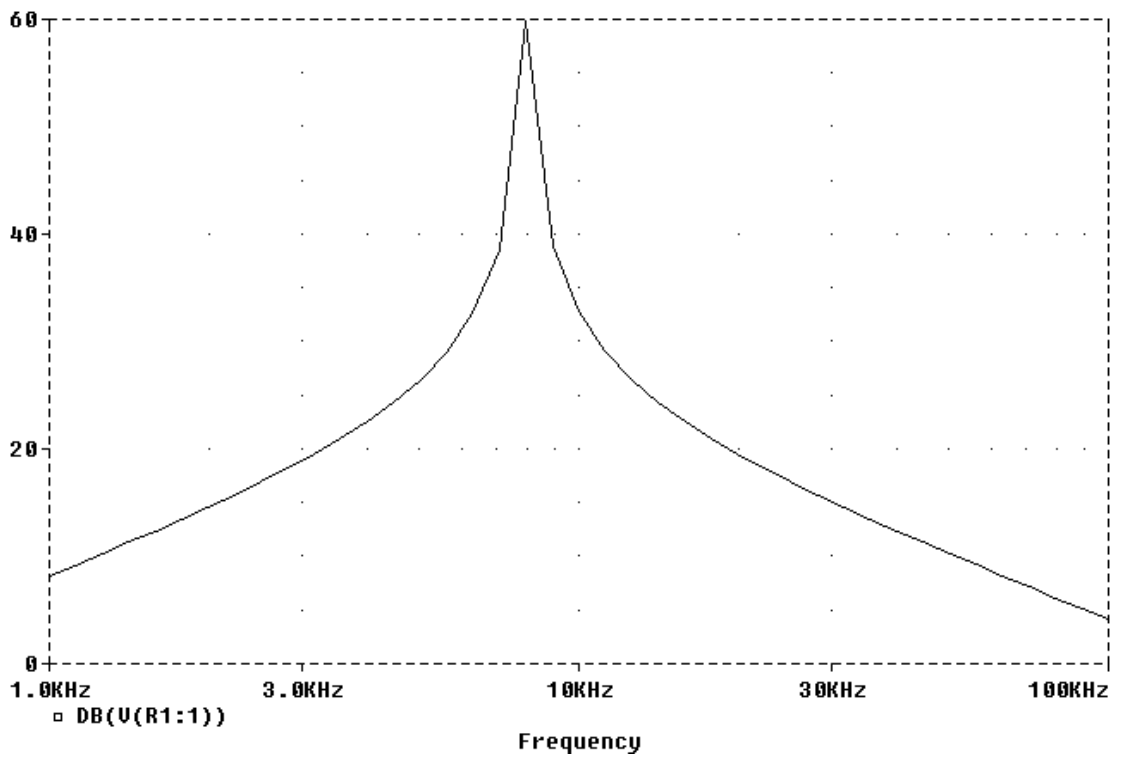

(b)

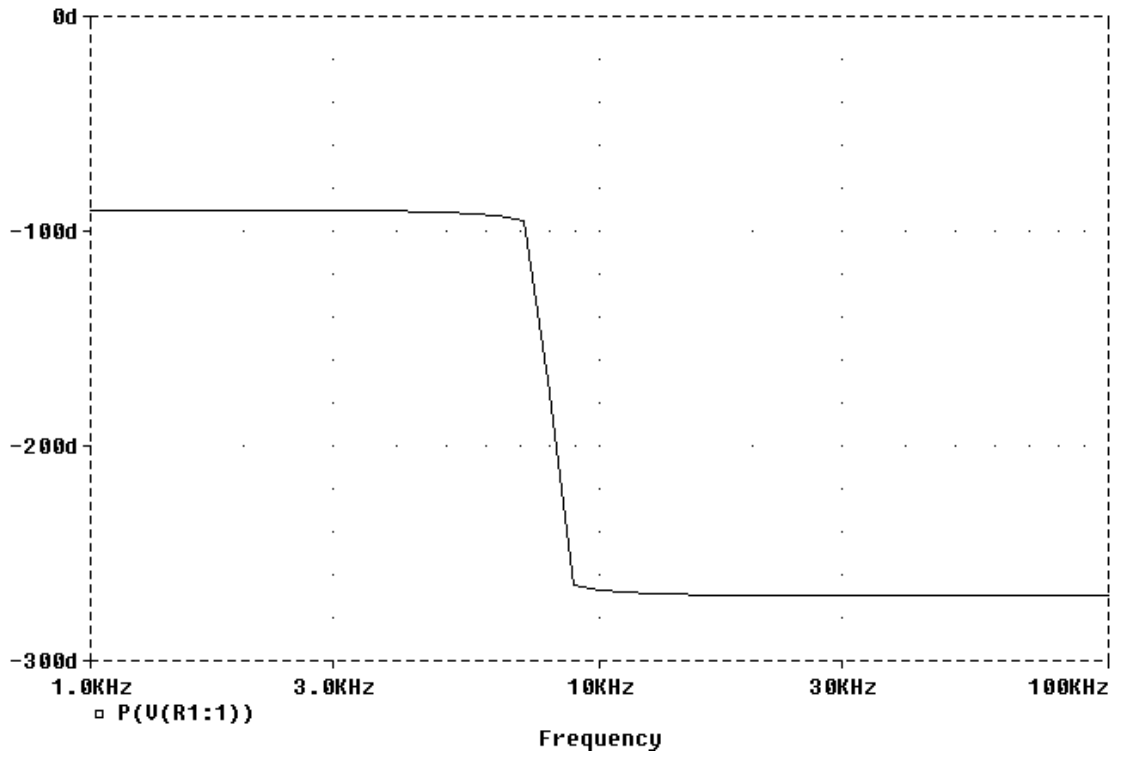

(c)

P.P.14.17 $\omega_0 = 2\pi f_0 = \frac{1}{\sqrt{LC}}$

or $C = \frac{1}{4\pi^2 f_0^2 L}$

For the high end of the band, $f_0 = 108 \text{ MHz}$

$$C_1 = \frac{1}{4\pi^2 (108^2 \times 10^{12})(4 \times 10^{-6})} = 0.543 \text{ pF}$$

For the low end of the band, $f_0 = 88 \text{ MHz}$

$$C_2 = \frac{1}{4\pi^2 (88^2 \times 10^{12})(4 \times 10^{-6})} = 0.818 \text{ pF}$$

Therefore, C must be adjustable and be in the range **0.543 pF to 0.818 pF** .

P.P.14.18

For BP_6 , $f_0 = 1336 \text{ Hz}$ and it passes frequencies in the range $1209 \text{ Hz} < f < 1477 \text{ Hz}$.

$$B = 2\pi(1477 - 1209) = 1683.9$$

$$L = \frac{R}{B} = \frac{600}{1683.9} = \mathbf{356 \text{ mH}}$$

$$C = \frac{1}{4\pi^2 f_0^2 L} = \frac{1}{4\pi^2 (1336)^2 (0.356)} = \mathbf{39.83 \text{ nF}}$$

P.P.14.19 $C = 10 \text{ } \mu\text{F}$ and $R_1 = R_2 = 8 \text{ } \Omega$

$$2\pi f_c = \frac{1}{R_1 C} \longrightarrow f_c = \frac{1}{2\pi R_1 C} = \frac{1}{(2\pi)(8)(10 \times 10^{-6})} = \mathbf{1.989 \text{ kHz}}$$

$$L = \frac{R_2}{2\pi f_c} = \frac{8}{(2\pi)(1.989 \times 10^3)} = \mathbf{0.64 \text{ mH}}$$