

CHAPTER 19

P.P.19.1 Comparing the network with that in Fig. 19.5, we observe that

$$\mathbf{z}_{12} = \mathbf{z}_{21} = 3 \Omega$$

$$\mathbf{z}_{22} - \mathbf{z}_{12} = 0 \text{ or } \mathbf{z}_{22} = \mathbf{z}_{12} = 3 \Omega$$

$$\mathbf{z}_{11} - \mathbf{z}_{12} = 4 \text{ or } \mathbf{z}_{11} = 4 + 3 = 7 \Omega$$

$$[\mathbf{z}] = \begin{bmatrix} 7 & 3 \\ 3 & 3 \end{bmatrix} \Omega$$

P.P.19.2 $\mathbf{V}_1 = 6\mathbf{I}_1 - j4\mathbf{I}_2 \quad (1)$

$$\mathbf{V}_2 = -j4\mathbf{I}_1 + 8\mathbf{I}_2 \quad (2)$$

But $\mathbf{V}_2 = 0$

and $2\angle 30^\circ = \mathbf{V}_1 + 2\mathbf{I}_1 \longrightarrow \mathbf{V}_1 = 2\angle 30^\circ - 2\mathbf{I}_1$

Substituting these into (1) and (2),

$$2\angle 30^\circ - 2\mathbf{I}_1 = 6\mathbf{I}_1 - j4\mathbf{I}_2$$

$$2\angle 30^\circ = 8\mathbf{I}_1 - j4\mathbf{I}_2 \quad (3)$$

$$0 = -j4\mathbf{I}_1 + 8\mathbf{I}_2$$

$$\mathbf{I}_1 = -j2\mathbf{I}_2 \quad (4)$$


Substituting (4) into (3),

$$2\angle 30^\circ = -j16\mathbf{I}_2 - j4\mathbf{I}_2 = -j20\mathbf{I}_2$$

$$\mathbf{I}_2 = \frac{2\angle 30^\circ}{20\angle -90^\circ} = 100\angle 120^\circ \text{ mA}$$

$$\mathbf{I}_1 = -j2\mathbf{I}_2 = 200\angle 30^\circ \text{ mA}$$

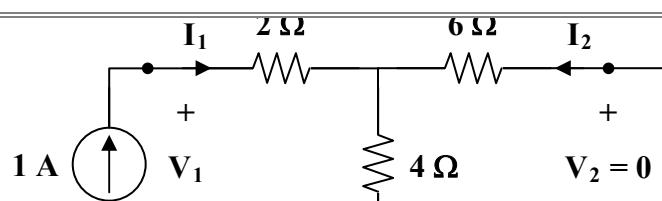P.P.19.3 Consider the circuit in Fig. (a) for \mathbf{y}_{11} and \mathbf{y}_{21} .



$$\mathbf{V}_1 = [2 + (4 \times 6 / (4+6))] \mathbf{I}_1 = 4.4 \mathbf{I}_1$$


$$\mathbf{y}_{11} = (\mathbf{I}_1 / \mathbf{V}_1) = 1 / 4.4 = \mathbf{0.2273 S}$$

By current division,

$$\mathbf{I}_2 = \frac{-4}{10} \mathbf{I}_1 = -0.4 \mathbf{I}_1$$

$$\mathbf{y}_{21} = \frac{\mathbf{I}_2}{\mathbf{V}_1} = -0.4 \mathbf{I}_1 / (4.4 \mathbf{I}_1) = -\mathbf{0.09091 S}$$

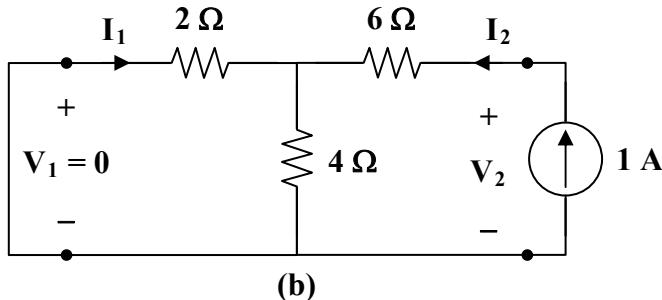For \mathbf{y}_{12} and \mathbf{y}_{22} , consider the circuit in Fig. (b).



$$\mathbf{V}_2 = [6 + (4 \times 2 / (4+2))] \mathbf{I}_2 = 7.333 \mathbf{I}_2$$

$$\mathbf{y}_{22} = \frac{\mathbf{I}_2}{\mathbf{V}_2} = 1 / 7.333 = \mathbf{0.13636 S}$$

By current division,


$$\mathbf{I}_1 = [-4 / (4+2)] \mathbf{I}_2 = -(2/3) \mathbf{I}_2$$

$$\mathbf{y}_{12} = \frac{\mathbf{I}_1}{\mathbf{V}_2} = -(2/3) \mathbf{I}_2 / 7.333 \mathbf{I}_2 = -\mathbf{0.09091 S}$$

Therefore,

$$[\mathbf{y}] = \begin{bmatrix} 227.3 & -90.91 \\ -90.91 & 136.36 \end{bmatrix} mS$$

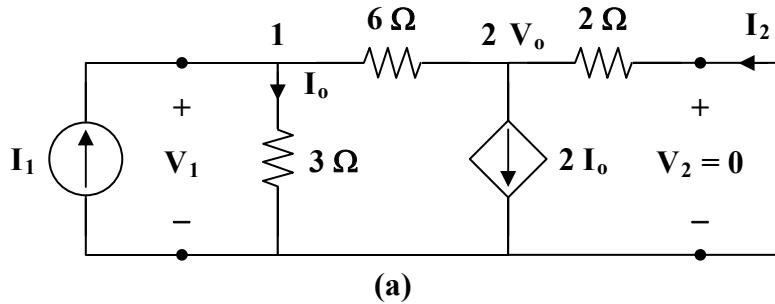P.P.19.4 Consider the circuit in Fig (a).



(a)

At node 1,

$$\begin{aligned} \mathbf{I}_1 &= \frac{\mathbf{V}_1}{3} + \frac{\mathbf{V}_1 - \mathbf{V}_o}{6} \\ 6\mathbf{I}_1 &= 3\mathbf{V}_1 - \mathbf{V}_o \end{aligned} \quad (1)$$

At node 2,

$$\frac{\mathbf{V}_1 - \mathbf{V}_o}{6} + \mathbf{I}_2 = 2\mathbf{I}_o = \frac{2}{3}\mathbf{V}_1$$

But $\mathbf{I}_2 = \frac{0 - \mathbf{V}_o}{2} = \frac{-\mathbf{V}_o}{2}$

Hence, $\frac{\mathbf{V}_1 - \mathbf{V}_o}{6} - \frac{\mathbf{V}_o}{2} = \frac{2}{3}\mathbf{V}_1 \longrightarrow \mathbf{V}_1 = \frac{-4}{3}\mathbf{V}_o$ (2)


From (1) and (2),

$$6\mathbf{I}_1 = -4\mathbf{V}_o - \mathbf{V}_o = -5\mathbf{V}_o \longrightarrow \mathbf{I}_1 = \frac{-5}{6}\mathbf{V}_o$$

Thus, $\mathbf{y}_{11} = \frac{\mathbf{I}_1}{\mathbf{V}_1} = \frac{(-5/6)\mathbf{V}_o}{(-4/3)\mathbf{V}_o} = \frac{5}{8} = 0.625 \text{ S}$

$$\mathbf{y}_{21} = \frac{\mathbf{I}_2}{\mathbf{V}_1} = \frac{(-1/2)\mathbf{V}_o}{(-4/3)\mathbf{V}_o} = \frac{3}{8} = 0.375 \text{ S}$$

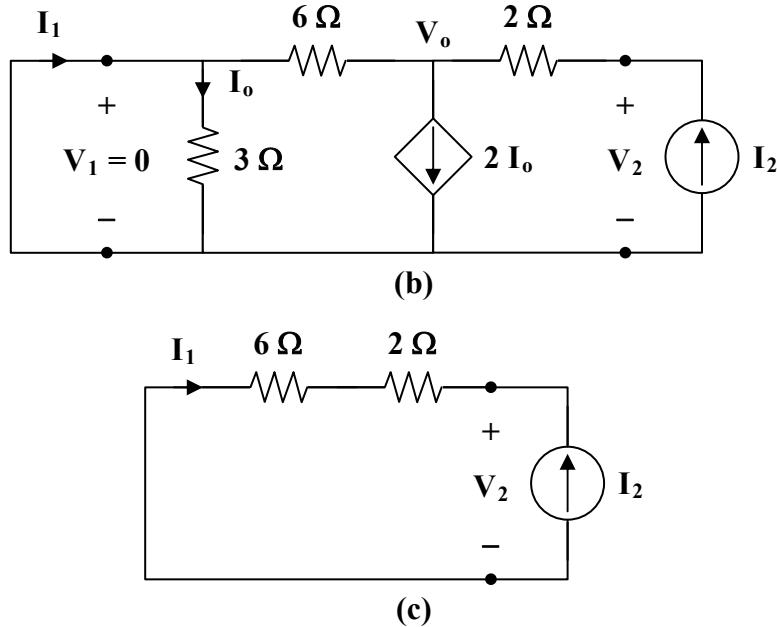Consider the circuit in Fig. (b). The 3- Ω resistor is short-circuited so that $I_o = 0$. Consequently, the circuit is equivalent to that shown in Fig.(c).



$$V_2 = 8I_2, \quad I_1 = -I_2$$


$$y_{22} = \frac{I_2}{V_2} = \frac{1}{8} = 0.125 \text{ S}$$

$$y_{12} = \frac{I_1}{V_2} = \frac{-I_2}{8I_2} = -0.125 \text{ S}$$

Therefore,

$$[y] = \begin{bmatrix} 0.625 & -0.125 \\ 0.375 & 0.125 \end{bmatrix} \text{S} \text{ or } \begin{bmatrix} 625 & -125 \\ 375 & 125 \end{bmatrix} \text{mS}$$

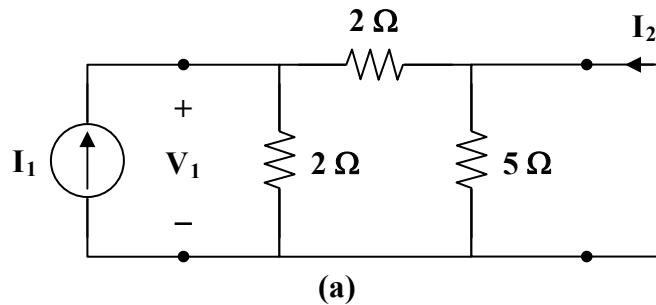P.P.19.5 To find h_{11} and h_{21} , we use the circuit in Fig. (a). Note that the 5- Ω resistor is short-circuited.




$$V_1 = [2x3/(2+3)]I_1 = 1.2I_1$$

$$h_{11} = \frac{V_1}{I_1} = 1.2 \Omega$$

$$-I_2 = \frac{2}{2+3}I_1 = 0.4I_1 = (4/(4+6))I_1 = 0.4I_1$$

$$h_{21} = \frac{I_2}{I_1} = -0.4$$

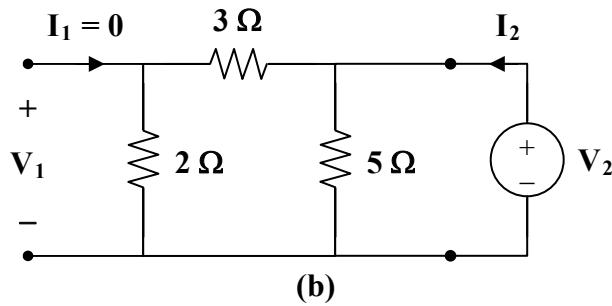To get h_{12} and h_{22} , we use the circuit in Fig. (b).



$$V_1 = [2/(2+3)]V_1 = 0.4V_1$$

$$h_{12} = \frac{V_1}{V_2} = 0.4$$


$$V_2 = [5x5/(5+5)]I_2 = 2.5I_2$$

$$h_{22} = \frac{I_2}{V_2} = \frac{1}{2.5} = 0.4 S$$

Therefore,

$$[h] = \begin{bmatrix} 1.2 \Omega & 0.4 \\ -0.4 & 400 mS \end{bmatrix}$$

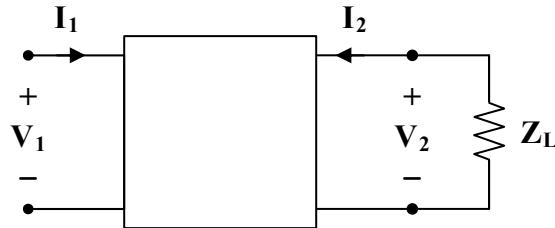P.P.19.6 Our goal is to get $\mathbf{Z}_{\text{in}} = \mathbf{V}_1 / \mathbf{I}_1$.



$$V_1 = h_{11} I_1 + h_{12} V_2 \quad (1)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad (2)$$

But $V_2 = -Z_L I_2$

Substituting this equation into (1) and (2),

$$I_2 = h_{21} I_1 - Z_L h_{22} I_2 \longrightarrow I_2 = \frac{h_{21} I_1}{1 + Z_L h_{22}}$$


$$V_2 = -Z_L I_2 = \frac{-Z_L h_{21} I_1}{1 + Z_L h_{22}}$$

$$V_1 = h_{11} I_1 - \frac{Z_L h_{12} h_{21} I_1}{1 + Z_L h_{22}}$$

$$\mathbf{Z}_{\text{in}} = \frac{\mathbf{V}_1}{\mathbf{I}_1} = h_{11} - \frac{Z_L h_{12} h_{21}}{1 + Z_L h_{22}}$$

$$\mathbf{Z}_{\text{in}} = 2000 - \frac{(50 \times 10^3)(10^{-4})(100)}{1 + (50 \times 10^3)(10^{-5})} = 1.6667 \text{ k}\Omega$$

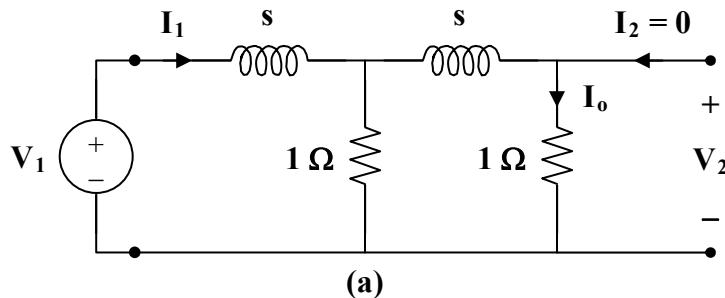P.P.19.7 We get \mathbf{g}_{11} and \mathbf{g}_{21} using the circuit in Fig. (a).



$$V_1 = [s + 1 \parallel (s + 1)] I_1$$

$$\frac{\mathbf{V}_1}{\mathbf{I}_1} = s + \frac{s+1}{s+2} = \frac{s^2 + 3s + 1}{s+2}$$

$$\mathbf{g}_{11} = \frac{\mathbf{I}_1}{\mathbf{V}_1} = \frac{s+2}{s^2 + 3s + 1}$$


By current division,

$$\mathbf{I}_o = \frac{1}{s+2} \mathbf{I}_1 = \frac{\mathbf{V}_1}{s^2 + 3s + 1}$$

$$\mathbf{V}_2 = \mathbf{I}_o = \frac{\mathbf{V}_1}{s^2 + 3s + 1}$$

$$\mathbf{g}_{21} = \frac{\mathbf{V}_2}{\mathbf{V}_1} = \frac{1}{s^2 + 3s + 1}$$

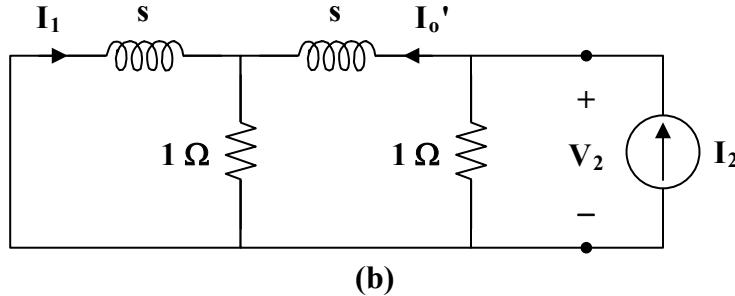We obtain \mathbf{g}_{12} and \mathbf{g}_{22} using the circuit in Fig. (b).



(b)

$$\mathbf{V}_2 = [1 \parallel (s+1 \parallel s)] \mathbf{I}_2 = \left[1 \parallel \left(s + \frac{s}{s+1} \right) \right] \mathbf{I}_2$$

$$\frac{\mathbf{V}_2}{\mathbf{I}_2} = 1 \parallel \frac{s^2 + 2s}{s+1} = \frac{s+1}{1 + \frac{s^2 + 2s}{s+1}} = \frac{s(s+2)}{s^2 + 3s + 1}$$

$$\mathbf{g}_{22} = \frac{\mathbf{V}_2}{\mathbf{I}_2} = \frac{s(s+2)}{s^2 + 3s + 1}$$

By current division,

$$\mathbf{I}_1 = \frac{-1}{s+1} \mathbf{I}_o'$$

and

$$\mathbf{I}_o' = \frac{1}{1 + \frac{s^2 + 2s}{s+1}} \mathbf{I}_2 = \frac{s+1}{s^2 + 3s + 1} \mathbf{I}_2$$


$$\mathbf{I}_1 = \frac{-1}{s^2 + 3s + 1} \mathbf{I}_2$$

$$\mathbf{g}_{12} = \frac{\mathbf{I}_1}{\mathbf{I}_2} = \frac{-1}{s^2 + 3s + 1}$$

Therefore,

$$[\mathbf{g}] = \begin{bmatrix} \frac{s+2}{s^2 + 3s + 1} & \frac{-1}{s^2 + 3s + 1} \\ \frac{1}{s^2 + 3s + 1} & \frac{s(s+2)}{s^2 + 3s + 1} \end{bmatrix}$$

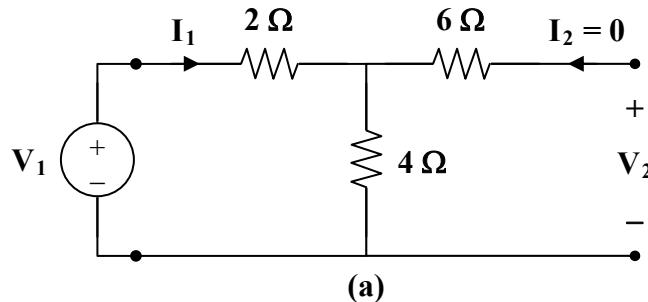
P.P.19.8 To get **A** and **C**, we use the circuit in Fig. (a).



$$\mathbf{A} = \mathbf{V}_1 / \mathbf{V}_2 = (2+4)\mathbf{I}_1 / (4\mathbf{I}_1) = 1.5$$

$$\mathbf{C} = \mathbf{I}_1 / \mathbf{V}_2 = \mathbf{I}_1 / (4\mathbf{I}_1) = 0.25 \text{ S}$$

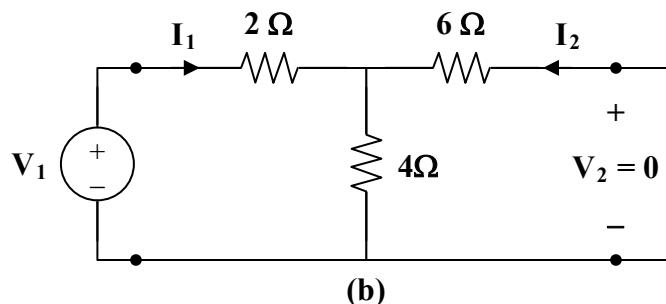To get **B** and **D**, we use the circuit in Fig. (b).



$$\mathbf{I}_2 = \frac{-4}{10} \mathbf{I}_1 \longrightarrow \mathbf{D} = \frac{-\mathbf{I}_1}{\mathbf{I}_2} = \frac{10}{4} = 2.5$$

Also,

$$\mathbf{V}_1 = [2 + (4 \times 6 / (4 + 6))] \mathbf{I}_1 = 4.4 \mathbf{I}_1$$

$$\mathbf{B} = -\mathbf{V}_1 / \mathbf{I}_2 = -4.4 \mathbf{I}_1 / (-0.4 \mathbf{I}_1) = 11 \Omega$$

Therefore,

$$[\mathbf{T}] = \begin{bmatrix} 1.5 & 11\Omega \\ 250\text{ mS} & 2.5 \end{bmatrix}$$

P.P.19.9 From Eq. (19.22),

$$\mathbf{V}_1 = 5\mathbf{V}_2 - 10\mathbf{I}_2 \quad (1)$$

$$\mathbf{I}_1 = 0.4\mathbf{V}_2 - \mathbf{I}_2 \quad (2)$$

At the output port, $\mathbf{V}_2 = -10\mathbf{I}_2$. At the input port, $\mathbf{V}_1 = 14 - 2\mathbf{I}_1$.

Substituting these into (1) and (2),

$$\begin{aligned} 14 - 2\mathbf{I}_1 &= -50\mathbf{I}_2 - 10\mathbf{I}_2 \\ 14 &= 2\mathbf{I}_1 - 60\mathbf{I}_2 \end{aligned} \quad (3)$$

$$\mathbf{I}_1 = -4\mathbf{I}_2 - \mathbf{I}_2$$

$$\mathbf{I}_1 = -5\mathbf{I}_2 \quad (4)$$

Substituting (4) into (3),

$$14 = -10\mathbf{I}_2 - 60\mathbf{I}_2$$

$$\mathbf{I}_2 = \frac{-14}{70} = -0.2 \text{ A}$$

$$\mathbf{I}_1 = (-5)(-0.2) = 1 \text{ A}$$

P.P.19.10

$$[\mathbf{Z}] = \begin{bmatrix} 6 & 4 \\ 4 & 6 \end{bmatrix} \quad \Delta_z = 36 - 16 = 20$$

$$\mathbf{Z}_{11} = 6 = \mathbf{Z}_{22} \quad \mathbf{Z}_{12} = \mathbf{Z}_{21} = 4$$

From Table 19.1,

$$\mathbf{y}_{11} = \frac{\mathbf{Z}_{22}}{\Delta_z} = \frac{6}{20} = 0.3 \text{ S} \quad \mathbf{y}_{12} = \frac{-\mathbf{Z}_{12}}{\Delta_z} = \frac{-4}{20} = -0.2 \text{ S}$$

$$\mathbf{y}_{21} = \frac{-\mathbf{Z}_{21}}{\Delta_z} = -0.2 \text{ S} \quad \mathbf{y}_{22} = \frac{\mathbf{Z}_{11}}{\Delta_z} = 0.3 \text{ S}$$

$$\mathbf{A} = \frac{\mathbf{Z}_{11}}{\mathbf{Z}_{21}} = \frac{6}{4} = 1.5 \quad \mathbf{B} = \frac{\Delta_z}{\mathbf{Z}_{21}} = \frac{20}{4} = 5 \Omega$$

$$\mathbf{C} = \frac{1}{\mathbf{Z}_{21}} = \frac{1}{4} = 0.25 \text{ S} \quad \mathbf{D} = \frac{\mathbf{Z}_{22}}{\mathbf{Z}_{21}} = \frac{6}{4} = 1.5$$

Therefore,

$$[\mathbf{y}] = \begin{bmatrix} 0.3 & -0.2 \\ -0.2 & 0.3 \end{bmatrix} S \quad [\mathbf{T}] = \begin{bmatrix} 1.5 & 5\Omega \\ 0.25S & 1.5 \end{bmatrix}$$