

CONTENTS

Chapter 1

Introduction 1

- 1.1** Power Electronics 1
- 1.2** Converter Classification 1
- 1.3** Power Electronics Concepts 3
- 1.4** Electronic Switches 5
 - The Diode* 6
 - Thyristors* 7
 - Transistors* 8
- 1.5** Switch Selection 11
- 1.6** Spice, PSpice, and Capture 13
- 1.7** Switches in PSpice 14
 - The Voltage-Controlled Switch* 14
 - Transistors* 16
 - Diodes* 17
 - Thyristors (SCRs)* 18
 - Convergence Problems in PSpice* 18
- 1.8** Bibliography 19
 - Problems 20

- 2.5** Effective Values: RMS 34
- 2.6** Apparent Power and Power Factor 42
 - Apparent Power S* 42
 - Power Factor* 43
- 2.7** Power Computations for Sinusoidal AC Circuits 43
- 2.8** Power Computations for Nonsinusoidal Periodic Waveforms 44
 - Fourier Series* 45
 - Average Power* 46
 - Nonsinusoidal Source and Linear Load* 46
 - Sinusoidal Source and Nonlinear Load* 48
- 2.9** Power Computations Using PSpice 51
- 2.10** Summary 58
- 2.11** Bibliography 59
 - Problems 59

Chapter 2

Power Computations 21

- 2.1** Introduction 21
- 2.2** Power and Energy 21
 - Instantaneous Power* 21
 - Energy* 22
 - Average Power* 22
- 2.3** Inductors and Capacitors 25
- 2.4** Energy Recovery 27

Chapter 3

Half-Wave Rectifiers 65

- 3.1** Introduction 65
- 3.2** Resistive Load 65
 - Creating a DC Component*
 - Using an Electronic Switch* 65
- 3.3** Resistive-Inductive Load 67
- 3.4** PSpice Simulation 72
 - Using Simulation Software for Numerical Computations* 72

- 3.5** *RL-Source Load* 75
Supplying Power to a DC Source from an AC Source 75
- 3.6** *Inductor-Source Load* 79
Using Inductance to Limit Current 79
- 3.7** *The Freewheeling Diode* 81
Creating a DC Current 81
Reducing Load Current Harmonics 86
- 3.8** *Half-Wave Rectifier With a Capacitor Filter* 88
Creating a DC Voltage from an AC Source 88
- 3.9** *The Controlled Half-Wave Rectifier* 94
Resistive Load 94
RL Load 96
RL-Source Load 98
- 3.10** *PSpice Solutions For Controlled Rectifiers* 100
Modeling the SCR in PSpice 100
- 3.11** *Commutation* 103
The Effect of Source Inductance 103
- 3.12** *Summary* 105
- 3.13** *Bibliography* 106
Problems 106
- 4.3** *Capacitance Output Filter* 122
Voltage Doublers 125
LC Filtered Output 126
- 4.3** *Controlled Full-Wave Rectifiers* 131
Resistive Load 131
RL Load, Discontinuous Current 133
RL Load, Continuous Current 135
PSpice Simulation of Controlled Full-Wave Rectifiers 139
Controlled Rectifier with RL-Source Load 140
Controlled Single-Phase Converter Operating as an Inverter 142
- 4.4** *Three-Phase Rectifiers* 144
- 4.5** *Controlled Three-Phase Rectifiers* 149
Twelve-Pulse Rectifiers 151
The Three-Phase Converter Operating as an Inverter 154
- 4.6** *DC Power Transmission* 156
- 4.7** *Commutation: The Effect of Source Inductance* 160
Single-Phase Bridge Rectifier 160
Three-Phase Rectifier 162
- 4.8** *Summary* 163
- 4.9** *Bibliography* 164
Problems 164

Chapter 4

Full-Wave Rectifiers 111

- 4.1** *Introduction* 111
- 4.2** *Single-Phase Full-Wave Rectifiers* 111
The Bridge Rectifier 111
The Center-Tapped Transformer Rectifier 114
Resistive Load 115
RL Load 115
Source Harmonics 118
PSpice Simulation 119
RL-Source Load 120

Chapter 5

AC Voltage Controllers 171

- 5.1** *Introduction* 171
- 5.2** *The Single-Phase AC Voltage Controller* 171
Basic Operation 171
Single-Phase Controller with a Resistive Load 173
Single-Phase Controller with an RL Load 177
PSpice Simulation of Single-Phase AC Voltage Controllers 180

- 5.3 Three-Phase Voltage Controllers 183
 - Y-Connected Resistive Load* 183
 - Y-Connected RL Load* 187
 - Delta-Connected Resistive Load* 189
- 5.4 Induction Motor Speed Control 191
- 5.5 Static VAR Control 191
- 5.6 Summary 192
- 5.7 Bibliography 193
 - Problems 193

Chapter 6

DC-DC Converters 196

- 6.1 Linear Voltage Regulators 196
- 6.2 A Basic Switching Converter 197
- 6.3 The Buck (Step-Down) Converter 198
 - Voltage and Current Relationships* 198
 - Output Voltage Ripple* 204
 - Capacitor Resistance—The Effect on Ripple Voltage* 206
 - Synchronous Rectification for the Buck Converter* 207
- 6.4 Design Considerations 207
- 6.5 The Boost Converter 211
 - Voltage and Current Relationships* 211
 - Output Voltage Ripple* 215
 - Inductor Resistance* 218
- 6.6 The Buck-Boost Converter 221
 - Voltage and Current Relationships* 221
 - Output Voltage Ripple* 225
- 6.7 The Ćuk Converter 226
- 6.8 The Single-Ended Primary Inductance Converter (SEPIC) 231
- 6.9 Interleaved Converters 237
- 6.10 Nonideal Switches and Converter Performance 239
 - Switch Voltage Drops* 239
 - Switching Losses* 240
- 6.11 Discontinuous-Current Operation 241
 - Buck Converter with Discontinuous Current* 241
 - Boost Converter with Discontinuous Current* 244
- 6.12 Switched-Capacitor Converters 247
 - The Step-Up Switched-Capacitor Converter* 247
 - The Inverting Switched-Capacitor Converter* 249
 - The Step-Down Switched-Capacitor Converter* 250
- 6.13 PSpice Simulation of DC-DC Converters 251
 - A Switched PSpice Model* 252
 - An Averaged Circuit Model* 254
- 6.14 Summary 259
- 6.15 Bibliography 259
 - Problems 260

Chapter 7

DC Power Supplies 265

- 7.1 Introduction 265
- 7.2 Transformer Models 265
- 7.3 The Flyback Converter 267
 - Continuous-Current Mode* 267
 - Discontinuous-Current Mode in the Flyback Converter* 275
 - Summary of Flyback Converter Operation* 277
- 7.4 The Forward Converter 277
 - Summary of Forward Converter Operation* 283
- 7.5 The Double-Ended (Two-Switch) Forward Converter 285
- 7.6 The Push-Pull Converter 287
 - Summary of Push-Pull Operation* 290
- 7.7 Full-Bridge and Half-Bridge DC-DC Converters 291

- 7.8 Current-Fed Converters 294
 - 7.9 Multiple Outputs 297
 - 7.10 Converter Selection 298
 - 7.11 Power Factor Correction 299
 - 7.12 PSpice Simulation of DC Power Supplies 301
 - 7.13 Power Supply Control 302
 - Control Loop Stability* 303
 - Small-Signal Analysis* 304
 - Switch Transfer Function* 305
 - Filter Transfer Function* 306
 - Pulse-Width Modulation Transfer Function* 307
 - Type 2 Error Amplifier with Compensation* 308
 - Design of a Type 2 Compensated Error Amplifier* 311
 - PSpice Simulation of Feedback Control* 315
 - Type 3 Error Amplifier with Compensation* 317
 - Design of a Type 3 Compensated Error Amplifier* 318
 - Manual Placement of Poles and Zeros in the Type 3 Amplifier* 323
 - 7.14 PWM Control Circuits 323
 - 7.15 The AC Line Filter 323
 - 7.16 The Complete DC Power Supply 325
 - 7.17 Bibliography 326
 - Problems 327
- Chapter 8**
- Inverters 331**
- 8.1 Introduction 331
 - 8.2 The Full-Bridge Converter 331
 - 8.3 The Square-Wave Inverter 333
 - 8.4 Fourier Series Analysis 337
 - 8.5 Total Harmonic Distortion 339
 - 8.6 PSpice Simulation of Square Wave Inverters 340
 - 8.7 Amplitude and Harmonic Control 342
 - 8.8 The Half-Bridge Inverter 346
 - 8.9 Multilevel Inverters 348
 - Multilevel Converters with Independent DC Sources* 349
 - Equalizing Average Source Power with Pattern Swapping* 353
 - Diode-Clamped Multilevel Inverters* 354
 - 8.10 Pulse-Width-Modulated Output 357
 - Bipolar Switching* 357
 - Unipolar Switching* 358
 - 8.11 PWM Definitions and Considerations 359
 - 8.12 PWM Harmonics 361
 - Bipolar Switching* 361
 - Unipolar Switching* 365
 - 8.13 Class D Audio Amplifiers 366
 - 8.14 Simulation of Pulse-Width-Modulated Inverters 367
 - Bipolar PWM* 367
 - Unipolar PWM* 370
 - 8.15 Three-Phase Inverters 373
 - The Six-Step Inverter* 373
 - PWM Three-Phase Inverters* 376
 - Multilevel Three-Phase Inverters* 378
 - 8.16 PSpice Simulation of Three-Phase Inverters 378
 - Six-Step Three-Phase Inverters* 378
 - PWM Three-Phase Inverters* 378
 - 8.17 Induction Motor Speed Control 379
 - 8.18 Summary 382
 - 8.19 Bibliography 383
 - Problems 383

Chapter 9**Resonant Converters 387**

- 9.1** Introduction 387
- 9.2** A Resonant Switch Converter:
Zero-Current Switching 387
Basic Operation 387
Output Voltage 392
- 9.3** A Resonant Switch Converter:
Zero-Voltage Switching 394
Basic Operation 394
Output Voltage 399
- 9.4** The Series Resonant Inverter 401
Switching Losses 403
Amplitude Control 404
- 9.5** The Series Resonant
DC-DC Converter 407
Basic Operation 407
Operation for $\omega_s > \omega_o$ 407
Operation for $\omega_0/2 < \omega_s < \omega_0$ 413
Operation for $\omega_s < \omega_0/2$ 413
*Variations on the Series Resonant DC-DC
Converter* 414
- 9.6** The Parallel Resonant
DC-DC Converter 415
- 9.7** The Series-Parallel DC-DC
Converter 418
- 9.8** Resonant Converter Comparison 421
- 9.9** The Resonant DC Link Converter 422
- 9.10** Summary 426
- 9.11** Bibliography 426
Problems 427

Chapter 10**Drive Circuits, Snubber Circuits,
and Heat Sinks 431**

- 10.1** Introduction 431
- 10.2** MOSFET and IGBT Drive
Circuits 431
Low-Side Drivers 431
High-Side Drivers 433
- 10.3** Bipolar Transistor Drive
Circuits 437
- 10.4** Thyristor Drive Circuits 440
- 10.5** Transistor Snubber Circuits 441
- 10.6** Energy Recovery Snubber
Circuits 450
- 10.7** Thyristor Snubber Circuits 450
- 10.8** Heat Sinks and Thermal
Management 451
Steady-State Temperatures 451
Time-Varying Temperatures 454
- 10.9** Summary 457
- 10.10** Bibliography 457
Problems 458

**Appendix A Fourier Series for Some
Common Waveforms 461****Appendix B State-Space Averaging 467****Index 473**