

# Contents

Preface ix

## Chapter 1

### Diodes and the *pn* Junction 1

- 1.1 The Ideal Diode 3
- 1.2 Basic Diode Applications 10
- 1.3 Operational Amplifiers and Diode Applications 21
- 1.4 Semiconductors 25
- 1.5 The *pn* Junction in Equilibrium 34
- 1.6 Effect of External Bias on the SCL Parameters 39
- 1.7 The *pn* Diode Equation 43
- 1.8 The Reverse-Biased *pn* Junction 50
- 1.9 Forward-Biased Diode Characteristics 53
- 1.10 Dc Analysis of *pn* Diode Circuits 58
- 1.11 Ac Analysis of *pn* Diode Circuits 67
- 1.12 Breakdown-Region Operation 76
- 1.13 Dc Power Supplies 84
  - Appendix 1A: SPICE Models for Diodes 90
  - References 93
  - Problems 93

## Chapter 2

### Bipolar Junction Transistors 109

- 2.1 Physical Structure of the BJT 112
- 2.2 Basic BJT Operation 117
- 2.3 The *i-v* Characteristics of BJTs 130
- 2.4 Operating Regions and BJT Models 137
- 2.5 The BJT as an Amplifier/Switch 150
- 2.6 Small-Signal Operation of the BJT 157
- 2.7 BJT Biasing for Amplifier Design 169
- 2.8 Basic Bipolar Voltage Amplifiers 177

- 2.9 Bipolar Voltage and Current Buffers 189
- Appendix 2A: SPICE Models for BJTs 201
- References 203
- Problems 203

## Chapter 3

### MOS Field-Effect Transistors 221

- 3.1 Physical Structure of the MOSFET 224
- 3.2 The Threshold Voltage  $V_t$  226
- 3.3 The *n*-Channel Characteristic 237
- 3.4 The *i-v* Characteristics of MOSFETs 247
- 3.5 MOSFETs in Resistive Dc Circuits 259
- 3.6 The MOSFET as an Amplifier/Switch 273
- 3.7 Small-Signal Operation of the MOSFET 282
- 3.8 Basic MOSFET Voltage Amplifiers 290
- 3.9 MOSFET Voltage and Current Buffers 300
- 3.10 The CMOS Inverter/Amplifier 306
  - Appendix 3A: SPICE Models for MOSFETs 314
  - References 316
  - Problems 316

## Chapter 4

### Building Blocks for Analog Integrated Circuits 332

- 4.1 Design Considerations in Monolithic Circuits 334
- 4.2 BJT Characteristics and Models Revisited 342
- 4.3 MOSFET Characteristics and Models Revisited 357
- 4.4 Darlington, Cascode, and Cascade Configurations 371
- 4.5 Differential Pairs 386

- 4.6 Common-Mode Rejection Ratio in Differential Pairs** 396
- 4.7 Input Offset Voltage/Current in Differential Pairs** 404
- 4.8 Current Mirrors** 409
- 4.9 Differential Pairs with Active Loads** 421
- 4.10 Bipolar Output Stages** 432
- 4.11 CMOS Output Stages** 440
  - Appendix 4A: Editing SPICE Netlists 445
  - References 446
  - Problems 446

## Chapter 5

---

### Analog Integrated Circuits 472

- 5.1 The  $\mu$ A741 Operational Amplifier** 473
- 5.2 The Two-Stage CMOS Operational Amplifier** 487
- 5.3 The Folded-Cascode CMOS Operational Amplifier** 495
- 5.4 Voltage Comparators** 501
- 5.5 Current and Voltage References** 510
- 5.6 Current-Mode Integrated Circuits** 521
- 5.7 Fully Differential Operational Amplifiers** 532
- 5.8 Switched-Capacitor Circuits** 541
  - Appendix 5A: SPICE Macro-Models 553
  - References 554
  - Problems 554

## Chapter 6

---

### Frequency and Time Responses 564

- 6.1 High-Frequency BJT Model** 566
- 6.2 High-Frequency MOSFET Model** 574
- 6.3 Frequency Response of CE/CS Amplifiers** 581
- 6.4 Frequency Response of Differential Amplifiers** 592
- 6.5 Bipolar Voltage and Current Buffers** 599

- 6.6 MOS Voltage and Current Buffers** 606
- 6.7 Open-Circuit Time-Constant (OCTC) Analysis** 612
- 6.8 Frequency Response of Cascode Amplifiers** 623
- 6.9 Frequency and Transient Responses of Op Amps** 629
- 6.10 Diode Switching Transients** 639
- 6.11 BJT Switching Transients** 644
- 6.12 Transient Response of CMOS Gates and Voltage Comparators** 652
  - Appendix 6A: Transfer Functions and Bode Plots 665
  - References 672
  - Problems 672

## Chapter 7

---

### Feedback, Stability, and Noise 685

- 7.1 Negative-Feedback Basics** 688
- 7.2 Effect of Feedback on Distortion, Noise, and Bandwidth** 695
- 7.3 Feedback Topologies and Closed-Loop I/O Resistances** 704
- 7.4 Practical Configurations and the Effect of Loading** 714
- 7.5 Return Ratio Analysis** 741
- 7.6 Blackman's Impedance Formula and Injection Methods** 755
- 7.7 Stability in Negative-Feedback Circuits** 762
- 7.8 Dominant-Pole Compensation** 772
- 7.9 Frequency Compensation of Monolithic Op Amps** 780
- 7.10 Noise** 795
  - References 811
  - Problems 811

## Index 827