



CONTENTS

| | |
|--|-----------|
| <i>About the Author</i> | ii |
| <i>Foreword</i> | vi |
| <i>Preface</i> | vii |
| 1. INTRODUCTION | 1 |
| 1.1 Charge | 1 |
| 1.2 Voltage or Potential | 4 |
| 1.3 Basic Circuit | 6 |
| 1.4 Units and Symbols | 7 |
| <i>Rules to Use SI Prefixes</i> | 8 |
| <i>Guidelines for Using SI Units</i> | 8 |
| 1.5 Basics of Experimentation | 10 |
| <i>General Instructions and Precautions</i> | 10 |
| 2. OHM'S LAW | 14 |
| 2.1 OHM'S Law | 14 |
| 2.2 Resistance | 15 |
| 2.3 Duality | 28 |
| 2.4 Conductors and Resistors | 28 |
| 2.5 Variation of Resistance with Temperature | 30 |
| <i>Additional solved examples</i> | 32 |
| <i>Summary</i> | 39 |
| <i>Check your understanding</i> | 40 |
| <i>Review questions</i> | 41 |
| <i>Multiple choice questions</i> | 41 |
| <i>Problems</i> | 42 |
| <i>Experimental exercise</i> | 47 |
| 3. NETWORK ANALYSIS | 50 |
| 3.1 Network Components | 50 |
| 3.2 Series and Parallel Combinations | 54 |
| 3.3 Energy Sources | 57 |
| 3.4 Combination of Sources | 62 |
| 3.5 Types of Sources | 66 |
| 3.6 Kirchhoff's Laws | 67 |
| 3.7 Loop-current Analysis | 72 |
| 3.8 Mesh Analysis | 75 |
| 3.9 Node-voltage Analysis | 80 |
| 3.10 Nodal Analysis | 83 |
| 3.11 Choice of Method of Analysis | 84 |
| <i>Additional solved examples</i> | 85 |
| <i>Summary</i> | 93 |

| | | |
|---|-----|------------|
| <i>Check your understanding</i> | 94 | |
| <i>Review questions</i> | 95 | |
| <i>Multiple choice questions</i> | 95 | |
| <i>Problems</i> | 96 | |
| <i>Experimental exercises</i> | 100 | |
| 4. NETWORK THEOREMS | | 104 |
| 4.1 Introduction | 104 | |
| 4.2 Superposition Theorem | 104 | |
| 4.3 Thevenin's Theorem | 108 | |
| 4.4 Norton's Theorem | 112 | |
| 4.5 Maximum Power Transfer Theorem | 113 | |
| 4.6 Millman's Theorem | 116 | |
| 4.7 Reciprocity Theorem | 116 | |
| 4.8 Tellegen's Theorem | 117 | |
| <i>Additional solved examples</i> | 119 | |
| <i>Summary</i> | 128 | |
| <i>Check your understanding</i> | 129 | |
| <i>Review questions</i> | 130 | |
| <i>Multiple choice questions</i> | 130 | |
| <i>Problems</i> | 131 | |
| <i>Experimental exercises</i> | 134 | |
| A1 <i>Supplementary Exercises</i> | | 141 |
| 5. ELECTROMAGNETISM | | 185 |
| 5.1 Introduction | 185 | |
| 5.2 Magnetic Field due to Electric Current | 185 | |
| 5.3 Force on Current-carrying Conductor | 188 | |
| 5.4 Torque Experienced by a Coil | 190 | |
| 5.5 Force between Parallel Conductors | 191 | |
| 5.6 Electromagnetic Induction | 192 | |
| 5.7 Methods of Producing Induced EMF | 194 | |
| 5.8 Dynamically Induced EMF | 194 | |
| 5.9 Electromagnetic Induction and Lorentz Force | 197 | |
| <i>Additional solved examples</i> | 200 | |
| <i>Summary</i> | 203 | |
| <i>Check your understanding</i> | 204 | |
| <i>Review questions</i> | 205 | |
| <i>Multiple choice questions</i> | 205 | |
| <i>Problems</i> | 207 | |
| 6. MAGNETIC CIRCUITS | | 208 |
| 6.1 Introduction | 208 | |
| 6.2 Magnetomotive Force (MMF) | 208 | |
| 6.3 Magnetic Circuit Theory | 210 | |
| <i>Additional solved examples</i> | 217 | |
| <i>Summary</i> | 222 | |
| <i>Check your understanding</i> | 223 | |
| <i>Review questions</i> | 224 | |
| <i>Multiple choice questions</i> | 224 | |
| <i>Problems</i> | 224 | |
| 7. SELF AND MUTUAL INDUCTANCES | | 227 |
| 7.1 Self Inductance | 227 | |

| | | |
|--|-----|------------|
| 7.2 Inductors | 230 | |
| 7.3 Mutual Inductance | 230 | |
| 7.4 Dot Convention | 233 | |
| 7.5 Coupled Coils in Series | 235 | |
| 7.6 Coupled Coils in Parallel | 237 | |
| 7.7 Energy Stored in Magnetic Field | 239 | |
| 7.8 Lifting Power of a Magnet | 240 | |
| <i>Additional solved examples</i> | 240 | |
| <i>Summary</i> | 243 | |
| <i>Check your understanding</i> | 244 | |
| <i>Review questions</i> | 245 | |
| <i>Multiple choice questions</i> | 245 | |
| <i>Problems</i> | 246 | |
| B1 Supplementary Exercises | | 249 |
| 8. DC TRANSIENTS | | 273 |
| 8.1 Introduction | 273 | |
| 8.2 The Simple <i>RI</i> Circuit | 274 | |
| 8.3 The Simple <i>RC</i> Circuit | 281 | |
| 8.4 DC-excited Single-capacitor <i>RC</i> and Single-inductor <i>RI</i> Circuits | 285 | |
| 8.5 <i>RC</i> Timers | 288 | |
| <i>Additional solved examples</i> | 288 | |
| <i>Summary</i> | 296 | |
| <i>Check your understanding</i> | 297 | |
| <i>Review questions</i> | 298 | |
| <i>Multiple choice questions</i> | 299 | |
| <i>Problems</i> | 299 | |
| 9. ALTERNATING VOLTAGE AND CURRENT | | 301 |
| 9.1 Introduction | 301 | |
| 9.2 Sinusoidal Functions—Terminology | 302 | |
| 9.3 Concept of Phasors | 310 | |
| 9.4 Algebraic Operations on Phasors | 312 | |
| 9.5 Mathematics of Complex Numbers | 314 | |
| 9.6 Power and Power Factor | 322 | |
| 9.7 Behaviour of <i>R</i> , <i>L</i> and <i>C</i> in Ac Circuits | 324 | |
| <i>Additional solved examples</i> | 330 | |
| <i>Summary</i> | 334 | |
| <i>Check your understanding</i> | 336 | |
| <i>Review questions</i> | 337 | |
| <i>Multiple choice questions</i> | 337 | |
| <i>Problems</i> | 338 | |
| 10. AC CIRCUITS | | 340 |
| 10.1 Series <i>RL</i> Circuit | 340 | |
| 10.2 Series <i>RC</i> Circuit | 343 | |
| 10.3 Complex Power | 344 | |
| 10.4 Parallel <i>RL</i> Circuit | 346 | |
| 10.5 Parallel <i>RC</i> Circuit | 346 | |
| 10.6 Series <i>RLC</i> Circuit | 348 | |
| 10.7 Parallel <i>RLC</i> Circuit | 350 | |
| <i>Additional solved examples</i> | 357 | |
| <i>Summary</i> | 357 | |

| | | | |
|------------|---|-----|------------|
| | <i>Check your understanding</i> | 357 | |
| | <i>Review questions</i> | 358 | |
| | <i>Multiple choice questions</i> | 359 | |
| | <i>Problems</i> | 360 | |
| | <i>Experimental exercises</i> | 362 | |
| 11. | RESONANCE IN AC CIRCUITS | | 372 |
| | 11.1 Introduction | 372 | |
| | 11.2 Series Resonant Circuit | 372 | |
| | 11.3 Different Aspects of Resonance | 374 | |
| | 11.4 Resonance Curve | 380 | |
| | 11.5 Parallel Resonant Circuit | 382 | |
| | 11.6 Comparison between Series and Parallel Resonance | 386 | |
| | <i>Additional solved examples</i> | 388 | |
| | <i>Summary</i> | 391 | |
| | <i>Check your understanding</i> | 393 | |
| | <i>Review questions</i> | 393 | |
| | <i>Multiple choice questions</i> | 394 | |
| | <i>Problems</i> | 395 | |
| 12. | THREE-PHASE CIRCUITS AND SYSTEMS | | 397 |
| | 12.1 Introduction | 397 | |
| | 12.2 Double-subscript Notation | 398 | |
| | 12.3 Concept of Three-phase Voltages | 399 | |
| | 12.4 Generation of Three-phase Voltages | 400 | |
| | 12.5 Three-phase Loads | 401 | |
| | 12.6 Star (Y) Connected Three-phase System | 402 | |
| | 12.7 Delta (Δ) Connected Three-phase System | 404 | |
| | 12.8 Voltages and Currents Relations in 3- ϕ Systems | 405 | |
| | 12.9 Power in Three-phase System with a Balanced Load | 412 | |
| | 12.10 Comparison between Two Three-phase Systems | 413 | |
| | 12.11 Measurement of Power | 414 | |
| | <i>Additional solved examples</i> | 418 | |
| | <i>Summary</i> | 426 | |
| | <i>Check your understanding</i> | 427 | |
| | <i>Review questions</i> | 427 | |
| | <i>Multiple choice questions</i> | 428 | |
| | <i>Problems</i> | 429 | |
| | <i>Experimental exercise</i> | 431 | |
| | C1 <i>Supplementary Exercises</i> | | 435 |
| 13. | TRANSFORMERS | | 485 |
| | 13.1 Introduction | 485 | |
| | 13.2 Principle of Operation | 486 | |
| | 13.3 Ideal Transformer | 487 | |
| | 13.4 Practical Transformer at No Load | 492 | |
| | 13.5 Construction of Transformer | 496 | |
| | 13.6 Transformer on Load | 497 | |
| | 13.7 Practical Transformer on Load | 499 | |
| | 13.8 Equivalent Circuit of a Transformer | 500 | |
| | 13.9 Voltage Regulation of a Transformer | 503 | |
| | 13.10 Efficiency of a Transformer | 507 | |
| | 13.11 Autotransformers | 510 | |

| | | | |
|------------|--|-----|------------|
| 13.12 | Three-phase Transformers | 513 | |
| 13.13 | Some Special Transformers | 514 | |
| 13.14 | Transformer Testing | 515 | |
| | <i>Additional solved examples</i> | 517 | |
| | <i>Summary</i> | 523 | |
| | <i>Check your understanding</i> | 524 | |
| | <i>Review questions</i> | 525 | |
| | <i>Multiple choice questions</i> | 525 | |
| | <i>Problems</i> | 527 | |
| | <i>Experimental exercises</i> | 530 | |
| 14. | ALTERNATORS AND SYNCHRONOUS MOTORS | | 538 |
| 14.1 | Electro-mechanical Energy-conversion Machines | 538 | |
| 14.2 | Synchronous Machines | 544 | |
| 14.3 | Construction of Alternators | 546 | |
| 14.4 | Rotating Magnetic Flux Due to Three-phase Currents | 549 | |
| 14.5 | Armature Winding | 551 | |
| 14.6 | EMF Equation | 553 | |
| 14.7 | Armature Reaction | 555 | |
| 14.8 | Equivalent Circuit of an Alternator | 557 | |
| 14.9 | Power Delivered by an Alternator | 561 | |
| 14.10 | Measurement of Synchronous Impedance | 562 | |
| 14.11 | Synchronous Motors | 564 | |
| 14.12 | Power Developed by a Synchronous Motor | 567 | |
| 14.13 | Operation of a Synchronous Motor | 569 | |
| 14.14 | Synchronous Condenser | 571 | |
| | <i>Additional solved examples</i> | 572 | |
| | <i>Summary</i> | 582 | |
| | <i>Check your understanding</i> | 583 | |
| | <i>Review questions</i> | 584 | |
| | <i>Multiple choice questions</i> | 585 | |
| | <i>Problems</i> | 587 | |
| 15. | INDUCTION MOTORS | | 589 |
| 15.1 | Introduction | 589 | |
| 15.2 | Principle of Working | 589 | |
| 15.3 | Construction of Induction Motor | 592 | |
| 15.4 | Rotor Emf, Current and Power Factor | 594 | |
| 15.5 | Power Relations for an Induction Motor | 597 | |
| 15.6 | Equivalent Circuit of an Induction Motor | 599 | |
| 15.7 | Torque-slip Characteristics | 604 | |
| 15.8 | Starting of Induction Motors | 609 | |
| | <i>Additional solved examples</i> | 611 | |
| | <i>Summary</i> | 615 | |
| | <i>Check your understanding</i> | 616 | |
| | <i>Review questions</i> | 617 | |
| | <i>Multiple choice questions</i> | 618 | |
| | <i>Problems</i> | 619 | |
| | <i>Experimental exercise</i> | 621 | |
| 16. | DC MACHINES | | 626 |
| 16.1 | Importance | 626 | |
| 16.2 | Construction of a DC Machine | 627 | |

| | | | |
|------------|---|-----|------------|
| 16.3 | Armature Current and Flux | 629 | |
| 16.4 | Armature Winding | 629 | |
| 16.5 | EMF Equation for A DC Generator | 632 | |
| 16.6 | Types of DC Machines | 633 | |
| 16.7 | Armature Reaction | 639 | |
| 16.8 | Losses in A DC Machine | 640 | |
| 16.9 | Efficiency of A DC Generator | 641 | |
| 16.10 | Characteristics of DC Generators | 642 | |
| 16.11 | DC Motors | 648 | |
| 16.12 | Torque Developed by a DC Motor | 650 | |
| 16.13 | Torque and Speed Characteristics of a DC Motor | 651 | |
| 16.14 | Starting of DC Motors | 655 | |
| | <i>Additional solved examples</i> | 656 | |
| | <i>Summary</i> | 662 | |
| | <i>Check your understanding</i> | 663 | |
| | <i>Review questions</i> | 664 | |
| | <i>Multiple choice questions</i> | 664 | |
| | <i>Problems</i> | 666 | |
| | <i>Experimental exercises</i> | 668 | |
| 17. | FRACTIONAL HORSEPOWER MOTORS | | 674 |
| 17.1 | Introduction | 674 | |
| 17.2 | Problem with Single-phase Motor | 675 | |
| 17.3 | Types of Single-phase Motors | 679 | |
| 17.4 | AC Series Motor | 684 | |
| 17.5 | Universal Motor | 685 | |
| 17.6 | Geneva Cam | 686 | |
| 17.7 | Stepper Motors | 686 | |
| 17.8 | Variable Reactance (VR) Stepper Motors | 687 | |
| 17.9 | Permanent Magnet (PM) Stepper Motors | 692 | |
| 17.10 | Hybrid Stepper Motors | 695 | |
| | <i>Summary</i> | 697 | |
| | <i>Check your understanding</i> | 698 | |
| | <i>Review questions</i> | 698 | |
| | <i>Multiple choice questions</i> | 699 | |
| | <i>Problems</i> | 701 | |
| <i>D1</i> | <i>Supplementary Exercises</i> | | 705 |
| 18. | ELECTRICAL MEASURING INSTRUMENTS | | 747 |
| 18.1 | Classification of Instruments | 747 | |
| 18.2 | Principle of Operation | 748 | |
| 18.3 | Essentials of an Instrument | 749 | |
| 18.4 | Moving Coil Instruments | 754 | |
| 18.5 | Permanent Magnet Moving Coil (PMMC) Instruments | 754 | |
| 18.6 | Dynamometer Type Instruments | 757 | |
| 18.7 | Moving-iron Instruments | 758 | |
| 18.8 | Ammeters and Voltmeters | 760 | |
| 18.9 | Resistance Measurement | 768 | |
| 18.10 | Meter Sensitivity (Ohms-per-volt Rating) | 770 | |
| 18.11 | Multimeter | 771 | |
| 18.12 | Measurement of Power | 771 | |

| | | | |
|------------|--|-----|------------|
| 18.13 | Measurement of Energy | 774 | |
| | <i>Additional solved examples</i> | 775 | |
| | <i>Summary</i> | 777 | |
| | <i>Check your understanding</i> | 778 | |
| | <i>Review questions</i> | 779 | |
| | <i>Multiple choice questions</i> | 780 | |
| | <i>Problems</i> | 781 | |
| 19. | ELECTRICAL INSTALLATION AND ILLUMINATION | | 782 |
| 19.1 | Introduction | 782 | |
| 19.2 | Distribution of Electrical Energy | 783 | |
| 19.3 | Wires and Cables for Internal Wiring | 784 | |
| 19.4 | Switches and Circuits | 785 | |
| 19.5 | Electric Wiring Systems | 789 | |
| 19.6 | Types of Wiring | 789 | |
| 19.7 | Other Accessories | 792 | |
| 19.8 | A Typical Control Circuit | 794 | |
| 19.9 | Earthing of Installation | 795 | |
| 19.10 | Safety Precautions In Handling Electrical Appliances | 796 | |
| 19.11 | Testing of Electrical Installation | 797 | |
| 19.12 | Incandescent or Filament Lamp | 799 | |
| 19.13 | Fluorescent Tube | 801 | |
| 19.14 | Compact Fluorescent Lamp (CFL) | 802 | |
| 19.15 | Mercury Vapour Lamp | 803 | |
| 19.16 | Sodium Vapour Lamp | 804 | |
| 19.17 | Neon Lamp | 805 | |
| | <i>Summary</i> | 805 | |
| | <i>Check your understanding</i> | 806 | |
| | <i>Review questions</i> | 807 | |
| E1 | <i>Supplementary Exercises</i> | | 811 |
| | <i>Glossary</i> | | 825 |
| | <i>Index</i> | | 841 |