

# C<sub>CHAPTER</sub> 10

## Additional Problems

### Solved Problems

**10.1** A single-phase to single-phase cycloconverter is supplying an inductive load comprising of a resistance of  $5\Omega$  and an inductance of  $40\text{ mH}$  from a  $230\text{ V}$ ,  $50\text{ Hz}$  single-phase supply. It is required to provide an output frequency which is  $1/3$  of the input frequency. If the converters are operated as semiconverter such that  $0 \leq \alpha \leq \pi$  and firing delay angle  $\alpha_p = 120^\circ$ . Neglecting the harmonic content of load voltage, determine:

- rms value of output voltage.
- rms current of each thyristor and
- input power factor.

**Sol.** Given:  $E = 230\text{ V}$ ,  $f_1 = 50\text{ Hz}$ ,  $\alpha_p = \frac{2\pi}{3}$

$$f_0 = 50/3 = 16.67\text{ Hz}, R = 5\Omega, L = 40\text{ mH}.$$

$$\omega_0 = 2\pi \times 50/3 = 104.72\text{ rad/s}.$$

$$X_L = \omega_0 L = 104.72 \times 40 \times 10^{-3} = 4.188\ \Omega$$

$$Z_L = \sqrt{5^2 + (4.188)^2} = 6.52\ \Omega.$$

$$\theta = \tan^{-1}(\omega_0 L/R) \cong 40^\circ.$$

- (a) For  $0 \leq \alpha \leq \pi$ , rms value of output voltage,

$$\begin{aligned} E_o &= E \cdot \left[ \frac{1}{\pi} \left( \pi - \alpha_p + \frac{\sin 2\alpha_p}{2} \right) \right]^{1/2} \\ &= 230 \cdot \left[ \frac{1}{\pi} \left\{ \left( \pi - \frac{2\pi}{3} \right) + \frac{\sin 240}{2} \right\} \right]^{1/2} \\ &= 101.6\text{ V} \end{aligned}$$

- (b) RMS value of load current,  $I_o = \frac{E_o}{Z_L}$

$$= \frac{101.6}{4.188} = 24.26\text{ A}.$$

The rms current through each converter group is

$$I_P = I_N = \frac{I_o}{\sqrt{2}} = 17.1542 \text{ A.}$$

and the *rms* current through each thyristor

$$I_{T_{rms}} = \frac{I_P}{\sqrt{2}} = \frac{17.1542}{\sqrt{2}} = 12.13 \text{ A.}$$

(c) *rms* input current,  $I_i = I_o = 24.26 \text{ A.}$

The volt-amp rating =  $E \cdot I_i = 230 \times 24.26 = 5580 \text{ VA}$

The output power,  $P_o = E_o \cdot I_o \cdot \cos \theta = 101.6 \times 24.26 \times \cos 40^\circ$   
 $= 1888.1 \text{ watts.}$

$$\begin{aligned} \therefore \text{Power factor} &= \frac{P_o}{E \cdot I_i} = \frac{1888}{5580} \\ &= 0.3384 \text{ (lagging)} \end{aligned}$$

$$\begin{aligned} \text{Now, P.F.} &= \frac{m_f}{\sqrt{2}} \cdot \cos \phi \\ m_f &= \cos (180 - \alpha_p) = \cos 60^\circ = 0.5 \\ \cos \phi &= \cos 40 = 0.766. \end{aligned}$$

$$\text{Hence, } P_f = \frac{0.5}{\sqrt{2}} \cdot \cos 40 = 0.27$$

which shows that the harmonic content in the output voltage reduces the power-factor.

**10.2** A six-pulse cycloconverter is supplying a load current of 50 A from a 440 V, 50 Hz supply having a reactance of 0.5  $\Omega$ /phase. Determine the input-load voltage for firing delay angles of  $0^\circ$  and  $45^\circ$ .

**Sol.** (1) When firing delay angle,  $\alpha = 0$ ,

we have the relation from chapter 6,

$$I_{dc} = \frac{\sqrt{2} \cdot E}{w \cdot L_s} \cdot \sin \frac{\pi}{p} \cdot [\cos \alpha - \cos (\alpha + \mu)]$$

Now,  $\alpha = 0$ , and  $\pi = 6$

$$\therefore (w \cdot L_s) \cdot I_{dc} = \sqrt{2} \times E \cdot \sin \frac{\pi}{6} [1 - \cos \mu]$$

$$0.5 \times 50 = \sqrt{2} \cdot 440 \times \frac{1}{2} [1 - \cos \mu]$$

$$\text{or, } 25 = 311.127 (1 - \cos \mu)$$

$$\text{or } \cos \mu = 0.917 = \cos (23.12^\circ)$$

$$\therefore \mu = 23.12^\circ$$

Now, average value of load voltage

$$E_{\text{omax}} = \sqrt{2} \cdot E \frac{p}{\pi} \cdot \sin \frac{\pi}{p} \cdot \left[ \frac{\cos (\alpha + \mu) + \cos \alpha}{2} \right] \quad \text{(ii)}$$

$$\begin{aligned} \therefore E_{\text{omax}} &= \sqrt{2} \times 440 \times \frac{6}{\pi} \cdot \frac{6}{\pi} \frac{1}{2} \left( \frac{1 + \cos 23.12^\circ}{2} \right) \\ &= 570.35 \text{ V.} \end{aligned}$$

$$\begin{aligned} \text{rms value of load voltage, } E_o &= \frac{570.35}{\sqrt{2}} \\ &= 403.3 \text{ V.} \end{aligned}$$

(ii) When firing delay angle  $\alpha = 45^\circ$ .

from eqn., (ii),

$$0.5 \times 50 = \sqrt{2} \times 440 \times \frac{1}{2} [\cos 45^\circ - \cos (45^\circ + \mu)]$$

$$0.08 = 0.707 - \cos (45^\circ + \mu)$$

$$\text{or } \cos (45^\circ + \mu) = 0.707 - 0.08 = 0.627$$

$$\text{or } \cos (45^\circ + \mu) = \cos (51.6^\circ)$$

$$\therefore \mu = 6.163^\circ.$$

Average d.c. voltage is given by

$$E_{\text{Oav}} = 1.35 \times 440 \times \left[ \frac{\cos 45^\circ + \cos (51.16)}{2} \right] = 396.27 \text{ V.}$$

$\therefore$  rms value of load voltage  $E_o$

$$= \frac{396.27}{\sqrt{2}} = 280.2 \text{ V.}$$