

# Contents

<b>1. Semiconductor Physics and PN Junction</b>	<b>1</b>
1.1 Introduction—Electronics and its Evolution	2
1.2 Atomic Structure	3
1.3 Covalent Bonding	5
1.4 Energy-Band Diagrams	7
1.5 Semiconductor Materials	10
1.6 Semiconductor Junction Diode	16
1.7 Diode Breakdown and Current Equation	20
1.8 Diode Equivalent Circuits	29
1.9 Transition and Diffusion Capacitance	32
1.10 Diode as a Switch and Reverse Recovery Time	33
1.11 Diode Specification Sheets	34
1.12 Diode Testing	34
1.13 Other Diodes	35
<i>Summary</i>	41
<i>Review Questions</i>	43
<i>Exercise Problems</i>	44
<i>Multiple-Choice Questions</i>	46
<b>2. Diode Applications</b>	<b>51</b>
2.1 Introduction	52
2.2 Power-Supply Block Diagram	52
2.3 Load Line Analysis	54
2.4 Rectifiers: Half-Wave Rectifier	56
2.5 Rectifiers: Centre-Tapped Full-Wave Rectifier	63
2.6 Rectifiers: Bridge-Type Full-Wave Rectifier	71
2.7 Filters: <i>RLC</i> Filters	79
2.8 Regulators	84
2.9 Voltage-Multiplier Circuits	90
2.10 Clipping Circuits	93
2.11 Clamping Circuits	95
<i>Summary</i>	100

*Review Questions* 101  
*Exercise Problems* 102  
*Multiple-Choice Questions* 105

<b>3.</b>	<b>Bipolar Junction Transistors</b>	<b>109</b>
3.1	Introduction	110
3.2	Transistor Construction and Operation	112
3.3	Transistor Configurations	114
3.4	Transistor as an Amplifier	122
3.5	Transistor Specification Sheet	124
3.6	Transistor Testing	126
3.7	Introduction to BJT Biasing	127
3.8	Load-Line Analysis and Operating Point	128
3.9	Two-Battery Bias Configuration	130
3.10	Fixed-Bias Configuration	131
3.11	Feedback-Bias Configuration	133
3.12	Self-Bias or Emitter-Bias Configuration	135
3.13	Voltage Divider-Bias Configuration	137
3.14	Bias Compensation	140
3.15	Emitter-Follower Configuration	142
3.16	Transistor as a Switch	143
	<i>Summary</i>	145
	<i>Review Questions</i>	146
	<i>Exercise Problems</i>	147
	<i>Multiple-Choice Questions</i>	151
<b>4.</b>	<b>BJT Amplifiers, Feedback and Oscillators</b>	<b>155</b>
4.1	Introduction	156
4.2	Amplifier Basics	156
4.3	Amplifier Classification	156
4.4	Amplifier Frequency Response	172
4.5	Multistage Amplifiers and Coupling	172
4.6	RC Coupled Amplifier	174
4.7	Feedback in Amplifiers	176
4.8	Advantages of Negative Feedback	180
4.9	Analysis of Amplifiers	182
4.10	Principle of Sinusoidal Oscillators	183
4.11	RC Phase-shift Oscillator	185
4.12	Wein Bridge Oscillator	185
4.13	Hartley Oscillator and Colpitts Oscillator	186
4.14	Crystal Oscillator	188
	<i>Summary</i>	191
	<i>Review Questions</i>	192
	<i>Exercise Problems</i>	193
	<i>Multiple-Choice Questions</i>	194

<b>5.</b>	<b>Communication Systems</b>	<b>199</b>
5.1	Introduction	200
5.2	Communication System	200
5.3	Amplitude Modulation (AM)	203
5.4	Angle Modulation	213
5.5	Demodulation Techniques	219
5.6	Radio Transmitter	221
5.7	Radio Receiver	222
5.8	Television System	225
	<i>Summary</i>	227
	<i>Review Questions</i>	228
	<i>Exercise Problems</i>	229
	<i>Multiple-Choice Questions</i>	230
<b>6.</b>	<b>Linear Integrated Circuits</b>	<b>235</b>
6.1	Introduction	236
6.2	Differential Amplifier Circuit	236
6.3	Op-Amp Characteristics	243
6.4	Op-Amp Specifications	248
6.5	Op-Amp Equivalent Circuit	249
6.6	Op-Amp Inverter	250
6.7	Op-Amp Non-Inverter	253
6.8	Op-Amp Buffer or Voltage Follower	255
6.9	Op-Amp Summer or Summing Amplifier	256
6.10	Op-Amp Integrator	259
6.11	Op-Amp Differentiator	260
6.12	Op-Amp Subtractor or Difference Amplifier	262
6.13	Instrumentation Amplifier	263
6.14	Op-Amp Comparator	265
6.15	Op-Amp Schmitt Trigger	269
6.16	Active Filters	271
6.17	Timer-555	279
6.18	PLL-565	284
	<i>Summary</i>	287
	<i>Review Questions</i>	288
	<i>Exercise Problems</i>	289
	<i>Multiple-Choice Questions</i>	292
<b>7.</b>	<b>Digital Electronics</b>	<b>297</b>
7.1	Introduction	298
7.2	Number Systems	300
7.3	Number Base Conversions	306
7.4	Addition and Subtraction	312
7.5	Basic Logic Gates	314
7.6	Universal Logic Gates	319
7.7	Boolean Postulates	323

7.8	De Morgan's Theorems	325	
7.9	Simplification of Boolean Switching Functions	326	
7.10	Combinational and Sequential Circuits	331	
7.11	Arithmetic Circuits	332	
7.12	Latches and Flip-Flops	336	
7.13	Counters	345	
7.14	Shift Registers	349	
	<i>Summary</i>	353	
	<i>Review Questions</i>	354	
	<i>Exercise Problems</i>	355	
	<i>Multiple-Choice Questions</i>	357	
<b>8.</b>	<b>Measuring Instruments</b>		<b>365</b>
8.1	Introduction	366	
8.2	Voltage Measurement	367	
8.3	Current Measurement	369	
8.4	Rectifier-Type Voltmeter	371	
8.5	Multimeters	372	
8.6	Cathode Ray Oscilloscope (CRO)	375	
8.7	Lissajous Figures	383	
8.8	Dual Trace Oscilloscope	387	
	<i>Summary</i>	388	
	<i>Review Questions</i>	388	
	<i>Exercise Problems</i>	389	
	<i>Multiple-Choice Questions</i>	390	
<b>9.</b>	<b>Transducers</b>		<b>393</b>
9.1	Introduction	394	
9.2	Classification of Transducers	397	
9.3	Capacitive Transducers	398	
9.4	Inductive Transducers	399	
9.5	Linearly Variable Differential Transducer (LVDT)	400	
9.6	Potentiometric Transducer	401	
9.7	Piezoelectric Transducer	402	
9.8	Electrical Strain Gauges	403	
9.9	Thermistors, Thermocouples and Hall Effect	405	
	<i>Summary</i>	411	
	<i>Review Questions</i>	412	
	<i>Exercise Problems</i>	412	
	<i>Multiple-Choice Questions</i>	413	
<b>10.</b>	<b>Field Effect Transistors and Other Devices</b>		<b>419</b>
10.1	Introduction	420	
10.2	Field Effect Transistors (FETs)	420	
10.3	MOSFETs	440	
10.4	Silicon-Controlled Rectifier (SCR)	450	
10.5	UniJunction Transistor (UJT)	455	

10.6	Other Special Devices	460
	<i>Summary</i>	464
	<i>Review Questions</i>	465
	<i>Exercise Problems</i>	467
	<i>Multiple-Choice Questions</i>	469

**Question Bank**

<b>Additional Solved Examples</b>	<b>477</b>
<b>Quiz Questions (Short-Answer Questions)</b>	<b>519</b>

<b>Appendix A: Some Important Tables</b>	<b>551</b>
--	------------

<b>Appendix B: Some Important Inventions</b>	<b>555</b>
--	------------

<b>Index</b>	<b>557</b>
--------------	------------