

CHAPTER 11

P.P.11.1 $i(t) = 33\sin(10t + 60^\circ) = 33\cos(10t - 30^\circ)$
 $v(t) = 330\cos(10t + 20^\circ)$

$$p(t) = v(t)i(t) = (330)(33)\cos(10t + 20^\circ)\cos(10t - 30^\circ)$$

$$p(t) = \frac{1}{2} \cdot 10890[\cos(20t + 20^\circ - 30^\circ) + \cos(20 - (-30^\circ))]$$

$$p(t) = \mathbf{(3.5 + 5.445\cos(20t - 10^\circ)) \text{ kW}}$$


$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \mathbf{3.5 \text{ kW}}$$

P.P.11.2 $\mathbf{V = IZ = 1320\angle 8^\circ}$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P = \frac{1}{2} (1320)(33) \cos(8^\circ - 30^\circ) = \mathbf{20.19 \text{ kW}}$$

P.P.11.3

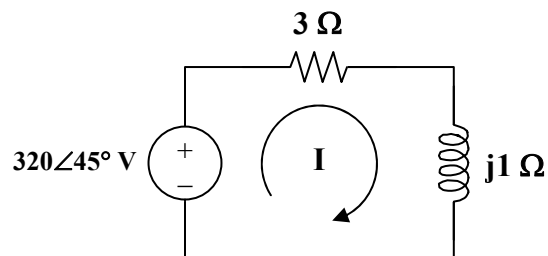

$$\mathbf{I = \frac{320\angle 45^\circ}{3 + j} = 101.19\angle 26.57^\circ}$$

For the resistor,

$$\mathbf{I_R = I = 101.19\angle 26.57^\circ}$$

$$\mathbf{V_R = 3I = 303.6\angle 26.57^\circ}$$

$$P_R = \frac{1}{2} V_m I_m = \frac{1}{2} (303.6)(101.19) = \mathbf{15.361 \text{ kW}}$$

For the inductor,

$$\mathbf{I}_L = 101.19 \angle 26.57^\circ$$


$$\mathbf{V}_L = j\mathbf{I}_L = 101.19 \angle (26.57^\circ + 90^\circ) = 101.19 \angle 116.57^\circ$$

$$P_L = \frac{1}{2}(101.19)^2 \cos(90^\circ) = \mathbf{0 \text{ W}}$$

The average power supplied is

$$P = \frac{1}{2}(320)(101.19) \cos(45^\circ - 26.57^\circ) = \mathbf{15.361 \text{ kW}}$$

P.P.11.4 Consider the circuit below.

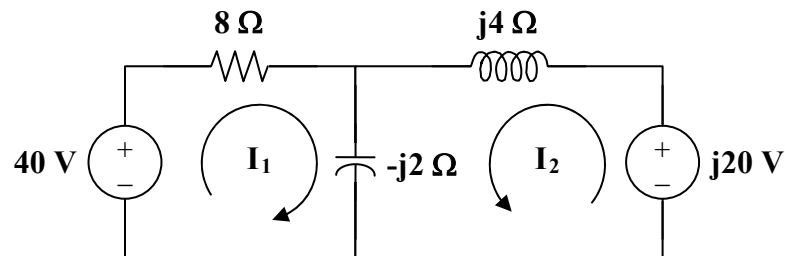

For mesh 1,

$$\begin{aligned} -40 + (8 - j2)\mathbf{I}_1 + (-j2)\mathbf{I}_2 &= 0 \\ (4 - j)\mathbf{I}_1 - j\mathbf{I}_2 &= 20 \end{aligned} \quad (1)$$

For mesh 2,

$$\begin{aligned} -j20 + (j4 - j2)\mathbf{I}_2 + (-j2)\mathbf{I}_1 &= 0 \\ -j\mathbf{I}_1 + j\mathbf{I}_2 &= j10 \end{aligned} \quad (2)$$

In matrix form,

$$\begin{bmatrix} 4 - j & -j \\ -j & j \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 20 \\ j10 \end{bmatrix}$$

$$\Delta = 2 + j4, \quad \Delta_1 = -10 + j20, \quad \Delta_2 = 10 + j60$$

$$\mathbf{I}_1 = \frac{\Delta_1}{\Delta} = 5 \angle 53.14^\circ \quad \text{and} \quad \mathbf{I}_2 = \frac{\Delta_2}{\Delta} = 13.6 \angle 17.11^\circ$$

For the 40-V voltage source,

$$\mathbf{V}_s = 40 \angle 0^\circ$$

$$\mathbf{I}_1 = 5 \angle 53.14^\circ$$

$$P_s = \frac{-1}{2}(40)(5) \cos(-53.14^\circ) = \mathbf{-60 \text{ W}}$$

For the j20-V voltage source,

$$\mathbf{V}_s = 20\angle 90^\circ$$

$$\mathbf{I}_2 = 13.6\angle 17.11^\circ$$

$$P_s = \frac{-1}{2}(20)(13.6)\cos(90^\circ - 17.11^\circ) = -40 \text{ W}$$

For the resistor,


$$I = |\mathbf{I}_1| = 5$$

$$V = 8|\mathbf{I}_1| = 40$$

$$P = \frac{1}{2}(40)(5) = 100 \text{ W}$$


The average power absorbed by the inductor and capacitor is **zero watts**.

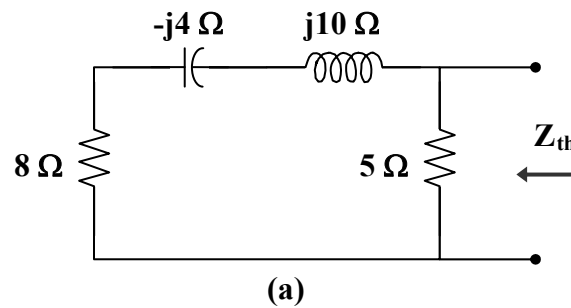P.P.11.5 We first obtain the Thevenin equivalent circuit across \mathbf{Z}_L . \mathbf{Z}_{Th} is obtained from the circuit in Fig. (a).



$$\mathbf{Z}_{Th} = 5 \parallel (8 - j4 + j10) = \frac{(5)(8 + j6)}{13 + j6} = 3.415 + j0.7317$$

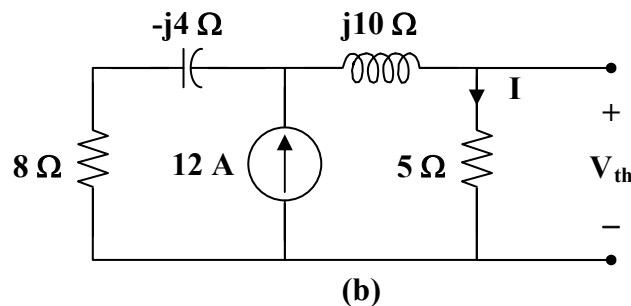\mathbf{V}_{Th} is obtained from the circuit in Fig. (b).



By current division,

$$\mathbf{I} = \frac{8 - j4}{8 - j4 + j10 + 5}(12)$$

$$\mathbf{V}_{Th} = 5\mathbf{I} = \frac{(60)(8 - j4)}{13 + j6} = 37.5 \angle -51.34^\circ$$

$$\mathbf{Z}_L = (\mathbf{Z}_{Th})^* = [3.415 - j0.7317] \Omega$$

$$P_{\max} = \frac{|\mathbf{V}_{Th}|^2}{8R_L} = \frac{(37.5)^2}{(8)(3.415)} = 51.47 \text{ W}$$

P.P.11.6 We first find \mathbf{Z}_{Th} and \mathbf{V}_{Th} across R_L .

Let $\mathbf{Z}_1 = 80 + j60$

$$\mathbf{Z}_2 = 90 \parallel (-j30) = \frac{(90)(-j30)}{90 - j30} = 9(1 - j3)$$

$$\mathbf{Z}_{Th} = \mathbf{Z}_1 \parallel \mathbf{Z}_2 = \frac{(80 + j60)(9 - j27)}{80 + j60 + 9 - j27} = 17.181 - j24.57 \Omega$$

$$\mathbf{V}_{Th} = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} (120 \angle 60^\circ) = \frac{(9)(1 - j3)}{89 + j33} (120 \angle 60^\circ)$$

$$\mathbf{V}_{Th} = 35.98 \angle -31.91^\circ$$

$$R_L = |\mathbf{Z}_{Th}| = 30 \Omega$$

The current through the load is

$$\mathbf{I} = \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th} + R_L} = \frac{35.98 \angle -31.91^\circ}{47.181 - j24.57} = 0.6764 \angle -4.4^\circ$$

The maximum average power absorbed by R_L is

$$P_{\max} = \frac{1}{2} |\mathbf{I}|^2 R_L = \frac{1}{2} (0.6764)^2 (30) = 6.863 \text{ W}$$

P.P.11.7
$$i(t) = \begin{cases} 16t & 0 < t < 1 \\ 32 - 16t & 1 < t < 2 \end{cases} \quad T = 2$$

$$I_{rms}^2 = \frac{1}{T} \int_0^T i^2 dt = \frac{1}{2} \left[\int_0^1 (16t)^2 dt + \int_1^2 (32 - 16t)^2 dt \right]$$

$$I_{rms}^2 = \frac{256}{2} \left[\int_0^1 t^2 dt + \int_1^2 (4 - 4t + t^2) dt \right]$$

$$I_{rms}^2 = 128 \left[\frac{1}{3} + \left(4t - 2t^2 + \frac{t^3}{3} \right) \Big|_1^2 \right] = \frac{256}{3}$$

$$I_{rms} = \sqrt{\frac{256}{3}} = 9.238 \text{ A}$$

$$P = I_{rms}^2 R = (9.238^2)(9) = 768 \text{ W}$$

P.P.11.8 $T = \pi$, $v(t) = 100\sin(t)$, $0 < t < \pi$

$$V_{rms}^2 = \frac{1}{T} \int_0^T v^2 dt = \frac{1}{\pi} \int_0^\pi (100\sin(t))^2 dt$$

$$V_{rms}^2 = \frac{10^4}{\pi} \int_0^\pi \frac{1}{2} [1 - \cos(2t)] dt = 5000$$

$$V_{rms} = 70.71 \text{ V}$$

$$P = \frac{V_{rms}^2}{R} = \frac{5000}{6} = 833.3 \text{ W}$$

P.P.11.9 The load impedance is
 $Z = 60 + j40 = 72.11 \angle 33.7^\circ \Omega$

The power factor is
 $\text{pf} = \cos(33.7^\circ) = 0.8321$ lagging

Since the load is inductive

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{320 \angle 10^\circ}{72.11 \angle 33.7^\circ} = 4.438 \angle -23.69^\circ \text{ A}$$

The apparent power is

$$\mathbf{S} = \mathbf{V}_{rms}(\mathbf{I}_{rms})^* = 0.5(320)(4.438) \angle (10^\circ - (-23.69^\circ)) = 710 \angle 33.69^\circ \text{ VA}$$

P.P.11.10 The total impedance as seen by the source is

$$\mathbf{Z} = 10 + j4 \parallel (8 - j6) = 10 + \frac{(j4)(8 - j6)}{8 - j2}$$

$$\mathbf{Z} = 12.69 \angle 20.62^\circ$$

The power factor is

$$\text{pf} = \cos(20.62^\circ) = 0.936 \text{ (lagging)}$$

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{165 \angle 0^\circ}{12.69 \angle 20.62^\circ} = 13.002 \angle -20.62^\circ$$

The average power supplied by the source is equal to the power absorbed by the load.

$$P = I_{rms}^2 R = (13.002)^2 (11.88) = 1,062 \text{ W} = 2.008 \text{ kW}$$

$$\text{or } P = V_{rms} I_{rms} \text{pf} = (165)(13.002)(0.936) = 2.008 \text{ kW}$$

P.P.11.11

$$(a) \quad \mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = (110 \angle 85^\circ)(0.4 \angle -15^\circ)$$

$$\mathbf{S} = 44 \angle 70^\circ \text{ VA}$$

$$S = |\mathbf{S}| = 44 \text{ VA}$$

$$(b) \quad \mathbf{S} = 44 \angle 70^\circ = 15.05 + j41.35$$

$$P = 15.05 \text{ W}, \quad Q = 41.35 \text{ VAR}$$

$$(c) \quad \text{pf} = \cos(70^\circ) = 0.342 \quad (\text{lagging})$$

$$\mathbf{Z} = \frac{\mathbf{V}_{\text{rms}}}{\mathbf{I}_{\text{rms}}} = \frac{110 \angle 85^\circ}{0.4 \angle -15^\circ} = 275 \angle 70^\circ$$


$$\mathbf{Z} = 94.06 + j258.4 \Omega$$

P.P.11.12

$$(a) \quad \text{If } \mathbf{Z} = 250 \angle -75^\circ, \quad \text{pf} = \cos(-75^\circ) = 0.2588 \quad (\text{leading})$$

$$(b) \quad Q = S \sin \theta \longrightarrow S = \frac{Q}{\sin \theta} = \frac{-100 \text{ kVAR}}{\sin(-75^\circ)} = 103.53 \text{ kVA}$$

$$(c) \quad S = \frac{V_{\text{rms}}^2}{|\mathbf{Z}|} \longrightarrow V_{\text{rms}} = \sqrt{S \cdot |\mathbf{Z}|} = \sqrt{(103530)(250)} = 5.087 \text{ kV}$$

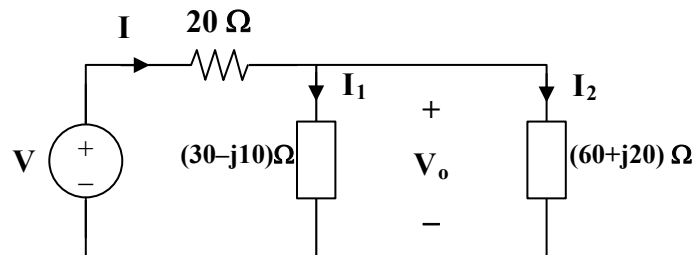P.P.11.13 Consider the circuit below.

Let \mathbf{I}_2 be the current through the $60\text{-}\Omega$ resistor.

$$P = \mathbf{I}_2^2 R \longrightarrow \mathbf{I}_2^2 = \frac{P}{R} = \frac{240}{60} = 4$$

$$\mathbf{I}_2 = 2 \text{ (rms)}$$

$$\mathbf{V}_o = \mathbf{I}_2 (60 + j20) = 120 + j40$$

$$\mathbf{I}_1 = \frac{\mathbf{V}_o}{30 - j10} = 3.2 + j2.4$$

$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2 = 5.2 + j2.4$$

$$\mathbf{V} = 20\mathbf{I} + \mathbf{V}_o = (104 + j48) + (120 + j40)$$

$$\mathbf{V} = 224 + j88 = \mathbf{240.7} \angle \mathbf{21.45^\circ} \mathbf{V}_{\text{rms}}$$

For the 20- Ω resistor,

$$\mathbf{V} = 20\mathbf{I} = 204 + j48 = 114.54 \angle 24.8^\circ$$

$$\mathbf{I} = 5.2 + j2.4 = 5.727 \angle 24.8^\circ$$

$$\mathbf{S} = \mathbf{VI}^* = (114.54 \angle 24.8^\circ)(5.727 \angle -24.8^\circ)$$

$$\mathbf{S} = \mathbf{656 \text{ VA}}$$

For the (30 - j10)- Ω impedance,

$$\mathbf{V}_o = 120 + j40 = 126.5 \angle 18.43^\circ$$

$$\mathbf{I}_1 = 3.2 + j2.4 = 4 \angle 36.87^\circ$$

$$\mathbf{S}_1 = \mathbf{V}_o \mathbf{I}_1^* = (126.5 \angle 18.43^\circ)(4 \angle -36.87^\circ)$$

$$\mathbf{S}_1 = 506 \angle -18.44^\circ = \mathbf{[480 - j160] \text{ VA}}$$

For the (60 + j20)- Ω impedance,

$$\mathbf{I}_2 = 2 \angle 0^\circ$$

$$\mathbf{S}_2 = \mathbf{V}_o \mathbf{I}_2^* = (126.5 \angle 18.43^\circ)(2 \angle -0^\circ)$$

$$\mathbf{S}_2 = 253 \angle 18.43^\circ = \mathbf{[240 + j80] \text{ VA}}$$

The overall complex power supplied by the source is

$$\mathbf{S}_T = \mathbf{VI}^* = (240.67 \angle 21.45^\circ)(5.727 \angle -24.8^\circ)$$

$$\mathbf{S_T} = 1378.3\angle-3.35^\circ = \mathbf{[1376-j80] VA}$$

P.P.11.14

For load 1,

$$P_1 = 2000, \quad \text{pf} = 0.75 = \cos \theta_1 \longrightarrow \theta_1 = -41.41^\circ$$

$$P_1 = S_1 \cos \theta_1 \longrightarrow S_1 = \frac{P_1}{\cos \theta_1} = 2666.67$$

$$Q_1 = S_1 \sin \theta_1 = -176.85$$

$$S_1 = P_1 + jQ_1 = 2000 - j1763.85 \quad (\text{leading})$$

For load 2,

$$P_2 = 4000, \quad \text{pf} = 0.95 = \cos \theta_2 \longrightarrow \theta_2 = 18.19^\circ$$

$$S_2 = \frac{P_2}{\cos \theta_2} = 4210.53$$

$$Q_2 = S_2 \sin \theta_2 = 1314.4$$

$$S_2 = P_2 + jQ_2 = 4000 + j1314.4 \quad (\text{lagging})$$

The total complex power is

$$S = S_1 + S_2 = [6 - j0.4495] \text{ kVA}$$

$$\text{pf} = \frac{P}{|S|} = \frac{6000}{6016.18} = \mathbf{0.9972} \quad (\text{leading})$$

P.P.11.15 $\text{pf} = 0.85 = \cos \theta \longrightarrow \theta = 31.79^\circ$

$$Q = S \sin \theta \longrightarrow S = \frac{Q}{\sin \theta} = \frac{140}{\sin(31.79^\circ)} = 265.8 \text{ kVA}$$

$$P = S \cos \theta = 225.93 \text{ kW}$$

For $\text{pf} = 1 = \cos \theta_1 \longrightarrow \theta_1 = 0^\circ$

Since P remains the same,

$$P = P_1 = S_1 \cos \theta_1 \longrightarrow S_1 = \frac{P_1}{\cos \theta_1} = 225.93$$

$$Q_1 = S_1 \sin \theta_1 = 0$$

The difference between the new Q_1 and the old Q is Q_c .

$$Q_c = 140 \text{ kVAR} = \omega C V_{\text{rms}}^2$$

$$C = \frac{140 \times 10^3}{(2\pi)(60)(110)^2} = \mathbf{30.69 \text{ mF}}$$

P.P.11.16 The wattmeter measures the average power from the source.

Let $Z_1 = 4 - j2$

$$Z_2 = 12 \parallel j9 = \frac{(12)(j9)}{12 + j9} = 4.32 + j5.76$$

$$Z = Z_1 + Z_2 = 8.32 + j3.76 = 9.13 \angle 24.32^\circ$$

$$S = \mathbf{VI}^* = \frac{|\mathbf{V}|^2}{\mathbf{Z}^*} = \frac{(120)^2}{9.13 \angle -24.32^\circ} = 1577.2 \angle 24.32^\circ \text{ VA}$$

$$P = |\mathbf{S}| \cos \theta = \mathbf{1.437 \text{ kW}}$$

P.P.11.17 Demand charge = $\$5 \times 32,000 = \$160,000$

Energy charge for the first 50,000 kWh = $\$0.08 \times 50,000 = \$4,000$

The remaining energy = $500,000 - 50,000 = 450,000 \text{ kWh}$

Charge for this bill = $\$0.05 \times 450,000 = \$22,500$

Total bill = $\$160,000 + \$4,000 + \$22,500 = \mathbf{\$186,500}$

P.P.11.18 Energy consumed = $800 \text{ kW} \times 20 \times 26 = 416,000 \text{ kWh}$

The power factor of 0.88 exceeds 0.85 by 3×0.01 . Hence, there is a power factor credit which amounts to an energy credit of

$$416,000 \times \frac{0.1}{100} \times 3 = 1248 \text{ kWh}$$

Total energy billed = $416,000 - 1,248 = 414,752 \text{ kWh}$

Energy cost = $\$0.06 \times 414,752 = \mathbf{\$24,885.12}$