

Contents

<i>Preface to the Third Edition</i>	<i>xix</i>
<i>List of Abbreviations</i>	<i>xxiii</i>
<i>List of Important Formulae</i>	<i>xxvi</i>
1. Qualities of Measurements	1
1.1 Introduction	1
1.2 Performance Characteristics	1
1.3 Static Characteristics	2
1.4 Error in Measurement	2
1.5 Types of Static Error	5
1.6 Sources of Error	8
1.7 Dynamic Characteristics	8
1.8 Statistical Analysis	11
1.9 Standard	15
1.10 Electrical Standards	16
1.11 Atomic Frequency and Time Standards	19
1.12 Graphical Representation of Measurements as a Distribution	20
<i>Review Questions</i>	<i>22</i>
<i>Multiple Choice Questions</i>	<i>23</i>
<i>Practice Problems</i>	<i>24</i>
<i>Further Reading</i>	<i>24</i>
2. Indicators and Display Devices	25
2.1 Introduction	25
2.2 Basic Meter Movement	26
2.3 Taut Band Instrument	31
2.4 Electrodynamometer	32
2.5 Moving Iron Types Instrument	35
2.6 Concentric Vane Repulsion Type (Moving Iron Type) Instrument	36
2.7 Digital Display System and Indicators	38
2.8 Classification of Displays	38
2.9 Display Devices	39
2.10 Light Emitting Diodes (LED)	39
2.11 Liquid Crystal Display (LCD)	41

2.12	Other Displays	43	
2.13	Printers	54	
2.14	Classification of Printers	54	
2.15	Printer Character Set	55	
2.16	Character at a Time Impact Printers for Fully Formed Characters (Drum Wheel)	55	
2.17	Line at a Time Impact Printers for Fully Formed Characters (Line Printers)	57	
2.18	Drum Printer	58	
2.19	Dot-Matrix Printers	59	
2.20	Character at a Time Dot-Matrix Impact Printer	59	
2.21	Non-Impact Dot-Matrix (NIDM) Printers	61	
	<i>Review Questions</i>	61	
	<i>Multiple Choice Questions</i>	63	
	<i>Further Reading</i>	63	
3.	Ammeters		64
3.1	DC Ammeter	64	
3.2	Multirange Ammeters	66	
3.3	The Aryton Shunt or Universal Shunt	67	
3.4	Requirements of a Shunt	71	
3.5	Extending of Ammeter Ranges	71	
3.6	RF Ammeter (Thermocouple)	72	
3.7	Limitations of Thermocouples	73	
3.8	Effect of Frequency on Calibration	74	
3.9	Measurements of Very Large Currents by Thermocouples	75	
	<i>Review Questions</i>	76	
	<i>Multiple Choice Questions</i>	77	
	<i>Practice Problems</i>	77	
	<i>Further Reading</i>	78	
4.	Voltmeters and Multimeters		79
4.1	Introduction	79	
4.2	Basic Meter as a DC Voltmeter	79	
4.3	DC Voltmeter	80	
4.4	Multirange Voltmeter	81	
4.5	Extending Voltmeter Ranges	84	
4.6	Loading	87	
4.7	Transistor Voltmeter (TVM)	91	
4.8	Chopper Type DC Amplifier Voltmeter (Microvoltmeter)	92	
4.9	Solid State Voltmeter	95	
4.10	Differential Voltmeter	96	
4.11	DC Standard/Difference Voltmeter	96	
4.12	AC Voltmeter Using Rectifiers	99	

4.13	AC Voltmeter Using Half Wave Rectifier	100
4.14	AC Voltmeter Using Full Wave Rectifier	101
4.15	Multirange AC Voltmeter	104
4.16	Average Responding Voltmeter	105
4.17	Peak Responding Voltmeter	106
4.18	True RMS Voltmeter	107
4.19	True RMS Meter	107
4.20	Considerations in Choosing an Analog Voltmeter	109
4.21	Ohmmeter (Series Type Ohmmeter)	110
4.22	Shunt Type Ohmmeter	117
4.23	Calibration of DC Instrument	120
4.24	Calibration of Ohmmeter	120
4.25	Multimeter	121
4.26	Multimeter Operating Instructions	123
	<i>Review Questions</i>	124
	<i>Multiple Choice Questions</i>	125
	<i>Practice Problems</i>	126
	<i>Further Reading</i>	127
5.	Digital Voltmeters	128
5.1	Introduction	128
5.2	Ramp Technique	129
5.3	Dual Slope Integrating Type DVM (Voltage to Time Conversion)	130
5.4	Integrating Type DVM (Voltage to Frequency Conversion)	132
5.5	Most Commonly Used Principles of ADC (Analog to Digital Conversion)	135
5.6	Successive Approximations	136
5.7	Continuous Balance DVM or Servo Balancing Potentiometer Type DVM	140
5.8	3½-Digit	140
5.9	Resolution and Sensitivity of Digital Meters	141
5.10	General Specifications of a DVM	142
5.11	Microprocessor-Based Ramp Type DVM	142
	<i>Review Questions</i>	145
	<i>Multiple Choice Questions</i>	145
	<i>Practice Problems</i>	146
	<i>Further Reading</i>	146
6.	Digital Instruments	147
6.1	Introduction	147
6.2	Digital Multimeters	148
6.3	Digital Frequency Meter	152
6.4	Digital Measurement of Time	155
6.5	Universal Counter	158

6.6	Decade Counter	159
6.7	Electronic Counter	160
6.8	Digital Measurement of Frequency (Mains)	162
6.9	Digital Tachometer	165
6.10	Digital pH Meter	165
6.11	Automation in Digital Instruments	166
6.12	Digital Phase Meter	171
6.13	Digital Capacitance Meter	172
6.14	Microprocessor-Based Instruments	173
6.15	The IEEE 488 Bus	173
	<i>Review Questions</i>	174
	<i>Multiple Choice Questions</i>	175
	<i>Further Reading</i>	175

7. Oscilloscope **176**

7.1	Introduction	176
7.2	Basic Principle	176
7.3	CRT Features	180
7.4	Block Diagram of Oscilloscope	184
7.5	Simple CRO	185
7.6	Vertical Amplifier	186
7.7	Horizontal Deflecting System	187
7.8	Triggered Sweep CRO	188
7.9	Trigger Pulse Circuit	189
7.10	Delay Line in Triggered Sweep	190
7.11	Sync Selector for Continuous Sweep CRO	191
7.12	Typical CRT Connections	191
7.13	High Frequency CRT or Travelling Wave Type CRT	192
7.14	Dual Beam CRO	193
7.15	Dual Trace Oscilloscope	194
7.16	Electronic Switch	200
7.17	(VHF) Sampling Oscilloscope	201
7.18	Storage Oscilloscope (For VLF Signal)	202
7.19	Digital Readout Oscilloscope	204
7.20	Measurement of Frequency by Lissajous Method	206
7.21	Spot Wheel Method	208
7.22	Gear Wheel Method	209
7.23	Checking of Diodes	211
7.24	Basic Measurement of Capacitance and Inductance	211
7.25	Oscilloscope as a Bridge Null Detector	213
7.26	Use of Lissajous Figures for Phase Measurement	214
7.27	Standard Specifications of a Single Beam CRO	216
7.28	Probes for CRO	217
7.29	Attenuators	220

7.30	Applications of Oscilloscope	222
7.31	Delayed Sweep	223
7.32	Digital Storage Oscilloscope (DSO)	224
7.33	Fibre Optic CRT Recording Oscilloscope	226
7.34	Oscilloscope Operating Precautions	228
7.35	Placing an Oscilloscope in Operation	229
	<i>Review Questions</i>	230
	<i>Multiple Choice Questions</i>	231
	<i>Practice Problems</i>	232
	<i>Further Reading</i>	232
8.	Signal Generators	233
8.1	Introduction	233
8.2	Fixed Frequency AF Oscillator	234
8.3	Variable AF Oscillator	234
8.4	Basic Standard Signal Generator (Sine Wave)	235
8.5	Standard Signal Generator	235
8.6	Modern Laboratory Signal Generator	236
8.7	AF Sine and Square Wave Generator	238
8.8	Function Generator	239
8.9	Square and Pulse Generator (Laboratory Type)	240
8.10	Random Noise Generator	242
8.11	Sweep Generator	243
8.12	TV Sweep Generator	244
8.13	Marker Generator	245
8.14	Sweep-Marker Generator	247
8.15	Wobbluscope	247
8.16	Video Pattern Generator	247
8.17	Colour Bar Generator	249
8.18	Vectroscope	253
8.19	Beat Frequency Oscillator (BFO)	255
8.20	Standard Specifications of a Signal Generator	256
	<i>Review Questions</i>	257
	<i>Multiple Choice Questions</i>	258
	<i>Further Reading</i>	259
9.	Wave Analyzers and Harmonic Distortion	260
9.1	Introduction	260
9.2	Basic Wave Analyzer	261
9.3	Frequency Selective Wave Analyzer	262
9.4	Heterodyne Wave Analyzer	263
9.5	Harmonic Distortion Analyzer	265
9.6	Spectrum Analyzer	267
9.7	Digital Fourier Analyzer	269

9.8	Practical FFT Spectrum Analysis Using a Waveform Processing Software (Ss-36)	273
	<i>Review Questions</i>	276
	<i>Multiple Choice Questions</i>	277
	<i>Further Reading</i>	277
10.	Measuring Instruments	278
10.1	Introduction	278
10.2	Output Power Meters	278
10.3	Field Strength Meter	279
10.4	Stroboscope	280
10.5	Phase Meter	281
10.6	Vector Impedance Meter (Direct Reading)	283
10.7	Q Meter	286
10.8	LCR Bridge	295
10.9	RX Meters	303
10.10	Automatic Bridges	304
10.11	Transistor Tester	305
10.12	Megger	310
10.13	Analog pH Meter	311
10.14	Telemetry	315
	<i>Review Questions</i>	319
	<i>Multiple Choice Questions</i>	320
	<i>Practice Problems</i>	321
	<i>Further Reading</i>	321
11.	Bridges	322
11.1	Introduction	322
11.2	Wheatstone's Bridge (Measurement of Resistance)	322
11.3	Kelvin's Bridge	328
11.4	Practical Kelvin's Double Bridge	331
11.5	Bridge Controlled Circuits	332
11.6	Digital Readout Bridges	334
11.7	Microprocessor Controlled Bridges	335
11.8	AC Bridges	336
11.9	Capacitance Comparison Bridge	337
11.10	Inductance Comparison Bridge	339
11.11	Maxwell's Bridge	340
11.12	Hay's Bridge	342
11.13	Schering's Bridge	345
11.14	Wien's Bridge	351
11.15	Wagner's Earth (Ground) Connection	354
11.16	Resonance Bridge	355
11.17	Maxwell–Wien Bridge	3356

- 11.18 Anderson Bridge 358
- 11.19 The Owen Bridge 359
- 11.20 De Sauty Bridge 360
- 11.21 Carey Foster / Heydweiller Bridge 361
- 11.22 Types of Detectors 363
- 11.23 Precautions to be Taken When Using a Bridge 363
 - Review Questions* 364
 - Multiple Choice Questions* 365
 - Practice Problems* 366
 - Further Reading* 369

12. Recorders **370**

- 12.1 Introduction 370
- 12.2 Strip Chart Recorder 371
- 12.3 Galvanometer Type Recorder 374
- 12.4 Null Type Recorder (Potentiometric Recorders) 376
- 12.5 Circular Chart Recorder 381
- 12.6 X–Y Recorder 382
- 12.7 Magnetic Recorders 385
- 12.8 Frequency Modulation (FM) Recording 388
- 12.9 Digital Data Recording 390
- 12.10 Objectives and Requirements of Recording Data 392
- 12.11 Recorder Selections for Particular Applications 393
- 12.12 Recorder Specifications 393
- 12.13 Potentiometric Recorder (Multipoint) 394
- 12.14 Digital Memory Waveform Recorder (DWR) 399
- 12.15 Applications of a Strip Chart Recorder 401
 - Review Questions* 403
 - Multiple Choice Questions* 404
 - Practice Problems* 405
 - Further Reading* 405

13. Transducers **406**

- 13.1 Introduction 406
- 13.2 Electrical Transducer 406
- 13.3 Selecting a Transducer 408
- 13.4 Resistive Transducer 408
- 13.5 Resistive Position Transducer 411
- 13.6 Strain Gauges 413
- 13.7 Resistance Thermometer 423
- 13.8 Thermistor 425
- 13.9 Inductive Transducer 428
- 13.10 Differential Output Transducers 432
- 13.11 Linear Variable Differential Transducer (LVDT) 433

13.12	Pressure Inductive Transducer	440
13.13	Capacitive Transducer (Pressure)	446
13.14	Load Cell (Pressure Cell)	448
13.15	Piezo Electrical Transducer	449
13.16	Photo Electric Transducer	451
13.17	Photo-Voltaic Cell	454
13.18	Semiconductor Photo Diode	454
13.19	The Photo-Transistor	455
13.20	Temperature Transducers	456
13.21	Frequency Generating Transducer	479
13.22	Reluctance Pulse Pick-Ups	479
13.23	Flow Measurement (Mechanical Transducers)	479
13.24	Mechanical Flow Meter	480
13.25	Magnetic Flow Meters	480
13.26	Turbine Flowmeter	483
13.27	Measurements of Thickness Using Beta Gauge	484
	<i>Review Questions</i>	488
	<i>Multiple Choice Questions</i>	491
	<i>Further Reading</i>	492
14.	Signal Conditioning	493
14.1	Introduction	493
14.2	Operational Amplifier (OPAMP)	497
14.3	Basic Instrumentation Amplifier	511
14.4	Applications of Instrumentation Amplifiers (Specific Bridge)	518
14.5	Chopped and Modulated DC Amplifier	521
14.6	Modulators	522
	<i>Review Questions</i>	530
	<i>Further Reading</i>	531
15.	Filters	532
15.1	Introduction	532
15.2	Fundamental Theorem of Filters	532
15.3	Passive Filters	536
15.4	Active Filters	540
15.5	Butterworth Filter	544
15.6	Band Pass Filter	554
15.7	Band Reject (Stop) Filter	562
15.8	All Pass Filter	564
15.9	Universal Active Filters	566
15.10	Designing Procedures for FLT-U2	568
15.11	Types of Active Filters	572
15.12	Digital Filters	574
15.13	Discrete Functions	575

15.14	The 1-D Sampling Theorem	576	
15.15	The 2-D Sampling Theorem	576	
15.16	The 1-D Z-Transform	576	
15.17	Fundamental Properties of 1-D Digital Systems	577	
15.18	Fundamental Property of 2-D Digital Systems	578	
15.19	Frequency Domain Representation	578	
15.20	Fir 1-D Digital Filter Design (The Window Method)	583	
15.21	Design Methods for IIR Digital Filters	585	
15.22	1-D IIR Filter Design	587	
15.23	Program for the Design of Butterworth and Chebyshev IIR Digital Filters by Means of the Bilinear Transformation	591	
15.24	Microprocessor Based Digital Filter	595	
15.25	Applications of Digital Filters	596	
	<i>Review Questions</i>	600	
	<i>Multiple Choice Questions</i>	603	
	<i>Practice Problems</i>	604	
	<i>Further Reading</i>	604	
16.	Measurement Set-up		605
16.1	Introduction	605	
16.2	Measurements of Microwave Frequencies	605	
16.3	Resonant Co-Axial Lines	606	
16.4	Cavity Wavemeters	607	
16.5	RF/UHF Field Strength Meter (Methods for Measuring the Strength of Radio Waves)	607	
16.6	Measurement of Sensitivity	608	
16.7	Measurement of Selectivity	609	
16.8	Intermodulation Method of Measuring Non-Linear Distortion	610	
16.9	Measuring Frequency Response in Audio Amplifiers	614	
16.10	Modulation	615	
16.11	Measuring Frequency Modulation	618	
16.12	Measuring Frequency Deviation with a Radio Receiver	618	
16.13	Measuring Amplitude Modulation Using CRO	619	
	<i>Review Questions</i>	623	
	<i>Multiple Choice Questions</i>	624	
	<i>Further Reading</i>	625	
17.	Data Acquisition System (DAS)		626
17.1	Introduction	626	
17.2	Objective of a DAS	628	
17.3	Signal Conditioning of the Inputs	628	
17.4	Single Channel Data Acquisition System	630	
17.5	Multi-Channel DAS	632	
17.6	Computer Based DAS	636	

17.7	Digital to Analog (D/A) and Analog to Digital (A/D) Converters	637
17.8	Data Loggers	653
17.9	Sensors Based Computer Data Systems	663
17.10	Electromechanical A/D Converter	671
17.11	Digital Transducer	673
	<i>Review Questions</i>	675
	<i>Multiple Choice Questions</i>	677
	<i>Practice Problems</i>	678
	<i>Further Reading</i>	679
18.	Data Transmission	680
18.1	Introduction	680
18.2	Data Transmission Systems	682
18.3	Advantages and Disadvantages of Digital Transmission Over Analog	682
18.4	Time Division Multiplexing (TDM)	684
18.5	Pulse Modulation	686
18.6	Digital Modulation	695
18.7	Pulse Code Format	704
18.8	Modems	706
	<i>Review Questions</i>	710
	<i>Multiple Choice Questions</i>	711
	<i>Further Reading</i>	712
19.	Frequency Standards	713
19.1	Introduction	713
19.2	Primary Standards	713
19.3	Secondary Standards of Frequency	714
19.4	Practical Frequency Standards	714
19.5	Radio Signals as Frequency Standards	715
19.6	Precision Frequency Standards	715
19.7	The Atomic Clock	716
	<i>Review Questions</i>	717
	<i>Multiple Choice Questions</i>	717
	<i>Further Reading</i>	717
20.	Measurement of Power	718
20.1	Introduction	718
20.2	Requirements of a Dummy Load	718
20.3	Bolometer	718
20.4	Bolometer Method of Power Measurement	719
20.5	Bolometer Element	719
20.6	Bolometer Mount	720
20.7	Measurement of Power by Means of a Bolometer Bridge	720

20.8	Unbalanced Bolometer Bridge	722
20.9	Self Balancing Bolometer Bridge	723
20.10	Measurement of Large Amount of RF Power (Calorimetric Method)	724
20.11	Measurement of Power on a Transmission Line	726
20.12	Standing Wave Ratio Measurements	727
20.13	Measurement of Standing Wave Ratio Using Directional Couplers	728
	<i>Review Questions</i>	731
	<i>Multiple Choice Questions</i>	732
	<i>Practice Problems</i>	732
	<i>Further Reading</i>	732
21.	Control Systems	733
21.1	Basic Control Action	733
21.2	Definition (Terminology)	734
21.3	On–Off Control Action	736
21.4	Proportional Control Action	738
21.5	Offset	739
21.6	Basic Controller Configuration	739
21.7	Classification of Controllers	740
21.8	Electronic Controllers (EC)	740
21.9	Analog Electronic Process Controllers	741
21.10	Temperature Control using an Analog Electronic Controller	745
21.11	Choice of Electronic Transmission Signal	747
21.12	Digital Controllers	748
21.13	Digital Process Controller	750
21.14	Cascade Process Controller with Digital Controllers	751
21.15	Programmable Logic Controller	752
21.16	Distributed Control Systems	796
	<i>Review Questions</i>	815
	<i>Further Reading</i>	816
	<i>Answers to Objective Type Questions</i>	817
	<i>Index</i>	820